

Two-layer demonstration board based on the STA333IS

Introduction


The board shown in [Figure 1](#) is a two-layer demonstration board designed for the evaluation of the STA333IS two-channel, high-efficiency Sound Terminal[®] device.

The purpose of this application note is to show:

- how to connect the STA333IS demonstration board
- the performance of the STA333IS device
- how to avoid critical board and layout issues

All the results and characterization data included in this application note have been measured using Audio Precision equipment. Reference documents consist of the STA333IS datasheet, schematic diagrams and PCB layout.

Figure 1. STA333IS 2 layer demo board

 

Contents

- 1 Test conditions and connections of demonstration board 4**
 - 1.1 Power supply signal and interface connection 4
 - 1.2 Output configuration 4
 - 1.3 Required equipment 4
 - 1.4 Board connections 5

- 2 Schematic diagram and PCB layout 6**
 - 2.1 Schematic 6
 - 2.2 PCB layout 7
 - 2.3 Bill of material 9

- 3 APWorkbench settings 10**

- 4 Test results 11**

- 5 Thermal performance 15**

- 6 Design guidelines for schematic and PCB layout 16**
 - 6.1 General 16
 - 6.2 Decoupling capacitors 16
 - 6.3 Output filter 16
 - 6.3.1 Snubber network 16
 - 6.3.2 Main filter 17
 - 6.3.3 Damping network 17
 - 6.4 PCB layout 18
 - 6.4.1 Snubber network 18
 - 6.4.2 Electrolytic capacitor 18
 - 6.4.3 Ground plane and heatsink 19
 - 6.4.4 PCB symmetrical paths 20
 - 6.4.5 V_{CC} filter for high frequency 21

- 7 Revision history 22**

List of figures

Figure 1.	STA333IS 2 layer demo board	1
Figure 2.	Demonstration board (two-layer) - connectors	5
Figure 3.	Schematic diagram - part 1.	6
Figure 4.	Schematic diagram - part 2 (connectors)	7
Figure 5.	STA333IS demonstration board - two-layer PCB (top view).	7
Figure 6.	STA333IS demonstration board - two-layer PCB (bottom view).	8
Figure 7.	APWorkbench - device selection	10
Figure 8.	APWorkbench - control panel	10
Figure 9.	THD+N vs. power - $V_{CC} = 12\text{ V}$, load = 8 W, 1 kHz	11
Figure 10.	THD+N vs. frequency - $V_{CC} = 12\text{ V}$, load = 8 W, $P_{out} = 1\text{ W}$ at 1 kHz.	11
Figure 11.	Frequency response - $V_{CC} = 12\text{ V}$, load = 8 W, $P_{out} = 1\text{ W}$ at 1 kHz	12
Figure 12.	Crosstalk - $V_{CC} = 12\text{ V}$, load = 8 W, $P_{out} = 1\text{ W}$ at 1 kHz	12
Figure 13.	FFT - $V_{CC} = 12\text{ V}$, load = 8 W, $P_{out} = 1\text{ W}$ at 1 kHz.	13
Figure 14.	Output power vs. supply voltage - load = 8 W, 1 kHz.	13
Figure 15.	Efficiency - $V_{CC} = 12\text{ V}$, 1 kHz, load = 8 W (stereo)	14
Figure 16.	Thermal performance	15
Figure 17.	Output filter	16
Figure 18.	Main filter	17
Figure 19.	Damping network	17
Figure 20.	Snubber network.	18
Figure 21.	Electrolytic capacitor.	18
Figure 22.	Ground plane	19
Figure 23.	Output path	20
Figure 24.	Coils	21
Figure 25.	V_{CC} filter capacitors	21

1 Test conditions and connections of demonstration board

1.1 Power supply signal and interface connection

1. Connect the power supply to the +V_{CC} and GND terminal blocks (J2)
2. Connect the STEVAL-CCA035V1 interface board to the J4 connector
3. Connect the S/PDIF signal cable to the RCA jack on the STEVAL-CCA035V1 board. The signal source should be the Audio Precision equipment or a DVD player.
4. Adjust the voltage level of the power supply. The voltage range of the DC power supply is 4.5 V to 18 V.
5. Connect the load to the connectors J1 and J3

1.2 Output configuration


The STA333IS demonstration board can be only configured for 2.0 channels and BTL outputs.

1.3 Required equipment

- Audio Precision (System 2700)
 - Audio Analyzer: Mod. SYS2722 -192K
 - Class-D filter: AUX-0025 filter
 - Multifunction module: DCX-127
- DC power supply (4.5 V to 18 V)
 - Lambda Genesys Gen 80-19
 - HP 6038A
- Digital oscilloscope: Tektronix TDS5054B
- Digital multimeter: AGILENT Mod. 34410A
- PC with APWorkbench control software installed

1.4 Board connections

Figure 2. Demonstration board (two-layer) - connectors

 

2 Schematic diagram and PCB layout

2.1 Schematic

Figure 3. Schematic diagram - part 1


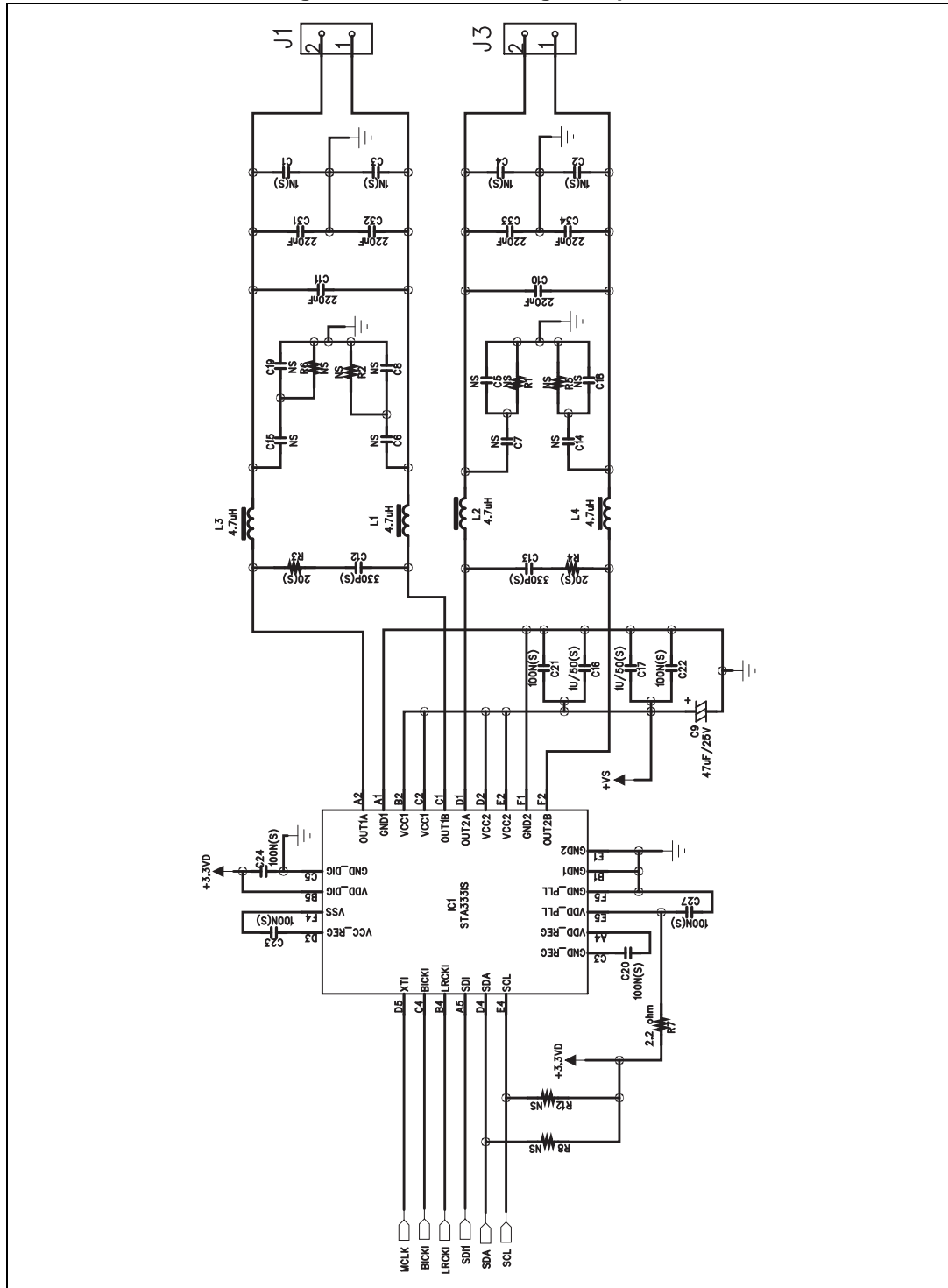


Figure 4. Schematic diagram - part 2 (connectors)

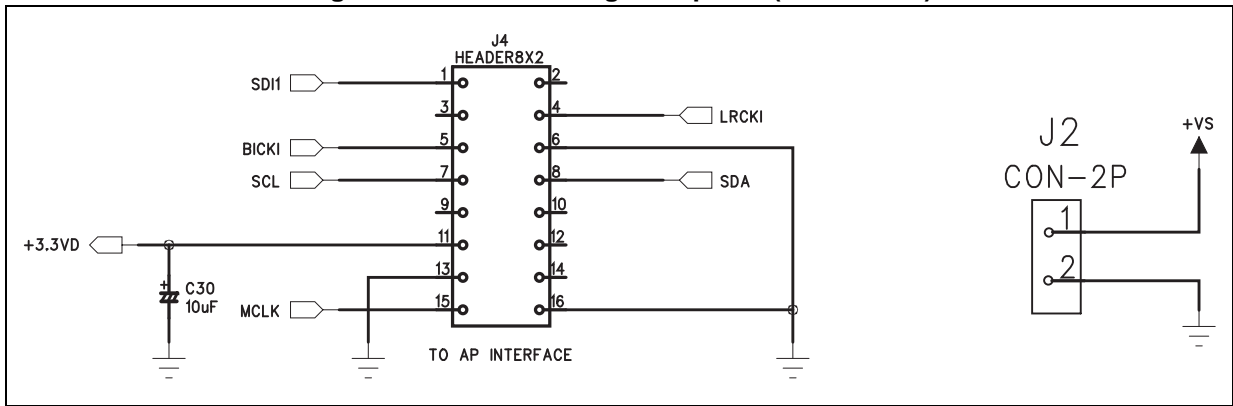

2.2 PCB layout

Figure 5. STA333IS demonstration board - two-layer PCB (top view)


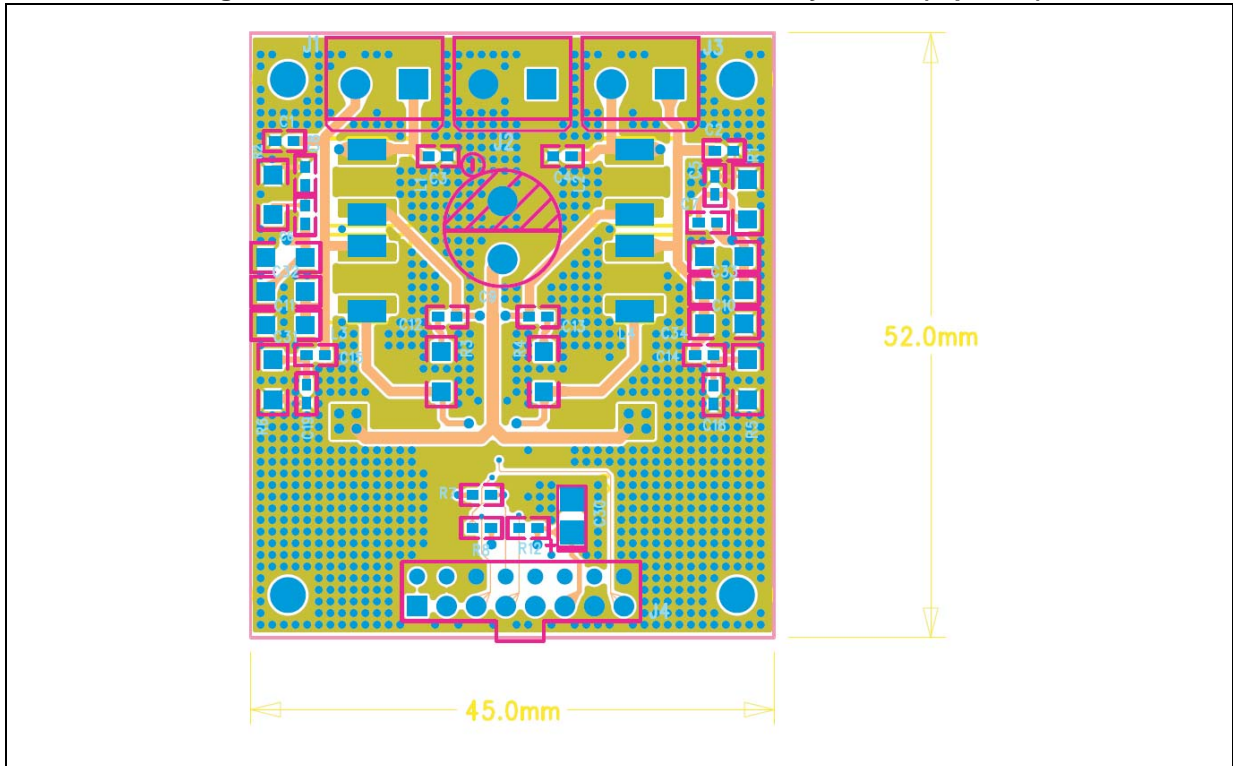


Figure 6. STA333IS demonstration board - two-layer PCB (bottom view)

 

2.3 Bill of material

Table 1. Bill of material

N°	Type	Footprint	Description	Q.ty	Reference	Manufacturer
1	Connector	Through-hole	2P pitch: 5 mm connector terminal	3	J1, J2, J3	
2	Header	Through-hole	16P (8x2 row) 2.5 mm header	1	J4	
3	CCAP	CAP0603	50 Volt NPO 330 pF ±10%	2	C12, C13	Murata
4	CCAP	CAP0603	50 Volt 1 nF ±10%	4	C1, C2, C3, C4	Murata
5	CCAP	CAP0603	50 Volt 100 nF ±10%	6	C20, C21, C22, C23, C24, C27	Murata
6	CCAP	CAP0603	NS	8	C5, C6, C7, C8, C14, C15, C18, C19	Murata
7	CCAP	CAP1206	50 Volt 220 nF ±10%	6	C10, C11, C31, C32, C33, C34	Murata
8	CCAP	CAP1206	50 Volt 1U ±10%	2	C16, C17	Murata
9	ECAP	CAP1206	10 µF / 16 V	1	C30	Samsung
10	ECAP	Through-hole	47 µF / 25 V, pitch = 5 mm, φ10 mm	1	C9	Panasonic
11	RES	R1206	NS	4	R1, R2, R5, R6	Murata
12	RES	R1206	20 ±5% 1/8W	2	R3, R4	Murata
13	RES	R0603	2R2 ±5% 1/16W	1	R7	Murata
14	RES	R0603	NS	2	R8, R12	
15	Plastic rod		Hexagonal rod 15 mm length, male type	4	Four corners	
16	Plastic rod		Hexagonal rod 8 mm length, female type	4	Four corners	
17	IC	BGA30	STA333IS	1	IC1	STMicroelectronics
18	Coil	SMD	SWPA6045S4R7MT, 4.7 µH	4	L1, L2, L3, L4	Sunlord
19	PCB		STA333IS CSP 2-layer 1V1	1		Fastprint

3 APWorkbench settings

Figure 7. APWorkbench - device selection


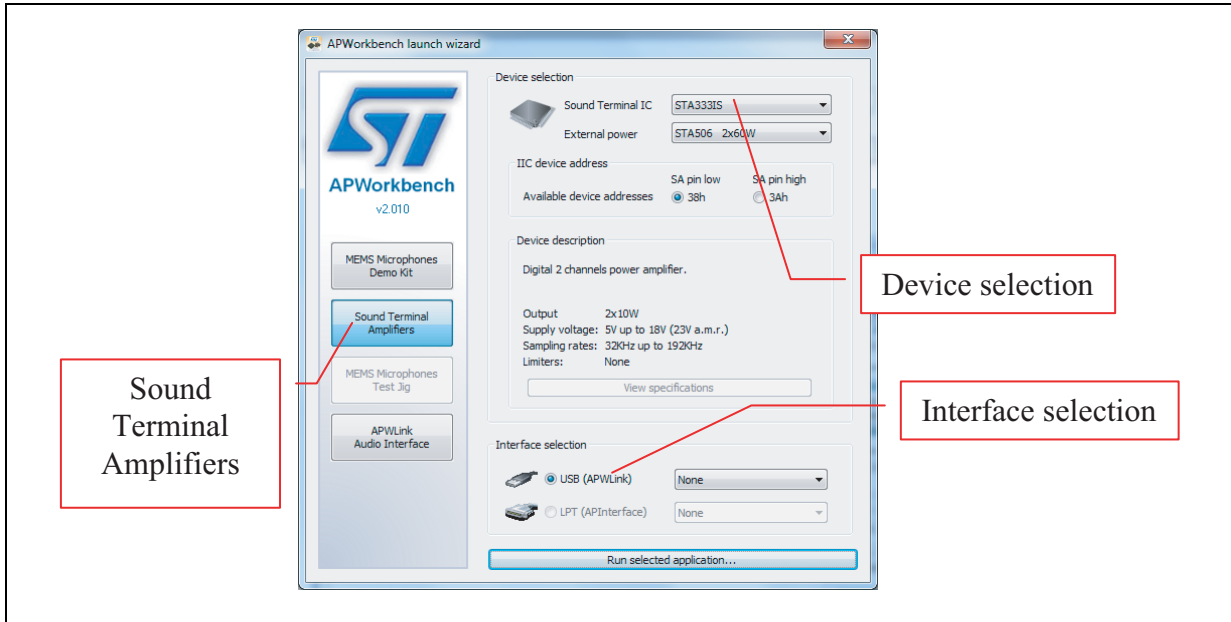


Figure 8. APWorkbench - control panel

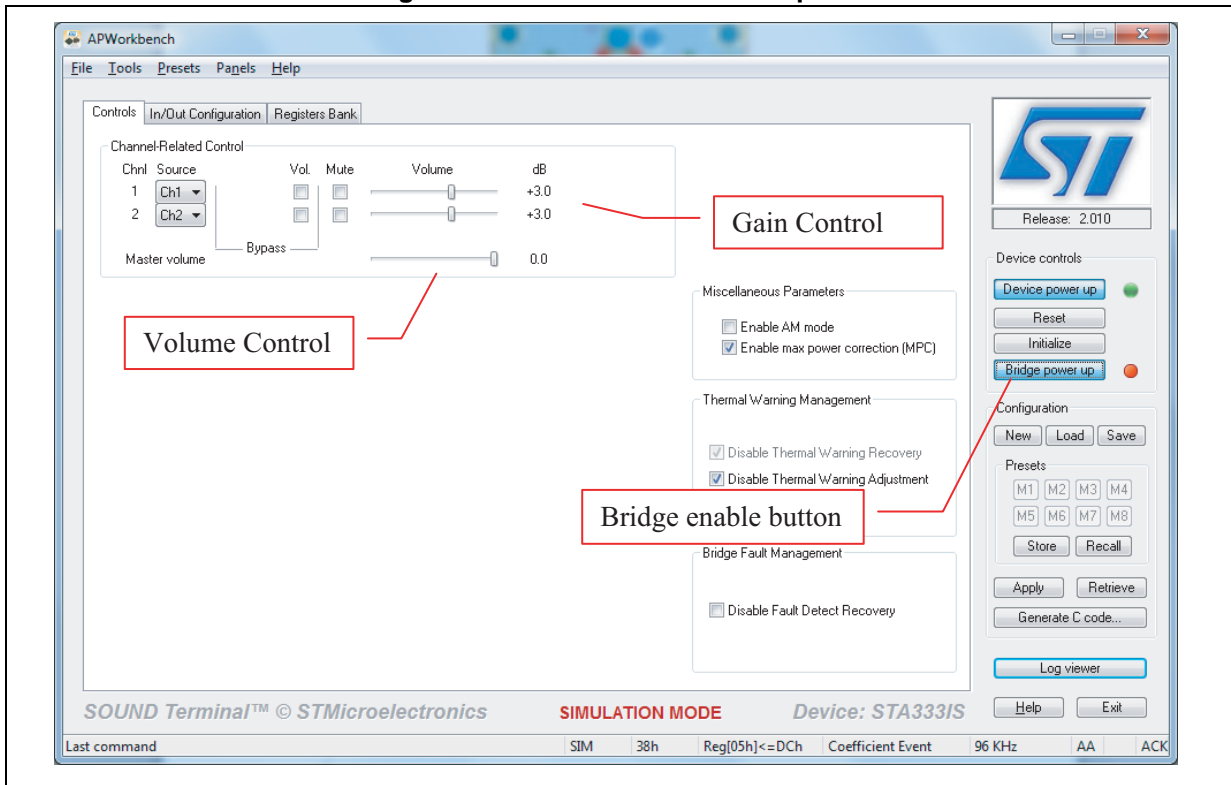

4 Test results

Figure 9. THD+N vs. power - $V_{CC} = 12\text{ V}$, load = $8\ \Omega$, 1 kHz

 


Figure 10. THD+N vs. frequency - $V_{CC} = 12\text{ V}$, load = $8\ \Omega$, $P_{out} = 1\text{ W}$ at 1 kHz

 


Figure 11. Frequency response - $V_{CC} = 12\text{ V}$, load = $8\ \Omega$, $P_{out} = 1\text{ W}$ at 1 kHz

 


Figure 12. Crosstalk - $V_{CC} = 12\text{ V}$, load = $8\ \Omega$, $P_{out} = 1\text{ W}$ at 1 kHz

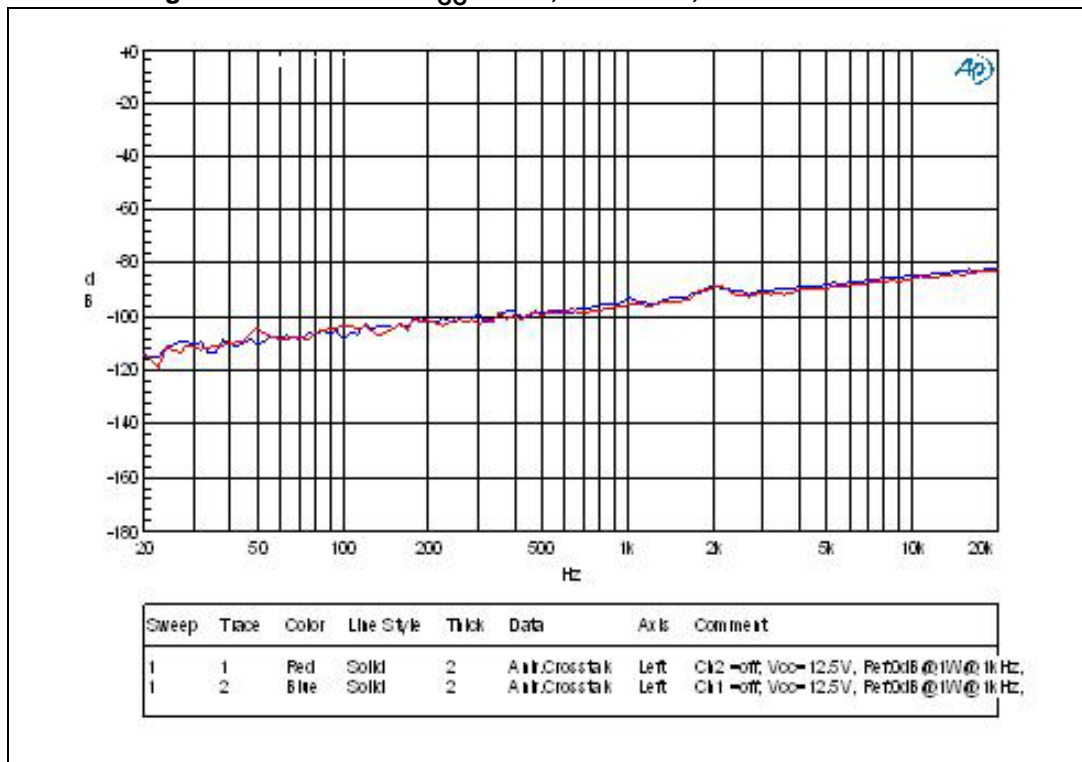


Figure 13. FFT - $V_{CC} = 12\text{ V}$, load = $8\ \Omega$, $P_{out} = 1\text{ W}$ at 1 kHz

 


Figure 14. Output power vs. supply voltage - load = $8\ \Omega$, 1 kHz


 


Figure 15. Efficiency - $V_{CC} = 12\text{ V}$, 1 kHz, load = $8\ \Omega$ (stereo)

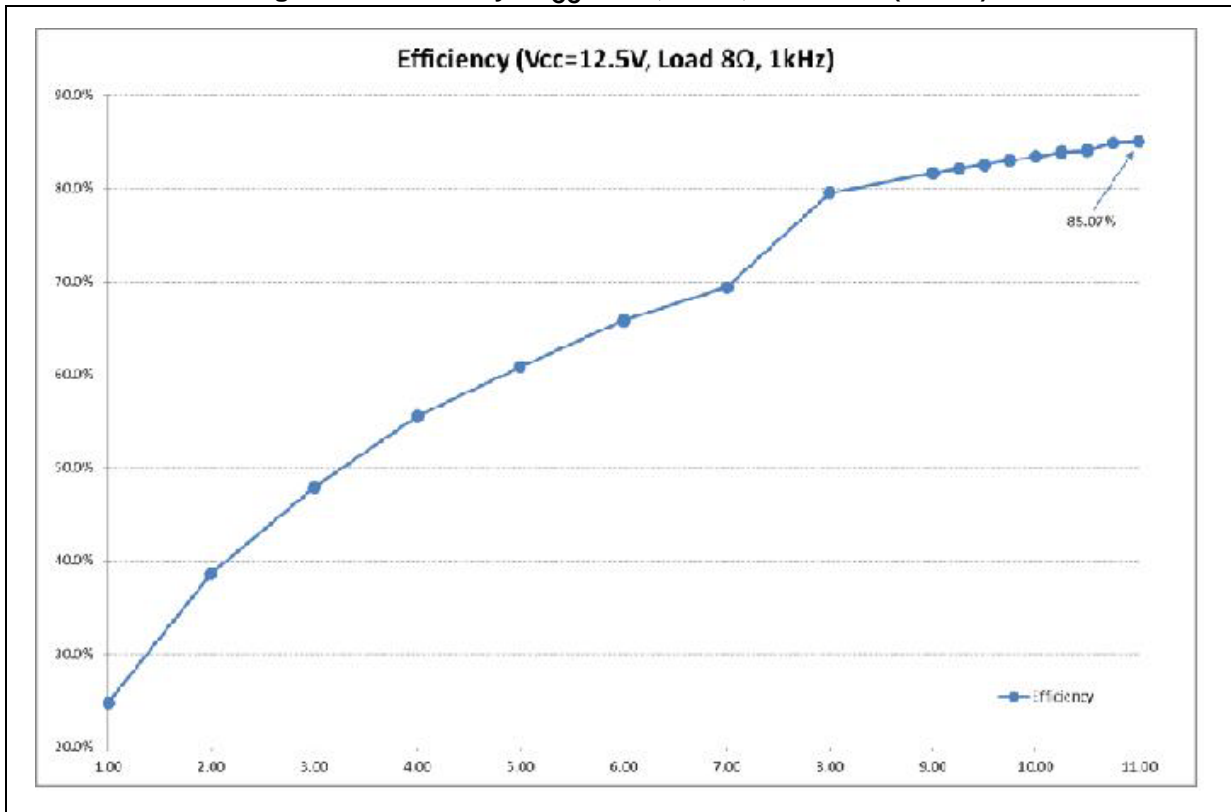


5 Thermal performance

Test conditions:

- $V_{CC} = 12\text{ V}$
- 1 kHz sine wave
- Load = $2 \times 8\ \Omega$
- Output power: $2 \times 10\text{ W}$

Figure 16. Thermal performance

 

	Tamb = 25 °C	Tamb = 40 °C
IC temp	78°C	93°C

6 Design guidelines for schematic and PCB layout

6.1 General


- Absolute maximum rating: 20 V
- Bypass capacitor 100 nF in parallel to 1 μF and 10 μF for each power V_{CC} branch. Preferable dielectric is X7R.
- V_{dd} and ground for the digital section should be separated from the other power supply.
- Coil saturation current compatible with the peak current of the application

6.2 Decoupling capacitors

The decoupling capacitors can be shared for each V_{CC} branch. The decoupling capacitors must be placed as close as possible to the IC pins.

6.3 Output filter

Figure 17. Output filter

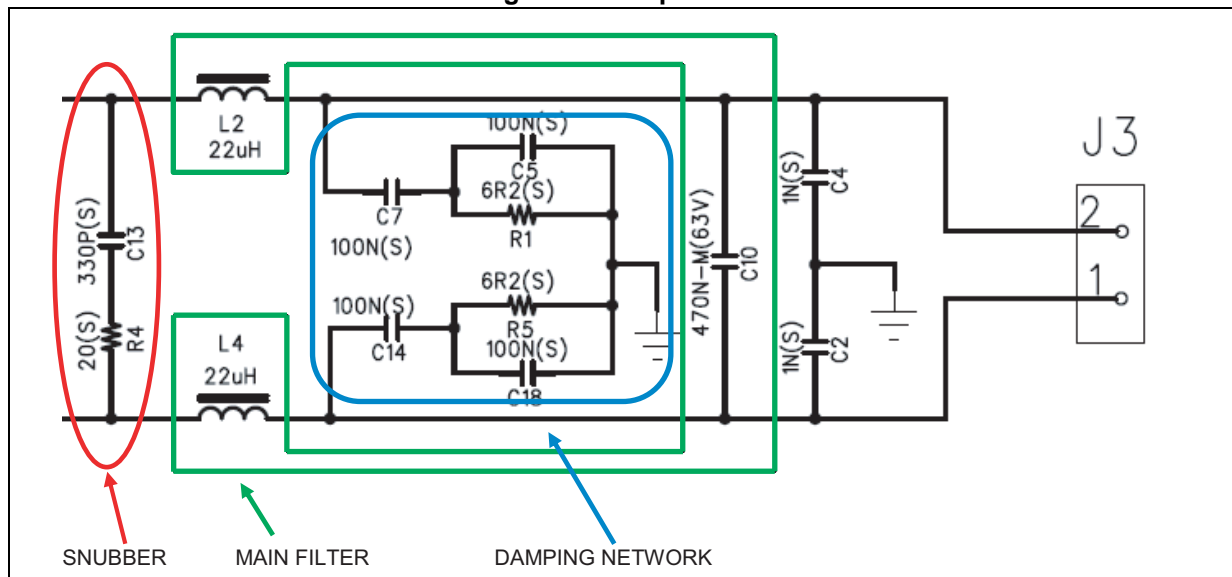

6.3.1 Snubber network

The snubber circuit must be optimized for the specific application. Starting values are 330 pF in series to 22 Ω.

The power dissipation in this network can be defined by the following formula which considers the power supply, frequency and capacitor value:


$$P = C \cdot \text{Freq}_{\text{PWM}} \cdot (2 \cdot V_{\text{out}})^2$$

This power is dissipated on the series resistance.

6.3.2 Main filter

The main filter is an L and C based Butterworth filter. The cut-off frequency must be chosen between the upper limit of the audio band (~20 kHz) and the carrier frequency (384 kHz).

Figure 18. Main filter

 

6.3.3 Damping network

The C-R-C is a damping network. It is mainly intended for high inductive loads where the speaker load could be disconnected.

Figure 19. Damping network

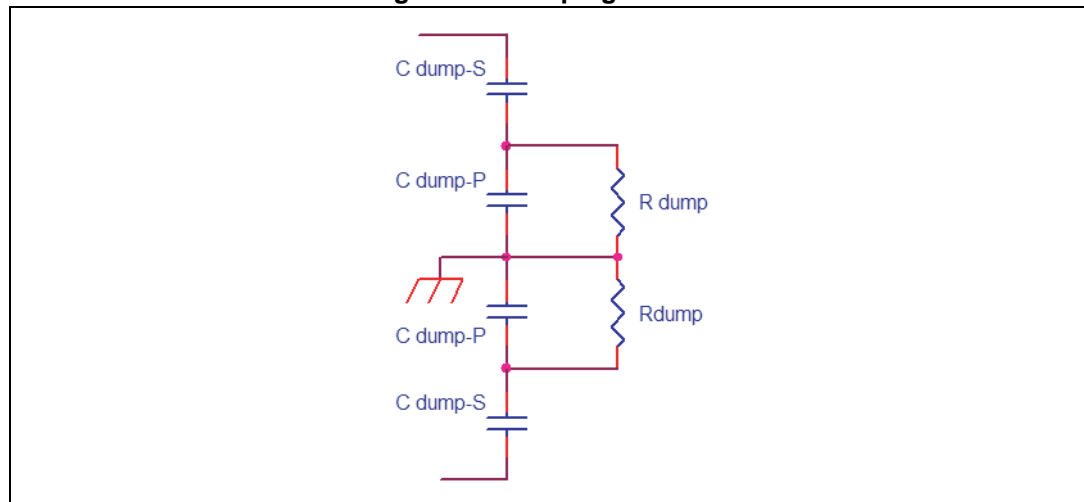


Table 2. Recommended values for main filter and damping network


	Rload	16 Ω	12 Ω	8 Ω	6 Ω	4 Ω
Main filter	Lload	47 μH	33 μH	22 μH	15 μH	10 μH
	Cload	220 nF	330 nF	470 nF	680 nF	1 μF
Damping network	C damp-S	100 nF	100 nF	100 nF	100 nF	220 nF
	C damp-P	100 nF	100 nF	100 nF	100 nF	220 nF
	R damp	10 Ω	8.2 Ω	6.2 Ω	4.7 Ω	2.7 Ω

6.4 PCB layout

6.4.1 Snubber network

Solder the snubber network as close as possible to the related IC pin.


Figure 20. Snubber network

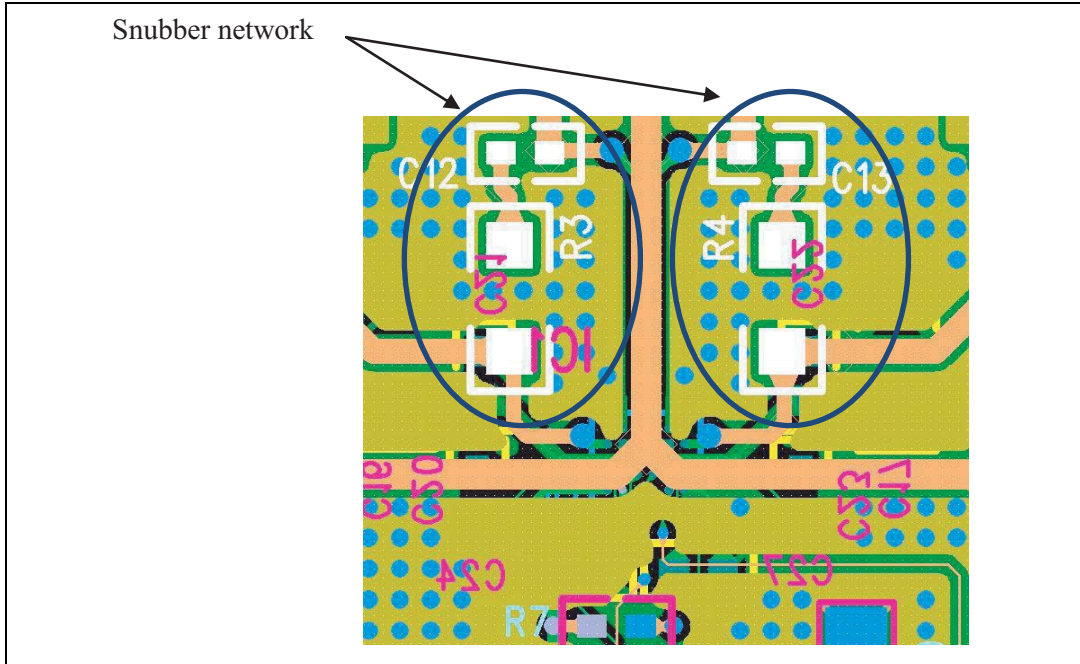

6.4.2 Electrolytic capacitor

Place the electrolytic capacitor first to separate the Vcc branches.


Figure 21. Electrolytic capacitor

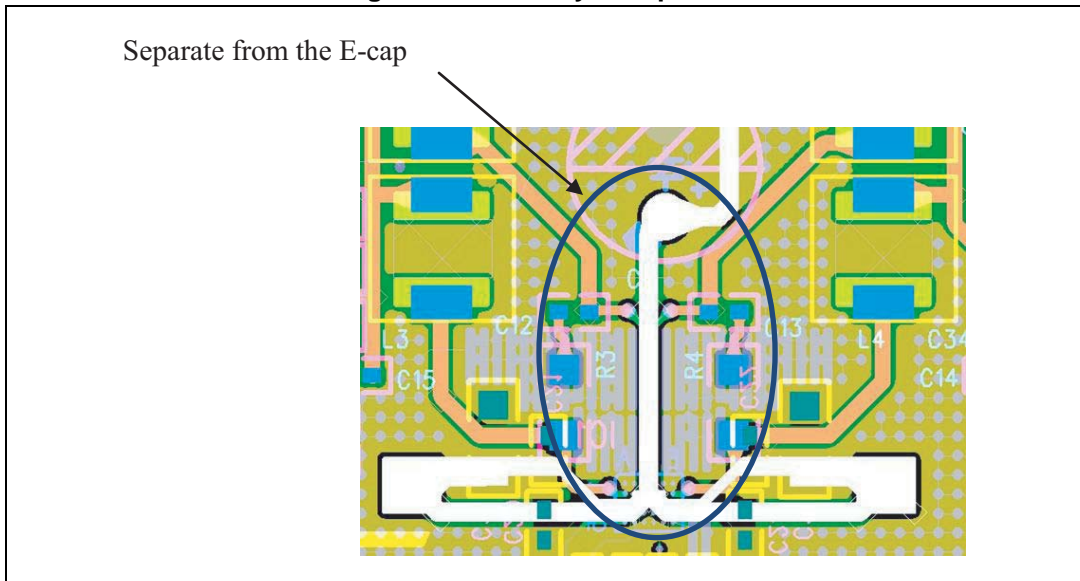

6.4.3 Ground plane and heatsink

In order to dissipate the heat, a large ground plane is used. It is mandatory to have a large ground plane on the top and bottom layers and solder the slug on the PCB.


Figure 22. Ground plane

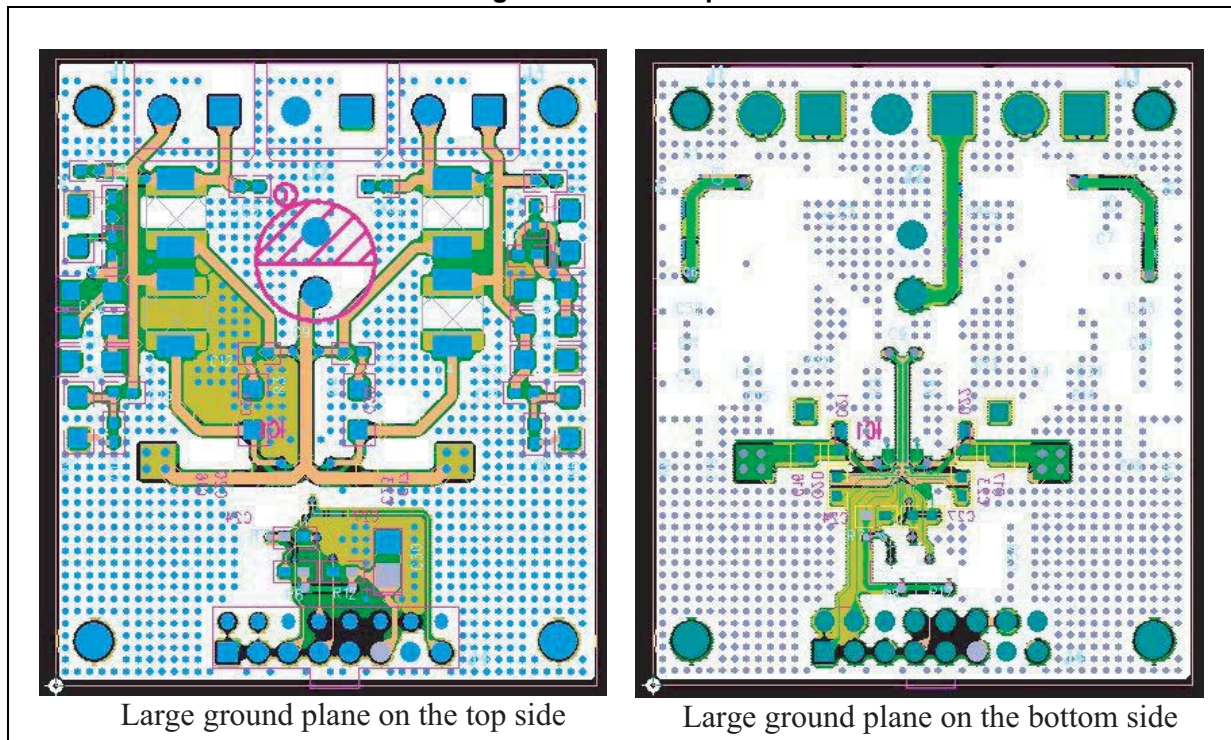

6.4.4 PCB symmetrical paths


For differential applications, creating symmetrical paths for the output stage is recommended.

Figure 23. Output path

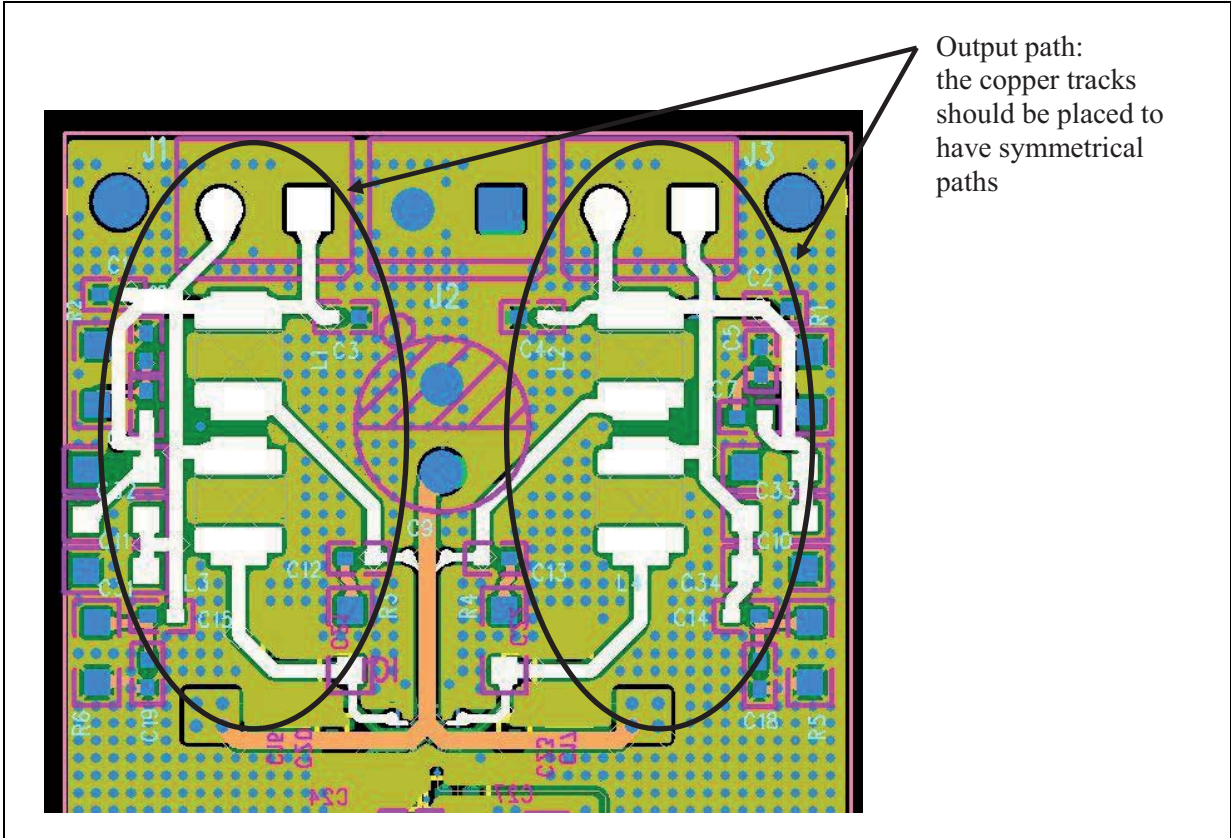

The coils must be separated to avoid crosstalk. Shielded parts must be used.


Figure 24. Coils

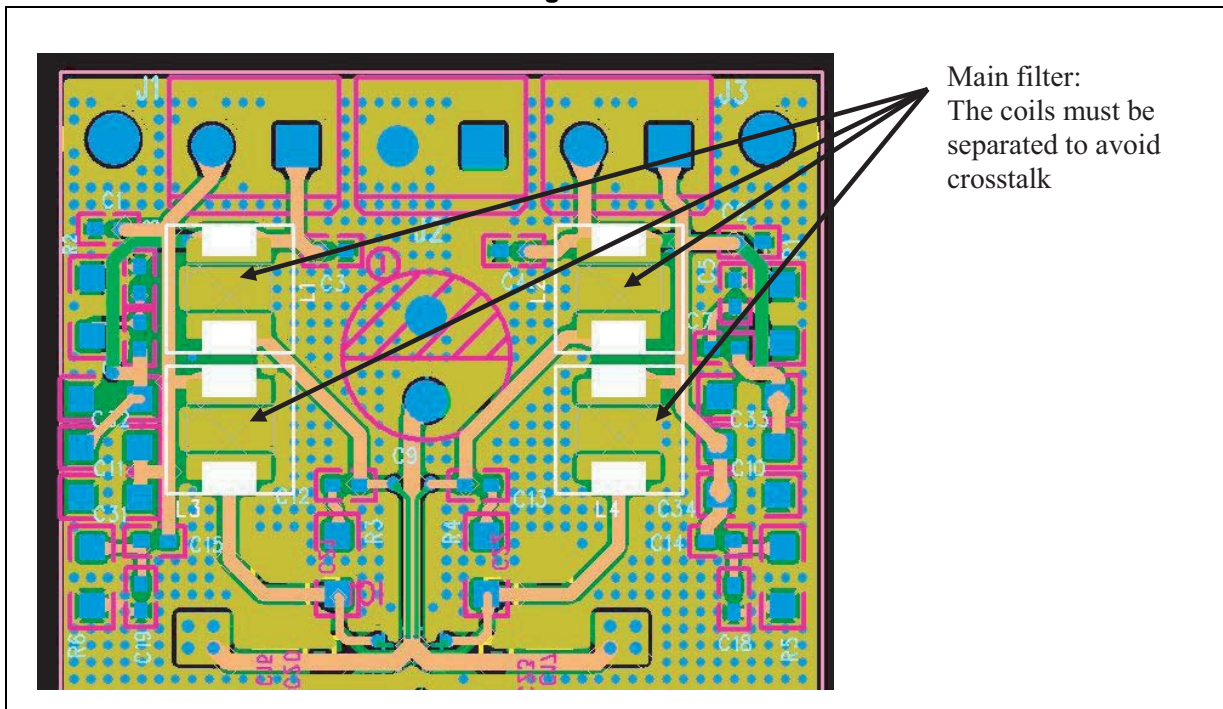

6.4.5 V_{CC} filter for high frequency

The V_{CC} filter capacitors must be placed as close as possible to the supply pins as well as the ceramic capacitors.

Figure 25. V_{CC} filter capacitors

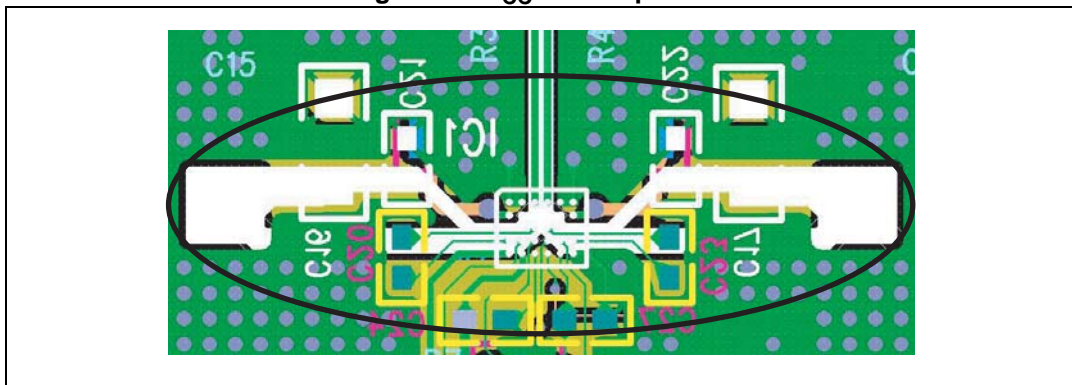

The PWM frequency is 384 kHz. In order to compensate the inductive effect of the copper track, the ceramic capacitors must be placed as close as possible to the supply pins. The recommended distance between the capacitors and the supply pins is less than 5 mm.

7 Revision history

Table 3. Document revision history

Date	Revision	Changes
01-Jul-2013	1	Initial release.

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

ST PRODUCTS ARE NOT AUTHORIZED FOR USE IN WEAPONS. NOR ARE ST PRODUCTS DESIGNED OR AUTHORIZED FOR USE IN: (A) SAFETY CRITICAL APPLICATIONS SUCH AS LIFE SUPPORTING, ACTIVE IMPLANTED DEVICES OR SYSTEMS WITH PRODUCT FUNCTIONAL SAFETY REQUIREMENTS; (B) AERONAUTIC APPLICATIONS; (C) AUTOMOTIVE APPLICATIONS OR ENVIRONMENTS, AND/OR (D) AEROSPACE APPLICATIONS OR ENVIRONMENTS. WHERE ST PRODUCTS ARE NOT DESIGNED FOR SUCH USE, THE PURCHASER SHALL USE PRODUCTS AT PURCHASER'S SOLE RISK, EVEN IF ST HAS BEEN INFORMED IN WRITING OF SUCH USAGE, UNLESS A PRODUCT IS EXPRESSLY DESIGNATED BY ST AS BEING INTENDED FOR "AUTOMOTIVE, AUTOMOTIVE SAFETY OR MEDICAL" INDUSTRY DOMAINS ACCORDING TO ST PRODUCT DESIGN SPECIFICATIONS. PRODUCTS FORMALLY ESCC, QML OR JAN QUALIFIED ARE DEEMED SUITABLE FOR USE IN AEROSPACE BY THE CORRESPONDING GOVERNMENTAL AGENCY.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2013 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com

