

Guidelines for the buck voltage mode on the B-G474E-DPOW1 Discovery kit

Introduction

The B-G474E-DPOW1 discovery kit is a complete digital power starter kit controlled by the STM32G474RET6 microcontroller. The kit showcases the features of digital power including LED dimming, buck-boost with variable load, power delivery (USB Type-C®), and audio class-D amplification.

This document focuses on the onboard step-down converter of the discovery kit. It details: the principles of voltage-mode control, and how to design a compensator to stabilize and regulate the voltage-mode controlled step-down converter. It explains how to implement these on the STM32 microcontroller.

The document also presents the buck voltage-mode usage with the X-CUBE-DPOWER STM32Cube expansion package.

Figure 1. B-G474E-DPOW1 top view


 


Figure 2. B-G474E-DPOW1 bottom view

 

Pictures are not contractual.

1 General information

The B-G474E-DPOW1 discovery kit runs with the STMicroelectronics STM32G474RET6 microcontroller, based on an Arm® Cortex®-M4 core.


Note: Arm is a registered trademark of Arm Limited (or its subsidiaries) in the US and/or elsewhere.



2 Step-down converter operation

The B-G474E-DPOW1 Discovery kit contains a synchronous step-down converter power stage. The simplified schematic of the power stage is shown in [Figure 3](#).


Figure 3. Simplified power stage schematic

 

2.1 Principle of operation

The operation of the synchronous buck is as follows. At the beginning of the switching period, the PWM of the top switch (Q1) is set to HIGH and the bottom switch (Q2) is set to LOW. This turns on MOSFET Q1 and turns off MOSFET Q2. With the Q1 switch conducting, the current through the inductor L1 begins increasing linearly. At the end of the high-side duty cycle, switch Q1 is turned off.

A dead-time is inserted between the high-side and low-side PWM for switches Q1 and Q2 to prevent shoot-through, where both switches are partially on at the same time causing a large current to flow through Q1 and Q2 and can damage the MOSFETs. When this dead time has elapsed the low-side PWM for the switch Q2 goes HIGH, which turns on the switch Q2. At this time, the inductor acts to continue the flow of current and the current now flows through switch Q2. The current through the inductor begins decreasing linearly. This switching action is described in the waveforms of [Figure 4](#).

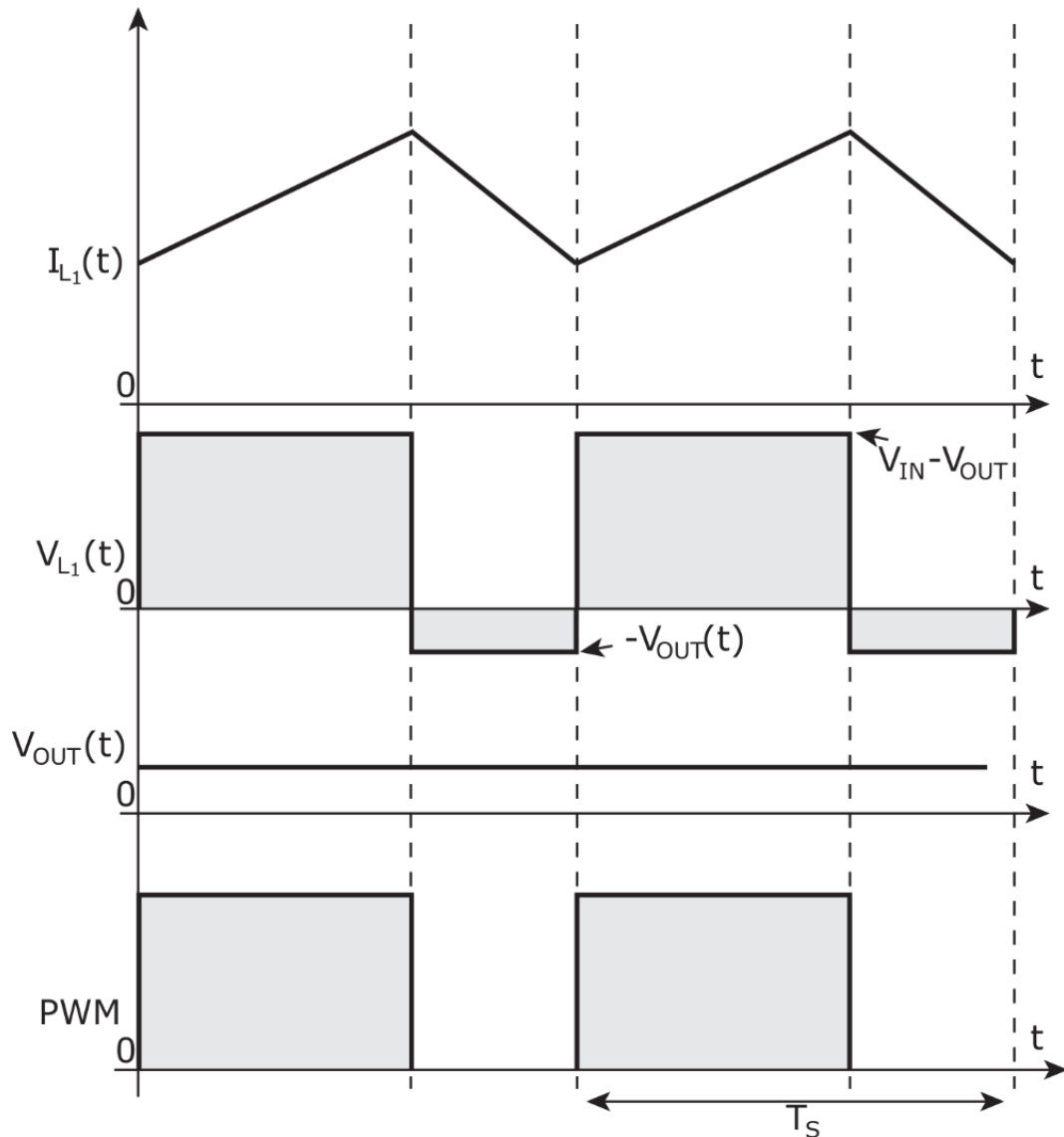Figure 4. Step-down converter operational waveforms


The output filter capacitor C_{out} filters the AC component of this current while the DC component of this current is the output load current, I_{out} . As this is a step-down converter, the output voltage is always less than or equal to the input voltage. In continuous conduction mode, the steady-state duty cycle of the high-side switch Q1 can be calculated in 1 as:

$$D = \frac{V_{out}}{V_{in}} \quad (1)$$

There are two main control methods for the step-down converter: namely voltage mode and peak current mode control. The software example preloaded onto the starter kit provides an example of a well-tuned digital voltage-mode controlled converter.

3 Voltage mode control explained

3.1 Advantages and disadvantages

Voltage mode control is one of the most popular control methods due to its simplicity and effectiveness in regulating an output voltage given any changes in load. Under voltage mode control, the output voltage is measured and compared with the desired set point or reference. The difference between the actual output voltage and the desired output voltage is used as an input to a controller and the output of the controller determines the new value of the duty cycle to close the control loop.


Therefore, unlike other methods of control such as peak current mode, the voltage mode controller only needs information about the output voltage to close the control loop and provide a regulated and stable output voltage. Typically, some current information is required to provide an overall power limit. Alternatively, this can be crudely achieved by limiting the maximum duty cycle.

Further advantages of voltage-mode control include the ability to step down the voltage by a significant amount and maintain proper regulation for small and no loads. The PCB layout process for a voltage-mode controlled step-down converter is typically simplified due to not requiring a switch or inductor current sense transducer, and voltage mode control is less sensitive to nonoptimal PCB layouts.

As discussed so far, voltage mode control has good load regulation. It compensates for any changes in load to maintain a set output voltage. However, in its standard implementation, voltage mode control has poor line regulation. There is a delay between the line voltage increasing or decreasing and the duty cycle adjusting to compensate for the subsequent change in output voltage. Therefore, it is common to add a *feed-forward* term to the control loop, which is a measure of the input voltage.

3.2 Step-by-step control loop

Figure 5. Step-down converter voltage control loop

 

The simplified control loop of a voltage mode converter is shown in Figure 5. Here, the power stage containing the switching MOSFET, output filter inductor, and output filter capacitor are all shown within the block $H_p(s)$. This is referred to as the plant transfer function. The controller, which is designed to compensate for this control loop, is shown as the block $H_C(s)$. This is referred to as the controller transfer function. The PWM block is usually included as part of the plant, $H_p(s)$ block, however, it is separated so that the effects of this block can be analyzed independently.

For this discussion, the current work is performed in the continuous-time domain, also known as the s-domain, and this is why the plant and controller are a function of the Laplace operator. The translation from the continuous-time domain to the discrete-time domain is discussed later in this application note.

At a steady state, the plant power stage provides a fixed output voltage given the fixed input voltage and duty cycle. In Figure 5 the output voltage of the power stage is fed back and compared with a reference, V_{REF} . This is the desired output voltage and therefore if there is any deviation from the reference there is a nonzero error term. The error term is used as an input to the controller, $H_C(s)$. The controller manipulates the error term in some way depending on the type of controller that is designed. The output of the controller is the duty cycle, which is used as an input to the power stage and modulates the MOSFET switches.

This closed-loop control process can be easily visualized through a numerical example. For now, let us assume that the controller $H_C(s)$ is a simple proportional controller with unity gain and the reference is the desired output voltage of 3.3 V.

If the output voltage dropped down to 3.2 V due to an increase in output load, then the error term can be calculated as follows:

$$V_{ERROR} = V_{REF} - V_{OUT}$$

$$V_{ERROR} = 3.3 V - 3.2 V$$

$$V_{ERROR} = 0.1 V$$

As the proportional controller has unity gain, the output of the controller can be calculated as follows:

$$H_C(s) = \frac{Y(s)}{X(s)}$$


$$Y(s) = H_C(s) \times X(s)$$

$$Y(s) = 1 \times 0.1 V$$

$$Y(s) = 0.1 V$$

The output of the controller is then used as an input for the PWM block. The PWM block takes the controller output and converts this to an effective duty cycle. There are several different methods for achieving this and, for analog voltage mode control, this is typically achieved using a PWM comparator and an RC ramp as shown in Figure 6.

Figure 6. PWM comparator comparing RC ramp to control voltage

 

DT71671V1

Within the PWM block the control voltage, V_{CTRL} , which is the output of the previous controller block, is compared with an RC ramp using a comparator. The output of the comparator is high when the control voltage is larger than the RC ramp voltage. Therefore, to achieve a 100% duty cycle the control voltage needs to be equal to the maximum RC ramp height. This is typically internal to many analog ICs and the implementation differs in digital and is discussed later in this application note. If for now, it is assumed that the maximum ramp height is 1 V, then the duty cycle can be calculated as follows:

$$Duty = Y(s) \times PWM_{COMP}$$

$$Duty = 0.1 V \times \left(\frac{100\%}{1 V} \right)$$

$$Duty = 10\%$$


This is then used as an input to the plant block, which contains the power stage and thus subsequently determines the output voltage and the loop is now closed. This simplified analysis helps to explain the different blocks within the closed-loop system. However, in reality, the analysis performed is a small-signal analysis to determine the s-domain transfer functions for the different blocks within the system.

The small-signal analysis aims to describe the behavior and therefore the output of the system given small changes in the input. The stability of the system can then be determined using this analysis. The modeled behavior of the system is used, through means of s-domain transfer functions, to characterize the plant and then analytically design a compensator to stabilize the control loop.

3.3 Buck plant transfer function

The derivation of the buck power stage transfer function is straightforward under voltage-mode control. The output filter inductor resonates with the output filter capacitor forming a double pole in the plant transfer function. Consider the output LC filter of the step-down converter shown in Figure 7.

Figure 7. LC output filter of the step-down converter power stage

 

The transfer function of the LC filter can be determined using Laplace and by analyzing the impedances in series and parallel.

$$Z_1 = sL$$

$$Z_2 = \frac{1}{sC} \parallel R$$

$$Z_2 = \frac{R \cdot \frac{1}{sC}}{R + \frac{1}{sC}}$$

$$Z_2 = \frac{R}{sCR + 1}$$

$$H_{LC}(s) = \frac{Z_2}{Z_1 + Z_2}$$

$$H_{LC}(s) = \frac{\frac{R}{sCR + 1}}{sL + \frac{R}{sCR + 1}}$$

$$H_{LC}(s) = \frac{R}{sL(sCR + 1) + R}$$

$$H_{LC}(s) = \frac{R}{s^2 LCR + sL + R}$$

$$H_{LC}(s) = \frac{1}{s^2 LC + s \frac{L}{R} + 1}$$

Putting this in the standard form for a second-order polynomial:

$$H_{LC}(s) = \frac{1}{\frac{s^2}{\omega_{LC}^2} + s \frac{1}{Q\omega_{LC}} + 1}$$


Therefore:

$$\omega_{LC} = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{2\zeta} = R\sqrt{\frac{C}{L}}$$

From this analysis, it can be seen that the double pole has an undamped natural frequency, ω_n , and a resonant peak depending on the Q . The typical Bode plot of this double pole output filter is shown in Figure 8.

Figure 8. Bode plot of the LC filter transfer function

 

In the Bode plot shown in Figure 8, the low-frequency gain is 0 dB. This is because the LC filter has no effect at low frequencies. However, in reality, there is some low-frequency gain introduced by the PWM block. As discussed earlier, the gain of this depends upon the height of the RC ramp in analog, in digital the implementation of the PWM gain differs as there is no RC ramp or analog comparator. The effect of the PWM block is that the low-frequency gain is shifted up by some amount. The amount by which the Bode plot is shifted can be calculated as follows:

$$G_{PWM} = \frac{\text{output}}{\text{input}}$$

$$G_{PWM} = \frac{V_{OUT(MAX)}}{V_{RAMP(MAX)}}$$


This equation is valid at other ramp heights provided that the corresponding duty cycle and output voltage are calculated. For example:

$$G_{PWM} = \frac{V_{OUT(@50\% \text{ duty})}}{V_{RAMP(@50\% \text{ duty})}}$$

3.4 Capacitor ESR zero

The model discussed so far does not include the parasitic elements of the output filter capacitor. The parasitic elements of the capacitor are shown in Figure 9.


Figure 9. Ideal capacitor and capacitor with parasitic elements

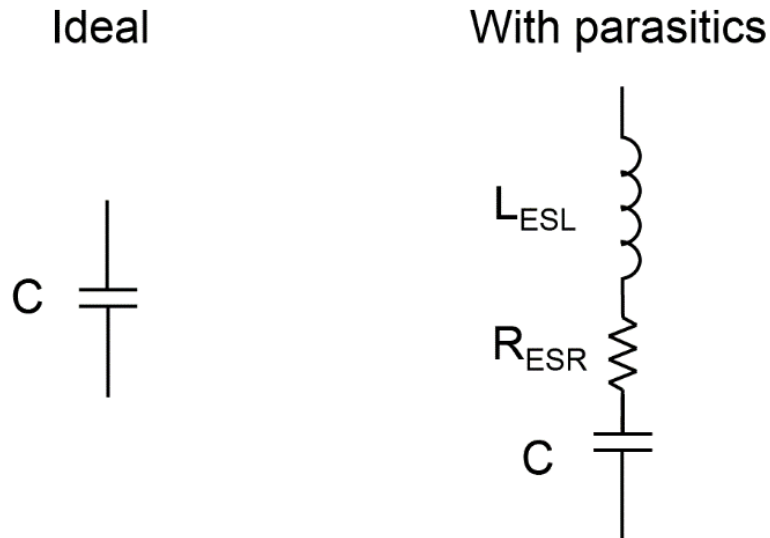

The parasitic equivalent series resistance (ESR) has a significant impact on the plant transfer function for the step-down converter. The parasitic equivalent series inductance of the capacitor is usually only dominant at much higher frequencies and therefore it can be ignored in this transfer function.

Likewise, the inductor has parasitic elements as shown in Figure 10. Typically, only the DC resistance (DCR) of the inductor winding is considered as the interwinding capacitance is only an issue at high frequencies, which are above that of the control loop.

Figure 10. Ideal inductor and inductor with parasitic elements

 

The effect of the capacitor ESR is that the zero is formed in the power stage transfer function. The zero is shown in the numerator of the plant transfer function in (2).

$$H_p(s) = \frac{1 + \frac{s}{\omega_{ESR}}}{\frac{s^2}{\omega_{LC}^2} + s \frac{1}{Q\omega_{LC}} + 1} \quad (2)$$

The location of the zero is given in (3) and is dependent on the capacitance and the ESR value.

$$\omega_{ESR} = \frac{1}{C \cdot R_{ESR}} \quad (3)$$

The addition of the capacitor ESR and inductor DCR also affects the damping of the double pole and the natural frequency. The updated equation for the Q and natural frequency of the double pole is given in (4) and (5).


$$\omega_{LC} = \frac{1}{\sqrt{LC\left(1 + \frac{R_{ESR}}{R}\right)}} \quad (4)$$

$$Q = \frac{1}{\omega_{LC}\left(\frac{L}{R} + C\left(R_{ESR} + \left(1 + \frac{R_{ESR}}{R}\right)R_{DCR}\right)\right)} \quad (5)$$

4 Voltage mode compensator design

4.1 Loop stability criteria

Figure 11. Closed and open-loop transfer functions

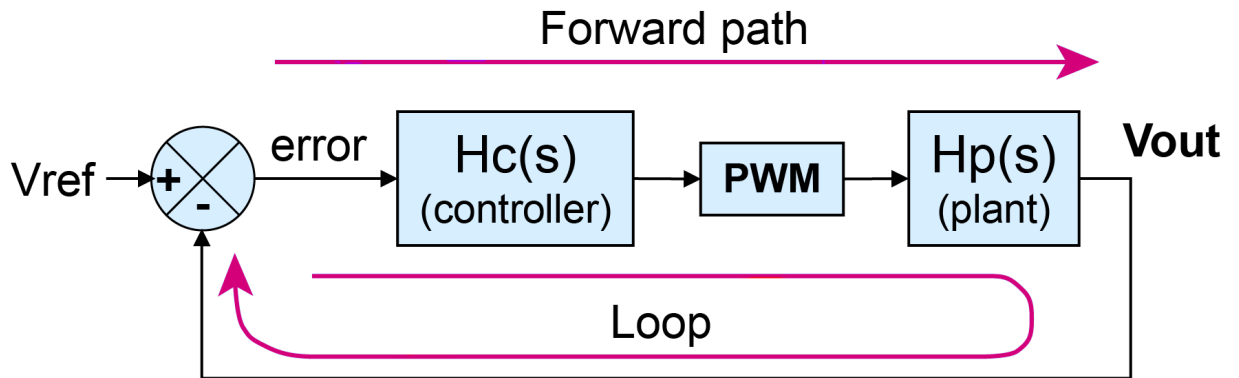


Consider the control loop of the step-down converter shown in Figure 11, where the forward and loop paths of the control loop are identified. The transfer function for the closed-loop system is given in (6).

$$TF = \frac{Forward}{1 - Loop} \quad (6)$$

The closed-loop transfer function can be derived by applying this to Figure 11:

$$H_{CL}(S) = \frac{Forward}{1 - (-Loop)} = \frac{H_c(S) \cdot G_{PWM} \cdot H_p(S)}{1 + H_c(S) \cdot G_{PWM} \cdot H_p(S)} \quad (7)$$

The loop response, also called the open-loop, is the controller transfer function $H_c(s)$ combined with the plant or power stage transfer function $H_p(s)$ and also includes the modulator gain – the PWM block. The Bode plot of a typical loop response is shown in Figure 12.

 Figure 12. Open-loop Bode plot of the step-down converter: plant, PWM, and compensator


Several terms can be defined from this Bode plot. The first is the crossover frequency at which the gain plot crosses the 0 dB axis. If the gain plot is falling at a rate of 20 dB/decade around the crossover frequency, then below the crossover frequency, which means at a lower frequency going left on the frequency X-axis, the gain plot has a positive gain. It means that it has a gain greater than 1.

At the crossover frequency, the value of the phase in the open loop determines the stability of the closed-loop system. If the phase is -180° or less with a gain greater than or equal to 1, then the closed-loop system becomes unstable. This can be seen from the denominator of (7).

Therefore, to ensure stability, the phase of the open loop system must be greater than -180° at the crossover frequency. This term is defined as the phase margin and is the amount by which the phase is above the -180° at the crossover frequency. Typically, the compensator is designed such that the phase margin is 45° or more at the crossover frequency. A phase margin of 45° equates to a loop phase of -135° . Therefore, the loop phase is 45° above the -180° point of instability. The phase margin is shown as 64° in Figure 12.

4.2 Crossover and phase margin specification

The choice of crossover frequency and phase margin determines how well the converter responds to line and load transients. Typically, the higher the crossover frequency is the faster the response and recovery in the time domain. However, certain limitations prevent the choice of a crossover frequency that is too high. In a standard analog voltage-mode controlled buck, the plant phase rolls off due to the double pole. The capacitor ESR zero adds phase to the loop however it cannot be relied upon to achieve stability. Furthermore, the op-amp internal to analog control ICs introduces a phase roll-off as the frequency approaches the bandwidth.


With a digital compensator, there is no analog op-amp bandwidth to consider. However, the delays within the digital system introduce a phase loss. As the frequencies approach the sampling frequency this phase loss becomes significant. A method for calculating the anticipated phase loss is covered later in this application note. Therefore, a recommended starting point for the crossover frequency is between 1/10th and 1/20th of the sampling frequency. This is assuming that the sampling frequency is the same as the switching frequency.

Crossover specification: 1/10th to 1/20th of the sampling/switching frequency

As discussed earlier, the phase margin is an indicator of the stability of the system. With 0° of phase margin, the system becomes unstable. For $<30^\circ$ of phase margin, the system likely has multiple oscillations in the time domain when subjected to the line and load transients. For 45° of phase margin, the system likely has one ring in the time domain after recovery from a transient. Therefore, 45° of phase margin is typically the minimum allowable.

Conversely, a larger phase margin may result in a slower response to line and load transients. For example, a phase margin of 60° may result in zero overshoot, no ringing, and a slower recovery. Therefore, there must be a balance between the choice of crossover frequency and the amount of phase margin that the combined system has. In Figure 13 the step response for a system with decreasing crossover frequency and phase margin is shown (from grey to green). The response becomes slower and more oscillatory as the crossover and phase margin are both decreased.

Figure 13. Step response for a system with decreasing crossover and phase margin (grey to green)

 


Phase margin specification: a minimum of 45° of phase margin at the crossover frequency, ideally between 50° and 60°

4.3 Types of compensators

A compensator needs to be designed and added into the loop. The aim is to shape the loop response to meet the desired crossover frequency and phase margin specifications. In the analog domain, a compensator usually consists of an inverting op-amp with a compensation network of capacitors and resistors around the negative feedback path. The combinations of capacitors and resistors determine the location of the poles and zeros of the compensator.

There are typically two types of compensators that are used for stabilizing power supplies. These are universally referred to as the Type-II and Type-III compensators. For voltage mode control, the Type-III compensator is required. This is because Type-II does not provide enough zeros to compensate for the phase lag. It is due to the double pole of the voltage mode buck plant transfer function. The circuit for a Type-III compensator is shown in Figure 14.

Figure 14. Type-III compensator implemented in analog using op-amp

 

The transfer function for this circuit can be derived in the same manner as that of the buck power stage. For brevity, the full transfer function is included without derivation in (8).

$$H_C(s) = \left(\frac{\omega_{CP0}}{s}\right) \frac{\left(\frac{s}{\omega_{CZ1}} + 1\right) \left(\frac{s}{\omega_{CZ2}} + 1\right)}{\left(\frac{s}{\omega_{CP1}} + 1\right) \left(\frac{s}{\omega_{CP2}} + 1\right)} \quad (8)$$

The transfer function in (8) has two zeros, two poles, and a pole at the origin. The locations of these zeros and poles are determined by the capacitors and resistors in the compensation network according to (9) through (13).

$$\omega_{CZ1} = \frac{1}{R_2 C_1} \quad (9)$$

$$\omega_{CZ2} = \frac{1}{C_2 (R_1 + R_3)} \quad (10)$$

$$\omega_{CP0} = \frac{1}{R_1 (C_1 + C_3)} \quad (11)$$

$$\omega_{CP1} = \frac{(C_1 + C_3)}{R_2 C_1 C_3} \quad (12)$$

$$\omega_{CP2} = \frac{1}{R_3 C_2} \quad (13)$$

In digital, this compensator is implemented on the MCU. The translation from analog to digital is discussed in the next section.

4.4 Compensator pole/zero placement

The locations of the poles and zeros of the compensator need to be selected such that, when the compensator is combined with the plant power stage, the open-loop frequency response meets the stability criteria of:

- Desired crossover frequency
- Desired phase margin at the crossover
- A shallow slope of -20 dB/decade around the crossover

Several different methods can be applied to achieve this. In this application note, the straightforward and intuitive method of pole/zero cancellation is applied. Consider the plant transfer function discussed earlier:

- The plant has a double pole due to the resonance between the output filter inductor and capacitor.
- The plant has a single zero due to the ESR of the output filter capacitor.
- The plant has a DC gain.

The effects of the plant double pole can be partially canceled out by placing the two compensator zeros at the natural frequency of the double pole. It is of course not possible to completely cancel out the complex conjugate double pole of the plant with two real zeros in the compensator, however, it lessens the effect of the double pole and provide 180° of phase boost at around one decade above this frequency:

$$\{\omega_{CZ1}, \omega_{CZ2}\} = \omega_n = \frac{1}{\sqrt{LC}} \quad (14)$$

Now that the two zeros of the compensator are placed, the two poles of the compensator and the pole at the origin remain. One of the compensator's poles can be used to cancel out the parasitic ESR zero of the power stage. This effectively eliminates the gain and phase contribution from the parasitic ESR zero. However, this is reliant on the accurate determination of the actual ESR value for the capacitor or capacitors used.

$$\omega_{CP1} = \omega_{ESR} = \frac{1}{C \cdot R_{ESR}} \quad (15)$$

The second compensator pole can be placed at half the switching frequency and in doing so the high-frequency gain is attenuated while not having a significant impact on the phase at around the crossover frequency.

$$\omega_{CP2} = \pi F_s \quad (16)$$

The final term of the compensator to calculate is the pole at the origin. As the name implies, this compensator pole is at the origin, and therefore setting the position of the pole at the origin is changing the gain and not moving the pole. This can be used to adjust the crossover frequency of the loop. Adding the pole at the origin to the compensator introduces the constant -20 dB/decade gain roll-off which is desirable around the crossover frequency. The pole at the origin also provides very high low-frequency gain which removes steady-state errors and rejections and low-frequency perturbations of the control loop.

The gain contributions from all of the other poles and zeros in the system must be taken into account to determine the exact gain required by the compensator to achieve the desired crossover frequency. The equality in (17) must be solved for the compensator pole at the origin:

$$20 \log_{10}|H_P(j\omega)| + 20 \log_{10}|H_C(j\omega)| = 0 \text{ dB} \quad (17)$$

Given that the plant transfer function and compensator transfer functions are both known, this can be solved for the unknown term ω_{CP0} with the result shown in (18). Evaluating this equation determines the amount of gain which needs to be added by the compensator to achieve the specified crossover frequency.

$$\omega_{CP0} = \frac{\omega_X}{\frac{V_{IN}}{V_{RAMP}} \times \frac{\sqrt{1 + \left(\frac{\omega_X}{\omega_{ESR}}\right)^2}}{\sqrt{\left(\frac{\omega_X}{\omega_{LC} \times Q}\right)^2 + \left(1 + \frac{-\omega_X^2}{\omega_{LC}^2}\right)^2}} \times \frac{\sqrt{1 + \left(\frac{\omega_X}{\omega_{CZ1}}\right)^2} \times \sqrt{1 + \left(\frac{\omega_X}{\omega_{CZ2}}\right)^2}}{\sqrt{1 + \left(\frac{\omega_X}{\omega_{CP1}}\right)^2} \times \sqrt{1 + \left(\frac{\omega_X}{\omega_{CP2}}\right)^2}}} \quad (18)$$

The method discussed so far gives the user control over the crossover frequency but not the phase margin.

Typically, it may result in a large phase margin, however, in a digital system, the phase loss due to the digitization delays may result in a significant amount of phase margin erosion. Therefore, it is possible to derive an equation that analytically calculates the precise location of one of the compensator zeros to achieve the specified phase margin. This is achieved by solving the equality shown in (19) for the compensator zero ω_{CZ1} .

$$\angle(H_P(j\omega) \cdot H_C(j\omega)) = -\pi + \theta_M \quad (19)$$

(19) states that the phase of the plant combined with the compensator must be equal to -180° plus the desired phase margin at the crossover frequency. Again, with some trigonometry, this equality can be solved for ω_{CZ1} and the result is given in (20).

$$\omega_{CZ1} = \frac{\omega_X}{\tan\left(-\frac{\pi}{2} + \Phi_M - \tan^{-1}\frac{\omega_X}{\omega_{PP1}} - \tan^{-1}\frac{\omega_X}{\omega_{PP2}} + \tan^{-1}\frac{\omega_X}{\omega_{CP2}} - \tan^{-1}\frac{\omega_X}{\omega_{CZ2}}\right)} \quad (20)$$

Where ω_{PP1} and ω_{PP2} are the complex conjugate poles of the double pole formed by the inductor and capacitor in the plant.

This equation requires the calculation of the inverse tangent of complex numbers necessitating the use of a mathematical package to evaluate. For this application note, the software tool Biricha ST-WDS is used to perform the calculations and is available for download free of charge from the Biricha website www.biricha.com/st-wds. This tool is discussed in detail through means of a complete design example later in this application note.

5 Discrete-time controller

5.1 Bi-linear transform


With the poles and zeros of the compensator placed in the continuous-time domain, the s-domain, they must be converted into the discrete-time domain to implement the controller on the MCU. To implement the discrete-time controller, the continuous-time Type III compensator, which is discussed in the previous section, is converted into its discrete-time equivalent.

There is a direct mapping between the continuous-time domain, the s-domain, and the discrete-time domain, the z-domain. The relationship is shown in (21).

$$z = e^{sT} \quad (21)$$

Several different methods can be used to convert an s-domain transfer function in the discrete-time z-domain. A commonly used method is the bilinear transform (also called the Tustin or trapezoidal transform). This transform approximates the continuous-time signal based on a trapezoid from k to $k+1$. An example of this is shown in Figure 15.


Figure 15. Continuous-time signal sampled in discrete time using a trapezoidal approximation

 

This trapezoidal approximation gives rise to the transform given in (22).

$$s \leftarrow \frac{2}{T_s} \frac{1-z^{-1}}{1+z^{-1}} \quad (22)$$

This transform has the advantage that a system with stable poles and zeros, which means a left-half plane, transforms into a system with stable z-domain poles and zeros. The stable region in the z-domain is the area on or inside the unit circle. Therefore, the mapping is shown in Figure 16.

 Figure 16. Trapezoidal approximation mapping from s to z-domain


There is inevitably some distortion with the mapping given that the entirety of the left-half s-plane is mapped to the unit circle in the z-domain. However, this distortion is only significant as the frequency approaches the sampling frequency. For this power supply application, most of the compensator poles and zeros are significantly below the sampling frequency. Furthermore, the crossover frequency is specified between 1/10th and 1/20th of the sampling frequency and there is no significant distortion from the mapping around this frequency.

However, this transform does not include the effects of the pure time delays in the discrete-time system and there is an additional phase roll-off that is not considered here. This manifests itself as a phase erosion at the crossover frequency and this must be taken into account when the compensator is being designed.

5.2 3p3z controller

The bilinear transform is applied to the s-domain Type-III compensator by replacing every instance of s in the s-domain transfer function with the bilinear mapping. The initial substitution is given in (23) and the simplified result is given in (24).

$$H_C[z] = \left(\frac{\omega_{CP0}}{\frac{2}{T_S} \frac{1-z^{-1}}{1+z^{-1}}} \right) \left(\frac{\frac{2}{T_S} \frac{1-z^{-1}}{1+z^{-1}}}{\omega_{CZ1}} + 1 \right) \left(\frac{\frac{2}{T_S} \frac{1-z^{-1}}{1+z^{-1}}}{\omega_{CZ2}} + 1 \right) \quad (23)$$

$$H_C[z] = \frac{B_3 z^{-3} + B_2 z^{-2} + B_1 z^{-1} + B_0}{-A_3 z^{-3} - A_2 z^{-2} - A_1 z^{-1} + 1} \quad (24)$$

In the discrete-time z-domain, the transfer function now has three z-domain poles and three z-domain zeros. Therefore, this controller is now referred to as a three-pole three-zero controller or 3p3z for short.

The numerator of the transfer function is grouped into like terms consisting of 'B' coefficients and likewise, the denominator is grouped into like terms consisting of 'A' coefficients. These coefficients are given in (25) to (31).

$$B_3 = \frac{T_S \times \omega_{CP0} \times \omega_{CP1} \times \omega_{CP2} \times (-2 + T_S \times \omega_{CZ1}) \times (-2 + T_S \times \omega_{CZ2})}{(2 \times (2 + T_S \times \omega_{CP1}) \times (2 + T_S \times \omega_{CP2}) \times \omega_{CZ1} \times \omega_{CZ2})} \quad (25)$$

$$B_2 = \frac{T_S \times \omega_{CP0} \times \omega_{CP1} \times \omega_{CP2} \times (-4 + 3T_S^2 \times \omega_{CZ1} \times \omega_{CZ2} - 2T_S \times (\omega_{CZ1} + \omega_{CZ2}))}{(2 \times (2 + T_S \times \omega_{CP1}) \times (2 + T_S \times \omega_{CP2}) \times \omega_{CZ1} \times \omega_{CZ2})} \quad (26)$$

$$B_1 = \frac{T_S \times \omega_{CP0} \times \omega_{CP1} \times \omega_{CP2} \times (-4 + 3T_S^2 \times \omega_{CZ1} \times \omega_{CZ2} + 2T_S \times (\omega_{CZ1} + \omega_{CZ2}))}{(2 \times (2 + T_S \times \omega_{CP1}) \times (2 + T_S \times \omega_{CP2}) \times \omega_{CZ1} \times \omega_{CZ2})} \quad (27)$$

$$B_0 = \frac{T_S \times \omega_{CP0} \times \omega_{CP1} \times \omega_{CP2} \times (2 + T_S \times \omega_{CZ1}) \times (2 + T_S \times \omega_{CZ2})}{(2 \times (2 + T_S \times \omega_{CP1}) \times (2 + T_S \times \omega_{CP2}) \times \omega_{CZ1} \times \omega_{CZ2})} \quad (28)$$

$$A_3 = \frac{(-2 + T_S \times \omega_{CP1}) \times (-2 + T_S \times \omega_{CP2})}{(2 + T_S \times \omega_{CP1}) \times (2 + T_S \times \omega_{CP2})} \quad (29)$$

$$A_2 = \frac{(12 - T_S^2 \times \omega_{CP1} \times \omega_{CP2} - 2 \times T_S \times (\omega_{CP1} + \omega_{CP2}))}{(2 + T_S \times \omega_{CP1}) \times (2 + T_S \times \omega_{CP2})} \quad (30)$$

$$A_1 = \frac{(-12 + T_S^2 \times \omega_{CP1} \times \omega_{CP2} - 2 \times T_S \times (\omega_{CP1} + \omega_{CP2}))}{(2 + T_S \times \omega_{CP1}) \times (2 + T_S \times \omega_{CP2})} \quad (31)$$


There is no need to calculate these controller coefficients by hand as the software tool Biricha ST-WDS available from www.biricha.com/st-wds performs these calculations.

Finally, now that the controller is in the discrete-time 3p3z form, it can be converted into a linear differential equation, which can be easily implemented on the MCU. This takes advantage of the shifting property of the z-domain transfer function and converts from a z-domain to a discrete sample (32).

$$y[n] = A_1 y[n-1] + A_2 y[n-2] + A_3 y[n-3] + B_0 x[n] + B_1 x[n-1] + B_2 x[n-2] + B_3 x[n-3] \quad (32)$$

Where $y[n]$ is the output for the current sampling interval. The structure of this controller is depicted in Figure 17.

Figure 17. 3p3z controller structure

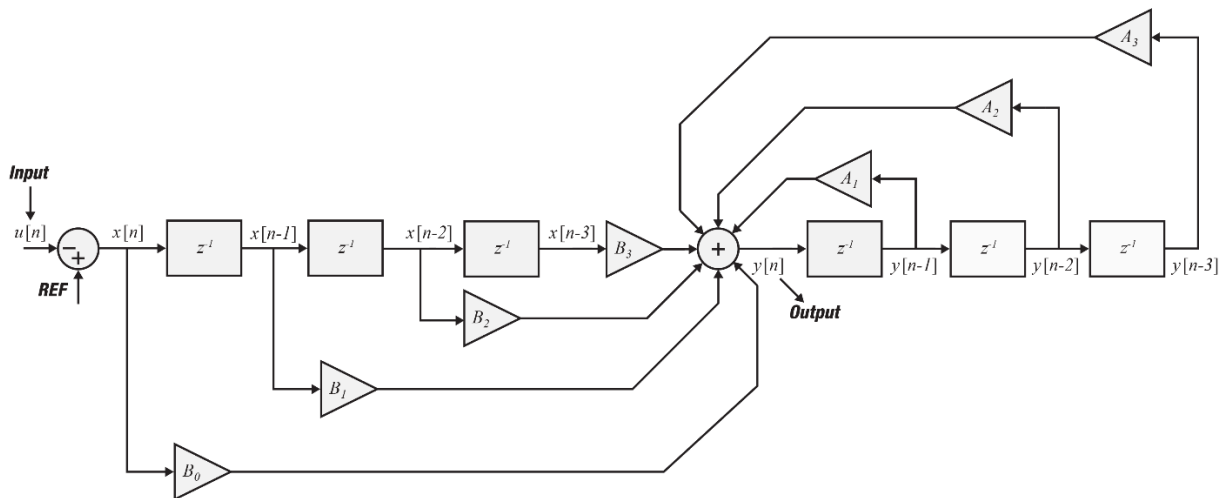


For this voltage mode step-down converter, the current output of the controller may be the new value of the duty cycle that is used in the following switching period. Therefore, there is now an equation that can implement the analytically designed controller and is calculated by the MCU at every sampling interval when there is a new sample available.

5.3 Pure time delays

In this discrete-time digital system, there are additional time delays that are not present in the equivalent analog continuous-time system. A pure time delay in the discrete-time system results in a phase delay that is proportional to the frequency and time delay.

There are two sources of time delay in the digital system. The first is the time from which the output voltage sample is taken, to the time at which it is used. This is referred to as the calculation delay. In effect the older the sample the more phase delay is associated with the sample. As an ideal example, a convenient time to trigger the ADC and sample the output voltage may be at the beginning of the switching period. In this case, the output voltage is sampled, converted, and used in the controller to provide the new value of the duty cycle. This sampling and calculation time may take several hundred nanoseconds and the new value of the duty cycle is ready to use towards the end of that switching period. This situation is described in Figure 18.

Figure 18. Sources of delay within the discrete-time system

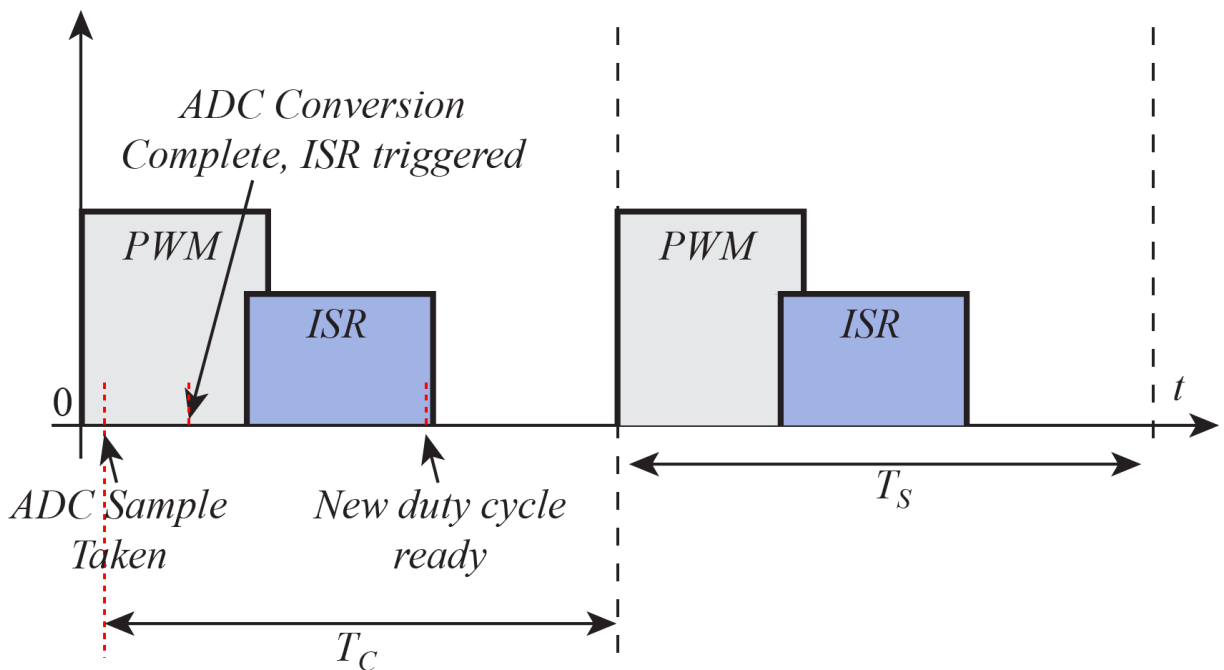

However, as the new duty cycle is not used until the following switching cycle, the total time delay for this calculation time is considered to be one complete switching period. Of course, if the user can delay the trigger for the ADC until later in the switching period then it is possible to reduce this time delay.

The second contribution to the time delay is that of the zero-order-hold (ZOH) introduced by this sampled data system. The ADC is triggered once per switching cycle, this sampled data is used to calculate the new value of the duty cycle, and that duty cycle is held constant for the remainder of the next switching period. Therefore, there is one zero-order hold in this system. The frequency response of a ZOH is given in (33).


$$F_{ZOH}(j\omega) = \frac{1 - e^{-j\omega T_S}}{j\omega} \quad (33)$$

This can be shown to be a complex number expressed in polar form, and therefore the phase angle is given in (34).

$$\angle F_{ZOH}(j\omega) = -\omega \frac{T_S}{2} \quad (34)$$

To understand how this phase angle can relate to a time delay, consider as an example the 1-Hz sine wave shown in Figure 19. If this sine wave is delayed by 0.5 s, the result is the sine wave shown as a dashed line in Figure 19.

Figure 19. Time delay relationship to phase delay

 

It is clear from this that the time-delayed sine wave now has a phase delay of 180° . Therefore, the equation to calculate the phase delay of a sine wave given the pure time delay T_D is given in (35).

$$p.d. = -2\pi f T_D \quad (35)$$

This indicates that there is some phase delay across all frequencies, however, when $T_D \ll 1/f$ the phase delay is negligible. This is true for very low frequencies assuming that the phase delays in the digital system can be kept to a minimum.

The frequency at which this phase delay may become a concern is the crossover frequency of the open-loop system as this is where the phase margin is defined. Earlier in this application note, it is specified that the phase margin has a minimum value of 45° to ensure a transient response that is not oscillatory in the time domain. Therefore, the amount of phase loss at the crossover frequency can be calculated given the known time delays in the digital system.


$$p.e. = -2\pi f_c T_D \quad (36)$$

The expected phase erosion at the crossover frequency can be added to the desired phase margin such that this phase loss is compensated for at design time. This can be achieved by adding the expected phase erosion to the phase margin specified in (36). This adjusts the location of the compensator zero to add the required phase boost and compensate for this phase loss such that the resulting overall phase margin meets the specification.

5.4 Digital gains

The output of the 3p3z controller in Figure 20 is scaled by a factor, K. This scaling factor is responsible for negating all of the additional gains introduced by the digital system. The compensator poles and zeros are analytically calculated to achieve the specified crossover frequency and phase margin. If the additional gains within the digital system are not accounted for then the overall loop gain, and thus the phase margin, is incorrect.

Figure 20. Additional gains within the digital system

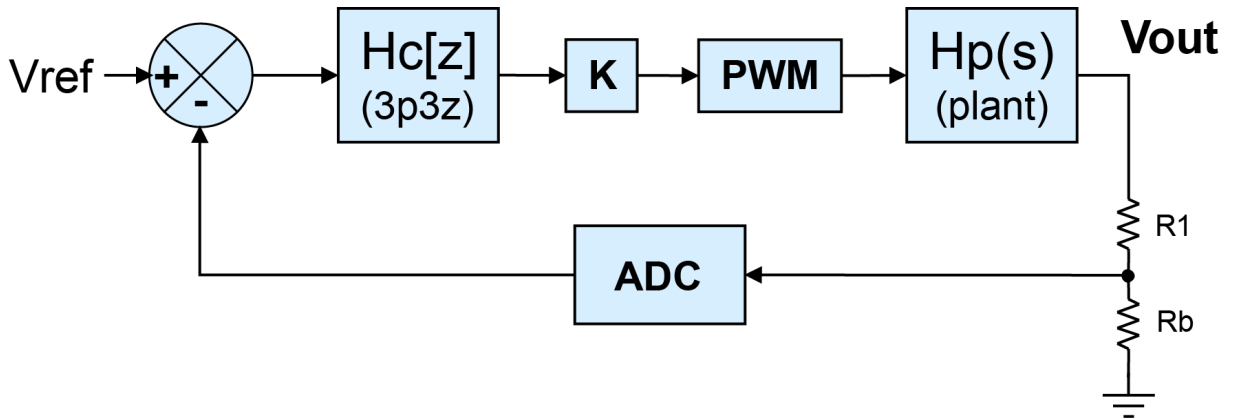

Consider the block diagram of the digital control loop shown in Figure 20. The output voltage V_{out} needs to be scaled down to a voltage suitable for sampling by the ADC onboard the MCU. This is the purpose of the potential divider formed by R1 and Rb. This also determines the setpoint value that the controller must regulate. The gain of the pre-ADC scaling potential divider can be calculated in (37).

$$G_{PD} = \frac{R_b}{R_1 + R_b} \quad (37)$$

Then the ADC onboard the MCU converts the voltage, which is between 0 and 3.3 V, and provides a 12-bit output, meaning a number between 0 and 4095. Therefore, the gain of the ADC can be calculated using (38).

$$G_{ADC} = \frac{2^{12} - 1}{3.3V} \quad (38)$$

The output of the controller is used to update the duty cycle register and therefore this must be in the correct scaling. The PWM is implemented using the HRTIM module onboard the MCU and the timer-compare register is used to control the effective duty cycle. The HRTIM module outputs a duty cycle of 100% when the timer-compare register is set to the period value. Therefore, the gain of the PWM module can be calculated using (39). This is similar to the RC ramp and analog comparator gain seen earlier in the analog voltage-mode example.

$$G_{PWM} = \frac{100\%}{period} \quad (39)$$

To achieve the correct loop gain, the controller must negate these additional gains. That is achieved using the scaling factor K, which can be calculated in (40).

$$K = \frac{1}{G_{PD}G_{ADC}G_{PWM}} \quad (40)$$

Finally, the ADC output is compared with the digital reference set point. This digital reference must be in the same scaling as the ADC output and account for the voltage divider on the input of the ADC. Therefore, the reference can be calculated using (41).

$$V_{REF} = V_{OUT}G_{PD}G_{ADC} \quad (41)$$

6 Software implementation

6.1 Targeted application

The following configuration sets up the STM32 MCU to operate a closed-loop voltage mode step-down converter using the onboard peripherals including the ADC, DMA, and HRTIM. The FMAC is used to implement the 3p3z controller. This implementation means that the main core usage is reduced to an absolute minimum and is the preferred option allowing the MCU to be used for other tasks, or running more power supplies. The example software project to accompany this application note is called `Buck_VoltageMode_HW` as it uses as many hardware peripherals as possible. However, it is possible to use the main core to implement the 3p3z controller instead of the FMAC. In this case, the configuration is different from that discussed below and an example of this is provided in the project titled `Buck_VoltageMode_SW`.

6.2 Configuration using STM32CubeMX

The following section contains step-by-step instructions for recreating the STM32CubeMX project for the step-down converter under voltage mode control on the Discovery kit. This complete project can be downloaded by following the links provided within this application note appendix. However, the full configuration is included here for completeness.

Open STM32CubeMX by clicking on the icon shown in Figure 21 (note that the icon may differ slightly).


Figure 21. STM32CubeMX icon



Now, create a new STM32CubeMX project. This project configures the MCU peripherals and also generates an IAR Embedded Workbench® project. IAR Systems® is used to compile and link the code as well as for programming and debugging the MCU.


Within the STM32CubeMX window click on `File, New Project`.

Figure 22. New project selection

 

The new project device selector window now opens. Within this window click on the `Board selector` tab and filter down the boards by selecting the `Discovery kit` for the `Type` and `STM32G4` for the `MCU/MPU Series`.


Figure 23. Board selection

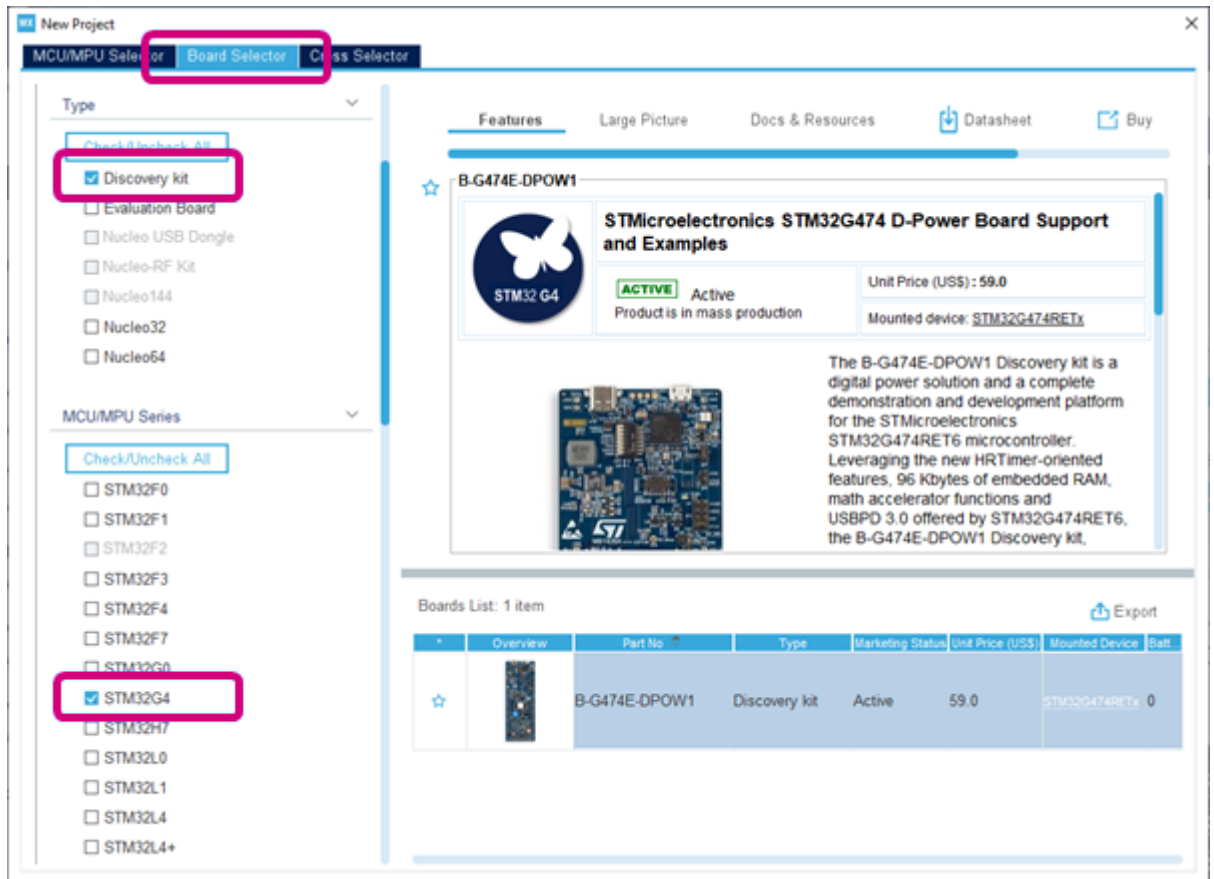

This may filter down the available boards on the right-hand side of this window to include the `B-G474E-DPOW1` Discovery kit, which this application note is using. Double-click on this board within the table.


A prompt is displayed asking if the user likes to initialize all peripherals with their default mode. Click `Yes`. This sets up the pins and peripherals with their default setting for this particular evaluation board.

Figure 24. Peripherals default mode initialization

 


Before making any changes to the project, save the project by going to File, Save Project As...

Figure 25. Project naming

 

The name given to the folder, Folder Name, is also the name of the project. If this folder does not exist it is created. Click Save when done.

Figure 26. Project saving

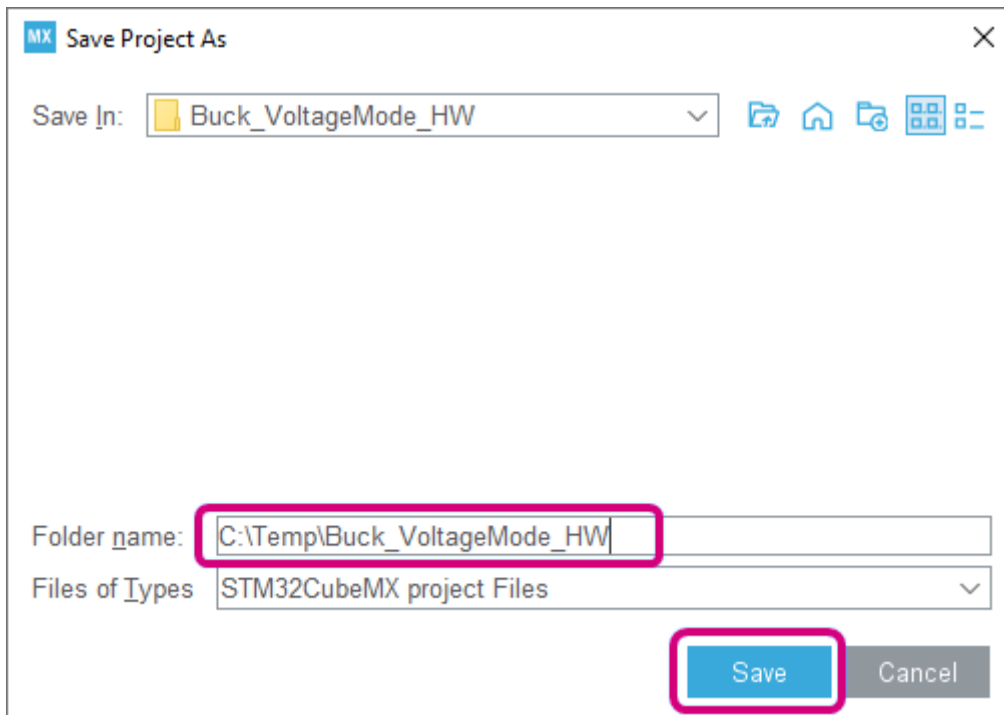

On the right-hand side of the main window, click `Project Manager` and select the preferred toolchain and version from the dropdown list as shown in [Figure 27](#).

Figure 27. Project manager configuration


The screenshot displays the Project Manager configuration interface. The breadcrumb navigation at the top indicates the path: Home > STM32G474RETx - NUCLEO-G474RE > Buck_VoltageMode_HW.ioc - Project Manager > GENERATE. The interface is divided into four main sections: Project, Code Generator, Advanced Settings, and Mcu and Firmware Package. The 'Code Generator' section is currently active and contains the following settings:

- Project Settings:**
 - Project Name: Buck_VoltageMode_HW
 - Project Location: C:\Temp\B-G474E-DPOW1\Examples
 - Application Structure: Basic (dropdown), with an unchecked checkbox for "Do not generate the main()".
 - Toolchain Folder Location: C:\Temp\B-G474E-DPOW1\Examples\Buck_VoltageMode_HW\
 - Toolchain / IDE: EWARM (dropdown)
 - Min Version: V8.32 (dropdown)
 - Generate Under Root: unchecked checkbox
- Linker Settings:**
 - Minimum Heap Size: 0x200
 - Minimum Stack Size: 0x400
- Mcu and Firmware Package:**
 - Mcu Reference: STM32G474RETx
 - Firmware Package Name and Version: STM32Cube FW_G4 V1.1.0
 - Use Default Firmware Location: checked checkbox

6.2.1 Clock configuration

Select the **Clock Configuration** tab, which is along the top of the main STM32CubeMX window. Locate the PLL section and change the peripheral clock divider to $/6$. Then select the clock source for the ADC12 clock MUX to PLLP. These settings are highlighted in Figure 28.

Figure 28. Clock configuration window

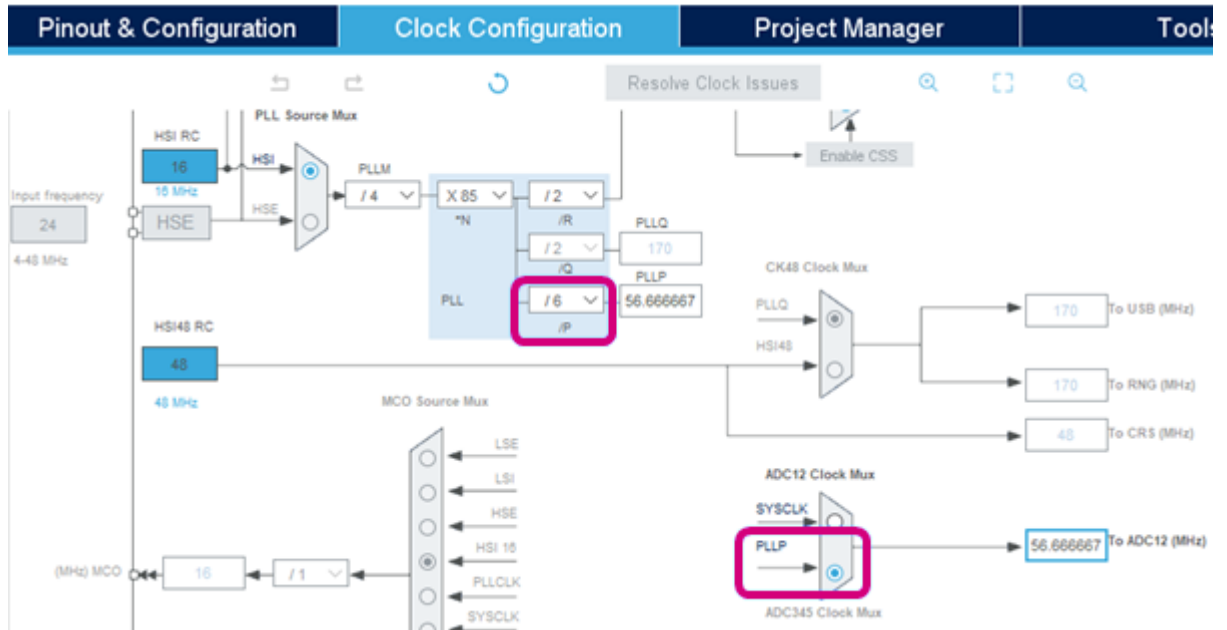


The ADC12 clock may now be 56.66 MHz.

6.2.2 GPIO peripheral configuration

For this application note, a digital pin is configured to allow timing measurements to be performed. On the `Pinout & Configuration` tab, locate the pin PB9 towards the top left of the microcontroller. Left-click on the pin PB9 and select `GPIO_Output` as in Figure 29.


Figure 29. GPIO peripheral configuration window

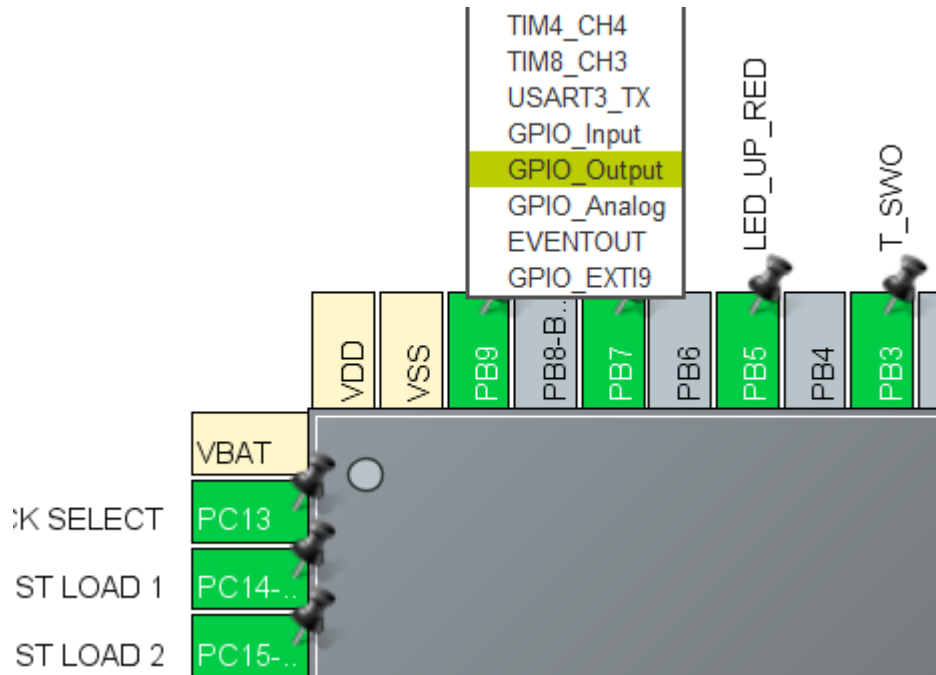

Then, right-click on PB9 and select `Enter User Label`. This allows us to change the name of the pin so that it can be easily referenced within the code. This pin is called `GPO1`.

Enter this into the pop-up box as in Figure 30.

Figure 30. GPIO renaming

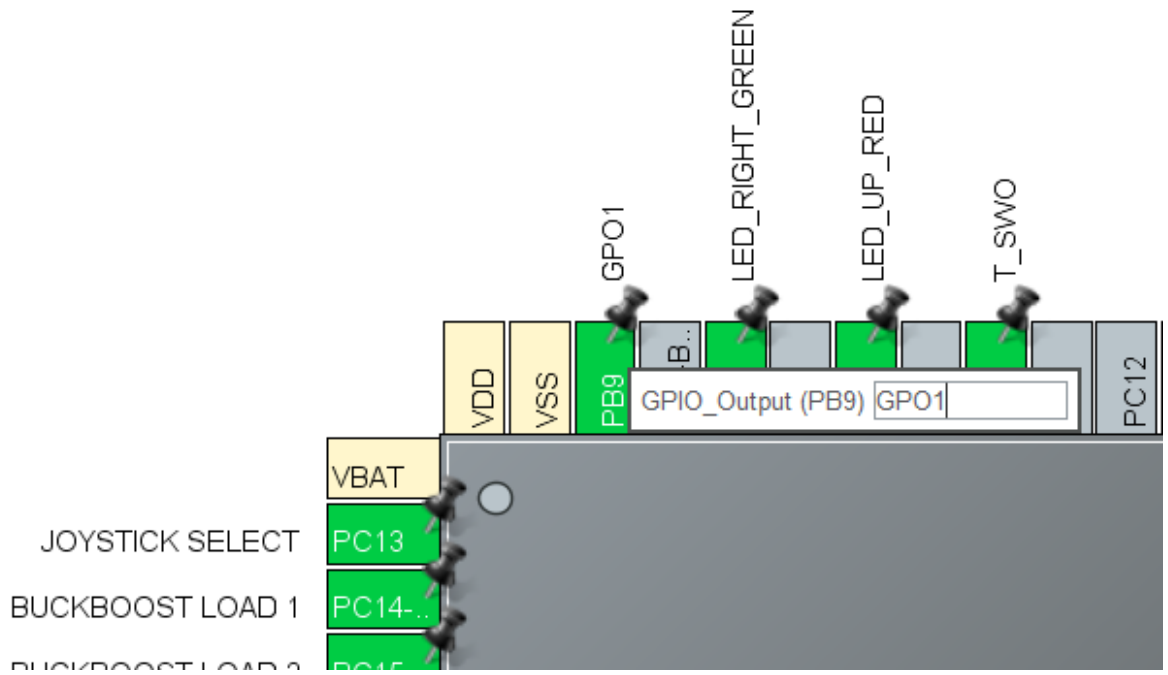

Now expand the `System Core` category on the left-hand side of the window. Click on `GPIO`. Under the `GPIO` tab, click on the row for `PB9`. Change the `Maximum output speed` setting to `Very high` as per the image below.

Figure 31. GPIO maximum output speed setting

The screenshot shows the IDE's peripheral configuration window. At the top, several peripheral categories are listed with checkmarks: HRTIM1, OPAMP5, SYS, NVIC, GPIO, Single Mapped Signals, ADC1, and COMP6. Below this is a search bar and a checkbox for 'Show only Modified Pins'. A table lists pins, with PB9 selected. Below the table, the 'PB9 Configuration' panel is open, showing various settings for the selected pin. The 'Maximum output speed' is set to 'Very High'.

Pin	Signal	GPIO o...	GPIO ...	GPIO ...	Maxim...	Fast M...	User L...	Modified
PB9	n/a	Low	Output...	No pull...	Very H...	Disable	GPO1	<input checked="" type="checkbox"/>

PB9 Configuration :

- GPIO output level: Low
- GPIO mode: Output Push Pull
- GPIO Pull-up/Pull-down: No pull-up and no pull-down
- Maximum output speed: Very High
- Fast Mode: Disable
- User Label: GPO1

The configuration for `GPO1` is now complete.


Now, some of the default pin labels must be changed to work with the example code provided. Within the pinout view of the MCU, locate the following pins, right-click on them and select `Enter User Label` and change the label to the new label listed in the table below:

Table 1. User label setting

Pin	Existing label	New label
PB7	LD4 [Green LED]	LED_RIGHT_GREEN
PB5	LD5 [Red LED]	LED_UP_RED
PA15	LD2 [Blue LED]	LED_DOWN_BLUE
PB1	LD3 [Orange LED]	LED_LEFT_ORANGE

The pin locations are highlighted in the image below.

Figure 32. Pins location

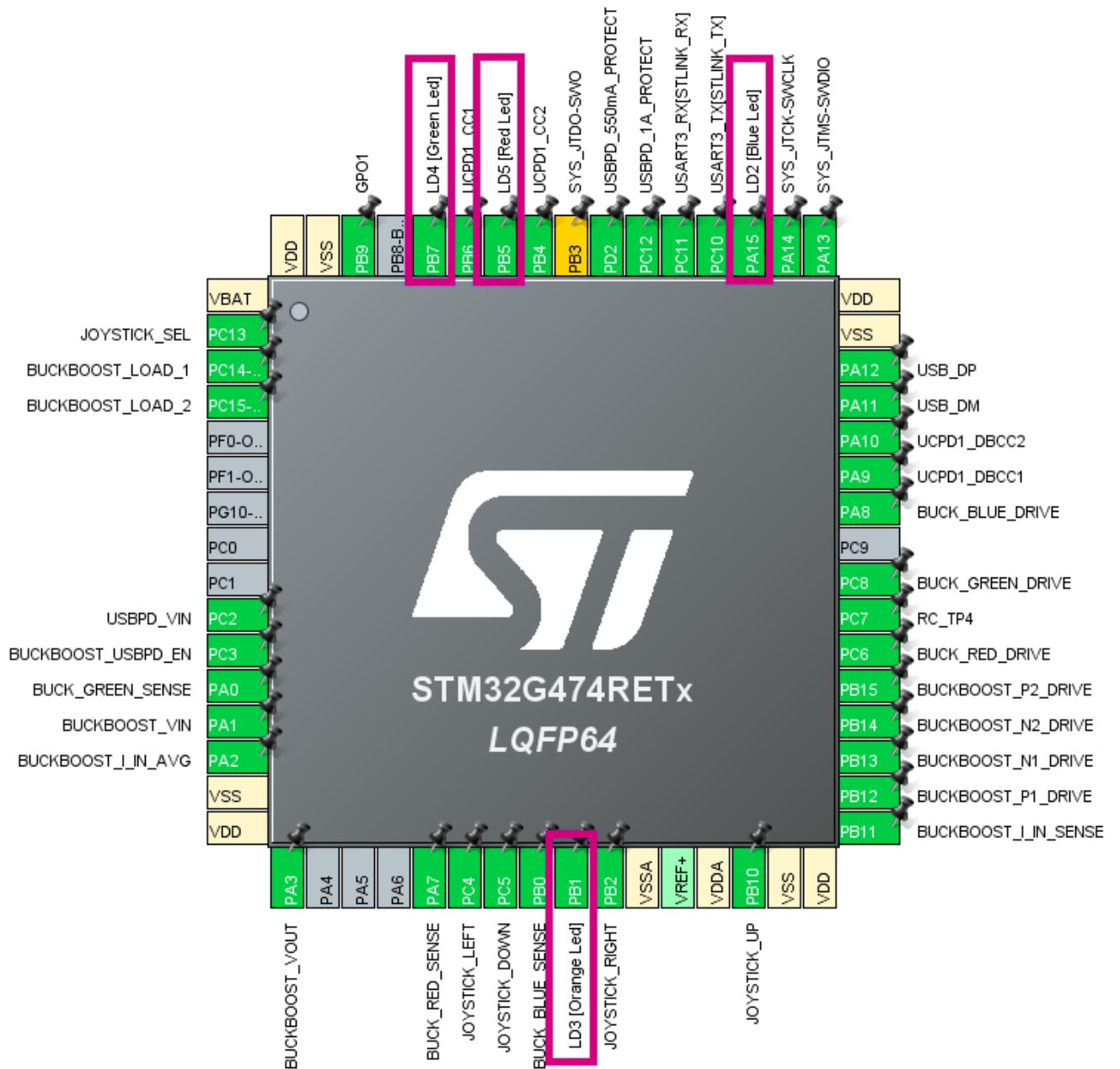


The GPIO configuration is now complete.

6.2.3 ADC peripheral configuration


The peripherals can now be configured. On the top menu select `Pinout & Configuration` and then on the left-hand pane, expand the `System Core` list and click on `DMA`. The DMA is used to copy the result from the ADC result register to the FMAC for the execution of the controller. By default, there is no DMA request configured and therefore one must be added for the ADC. On the `DMA1`, `DMA2` tab, click the `Add` button. Select `ADC1` as the `DMA Request` source. Set the `Mode` to `Circular` and untick the incremented address for memory. Change the `Data Width` to `Word` for both peripheral and memory. The configuration window may now look like the screenshot in Figure 33.

Figure 33. DMA mode and configuration screen

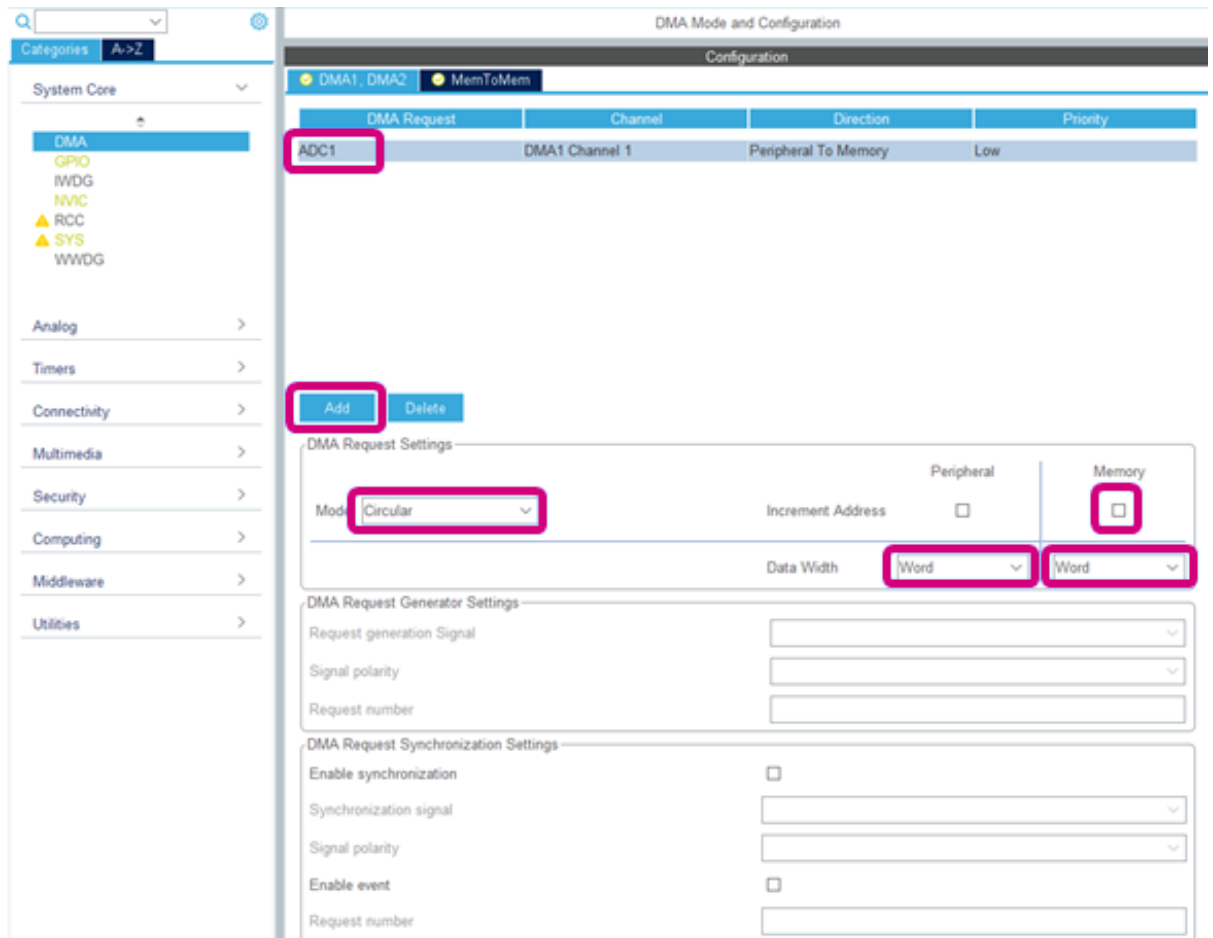

The DMA configuration on this tab is now complete. Next, the ADC is configured. Expand the Analog peripheral list and click on ADC1. Click on the GPIO Settings tab and the list of pins already configured is shown. These are configured based on the EVM default, which is loaded when the project is created. However, the USBPD_VIN is not required for this project and this can be removed by changing IN8 to Disable.

Figure 34. Removing pin from the project

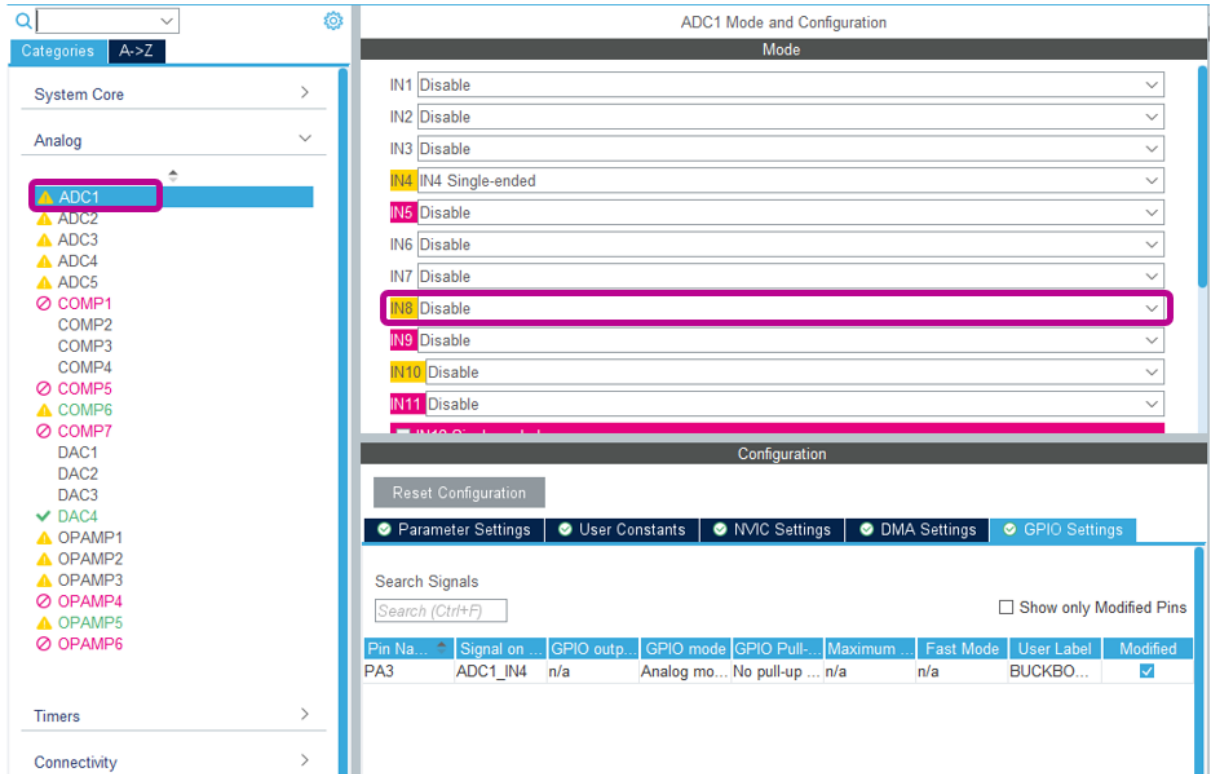

On this screen, it can also be seen that ADC Channel 4 (ADC_IN4) has the user label BUCKBOOST_VOUT and is connected to PA3. This is the output voltage of the step-down converter. This is required in the next configuration step. Click on the Parameter Settings tab. Here, under the ADC_Settings section, the Data Alignment may be changed to Left Aligned. This stores the 12-bit result from the ADC in the 16-bit results register with left alignment. That means the upper 12-bits (plus 1 sign bit) of the 16-bit register are used.

Change the DMA Continuous Requests setting to Enabled. Under the ADC_Regular_ConversionMode section, set the External Trigger Conversion Source to High Resolution Trigger 1 event. Then set the External Trigger Conversion Edge to Trigger detection on the rising edge. For this voltage mode step-down converter, only one ADC conversion is required. This is the output voltage rail that is regulated. Therefore, the number of conversions is currently set to one. This conversion can be configured by expanding the Rank subcategory. Set the Channel to Channel 4 (this is the channel associated with the output voltage from the previous step). Then configure the Offset Number to 1 Offset. The offset feature of the ADC allows an offset to be subtracted from the ADC value before it is stored in the results register. This is used to perform the error calculation, $VERR = VREF - VOUT$, in hardware. Set the Offset value to REF. REF is a term that is defined in the code later on. By default, STM32CubeMX has error-checking on the input fields. To disable this and allow the currently unknown value REF to be entered into this input field, click on the cog symbol on the right-hand side of the input value and change the check to No check.

Figure 35. ADC parameter settings

Parameter	Value
Mode	Independent mode
Clock Prescaler	Synchronous clock mode divided by 4
Resolution	ADC 12-bit resolution
Data Alignment	Left alignment
Gain Compensation	0
Scan Conversion Mode	Disabled
End Of Conversion Selection	End of single conversion
Low Power Auto Wait	Disabled
Continuous Conversion Mode	Disabled
Discontinuous Conversion Mode	Disabled
DMA Continuous Requests	Enabled
Overrun behaviour	Overrun data overwritten
Enable Regular Conversions	Enable
Enable Regular Oversampling	Disable
Number Of Conversion	1
External Trigger Conversion Source	High Resolution Timer Trigger 1 event
External Trigger Conversion Edge	Trigger detection on the rising edge
Rank	1
Channel	Channel 4
Sampling Time	12.5 Cycles
Offset Number	1 offset
Offset	REF
Offset Sign	Offset Sign Negative
Offset Saturation	Disable
Enable Injected Conversions	Disable

Still, on the ADC1 configuration pane, click on the `NVIC Settings` tab and disable the ADC interrupt by unticking the `ADC1 and ADC2 global interrupt` checkbox.

Figure 36. NVIC settings tab

Parameter Settings User Constants NVIC Settings DMA Settings GPIO Settings				
NVIC Interrupt Table		Enabled	Preemption Priority	Sub Priority
DMA1 channel1 global interrupt		<input checked="" type="checkbox"/>	0	0
ADC1 and ADC2 global interrupt		<input type="checkbox"/>	0	0


The ADC configuration is now complete.

6.2.4 HRTIM configuration

Next, the hi-resolution timer module is configured to generate the PWM. On the left-hand side peripherals pane, expand the `Timers` category, and click on `HRTIM1`.

The discovery kit has multiple switching power stages onboard and the timers for these are configured by default when the project is created. However, for this voltage mode step-down converter, only `Timer C` is required. Disable all of the other timers as shown in the screenshot below.

Figure 37. All timers except C disabled

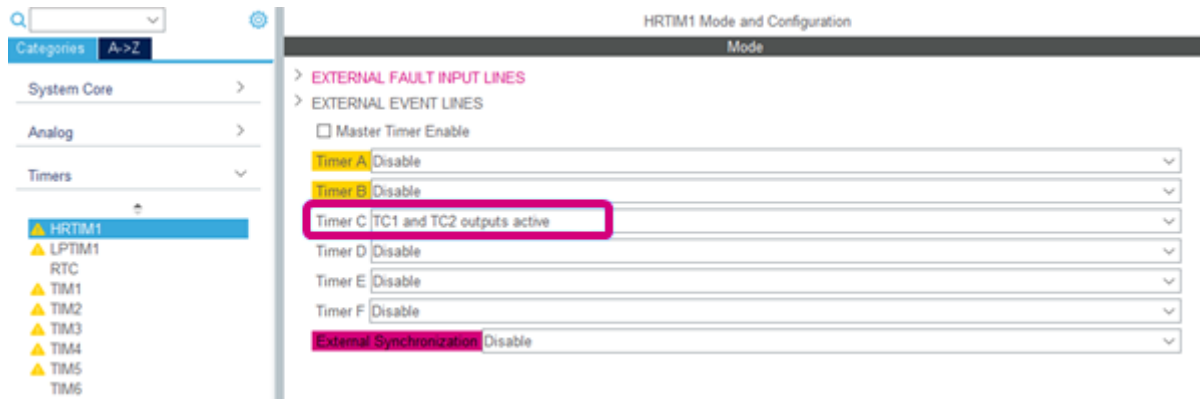

The power stage of the discovery kit contains boost switches that are following the buck stage and are used when operating as a noninverting buck-boost converter. These boost switches are controlled by timer D, however, in this application note, the boost switches are not driven by PWM. The boost switches form part of the buck power stage current path, and therefore they must be configured in either a HIGH or LOW state to allow the buck stage to function correctly.

Now that `Timer D` is disabled, go back to the `Pinout` view of the microcontroller. `PB15` and `PB14` may be highlighted in yellow. These are the pins that control the boost switches. Left-click on `PB15` and `PB14` and configure them both as a `GPIO_Output`.

Right-click on `PB15` and select `Enter User Label`. Enter the label: `BUCKBOOST_P2_DRIVE`.

Right-click on `PB14` and select `Enter User Label`. Enter the label: `BUCKBOOST_N2_DRIVE`.

Within the program code, these pins are set either HIGH or LOW to enable or disable the boost switches and allow the converter to operate under buck mode.

Next, within the `HRTIM1` configuration pane, click on the `Timer C` configuration tab. First, the `Time Base Settings` section must be configured. Set the period value to `27200`, and the tool may automatically switch from hex to decimal when pressing enter. The resulting PWM period may now be calculated as `200 000 Hz`.

The next section on the `Timer C` configuration tab is the `Timing Unit` section settings. Here, change the `Dead Time` insertion to `Deadtime is inserted between output 1 and output 2`. This enables the `deadtime` section, which allows the outputs to be configured such that both high-side and low-side switches are never driven at the same time.

Figure 38. Timer C configuration tab - part 1

The screenshot shows the STM32CubeMX configuration interface for Timer C. The top navigation bar includes tabs for Timer C, User Constants, NVIC Settings, DMA Settings, and GPIO Settings. Below this, there are sub-tabs for Fault Lines Configuration, ADC Triggers Configuration, Burst Mode Configuration, HRTIM Interrupt Configuration, Synchro Configuration, High Resolution, and External Event Configuration. The main configuration area is titled 'Configure the below parameters :'. A search bar is present at the top left. The 'General' section is expanded, showing 'Timer Idx' as 'Timer C' and 'Basic/Advanced Configuration' as 'Advanced (using HAL_Waveform methods)'. The 'Time Base Setting' section is expanded, showing 'Prescaler Ratio' as 'HRTIM Clock Multiplied by 32 (HRTIM Clock is set in Clock Configur...', 'fHRCK Equivalent Frequency' as '5.44E9 Hz', and 'Period' as '27200'. The 'Timing Unit' section is also expanded, showing 'Interleaved Mode' as 'Disabled', 'Start On Sync' as 'Synchronization input event has no effect on the timer', 'Reset On Sync' as 'Synchronization input event has no effect on the timer', 'Dac Synchro' as 'No DAC synchronization event generated', 'Preload Enable' as 'Preload disabled: the write access is directly done into the active re...', 'Update Gating' as 'Update done independently from the DMA burst transfer completion', 'Repetition Update' as 'Update on repetition disabled', 'Burst Mode' as 'Timer counter clock is maintained and the timer operates normally', 'Push Pull' as 'Push-Pull mode disabled', 'Number of Faults to enable' as '0', 'Fault Lock' as 'Timer fault enabling bits are read/write', 'Dead Time Insertion' as 'Deadtime is inserted between output 1 and output 2', 'Delayed Protection Mode' as 'No action', 'Update Trigger Sources Selection : Please enter the num...' as '0', 'Reset Update' as 'Update by Timer reset / roll-over disabled', 'Resynchronized Update' as 'Update taken into account immediately', 'Reset Trigger Sources Selection : Please enter the numb...' as '0', 'Interrupt Requests Sources Selection : Please enter the ...' as '0', and 'Number of Timer C Internal DMA Request Sources - you ...' as '0'.

Further down the `Timer C` configuration tab is the section for configuring the compare units. These compare units allow events to be configured based on a comparison between the individual compare unit and the timer counter. For this example, three compare units are configured as follows.

For `Compare Unit 1` section change the configuration setting to `Enable`. Set the `Compare Value` to `DUTY_TICKS_MIN`. This is the initial value of the duty cycle fixed at 0.35%. The compare event is used later on as a reset source to clear the output.

For `Compare Unit 2` section change the configuration setting to `Enable`. Set the `Compare Value` to `DUTY_TICKS_MAX`. This is the maximum value of the duty cycle fixed at 90%. The compare event is used later on as a reset source to clear the output. `DUTY_TICKS_MIN` and `DUTY_TICKS_MAX` terms that are defined on the code later on.

For Compare Unit 3 section change the configuration setting to Enable. Enter a Compare Value of 50. This is the event that is used to trigger the ADC sample. This can be moved to a clean point in the switching cycle, which means away from the turn-on or turn-off of the switch.

Figure 39. Timer C configuration tab-part 2

The screenshot shows the 'Timer C' configuration tab with several sub-tabs: User Constants, NVIC Settings, DMA Settings, GPIO Settings, Fault Lines Configuration, ADC Triggers Configuration, Burst Mode Configuration, HRTIM Interrupt Configuration, Synchro Configuration, High Resolution, and External Event Configuration. The main configuration area is titled 'Configure the below parameters :'. It contains a search bar and a list of configuration items for Compare Units 1 through 4. The following table summarizes the visible settings:

Parameter	Value	Description
Compare Unit 1 Configuration	Enable	
Compare Value	DUTY_TICKS_MIN	Timer Compare 1 event is generated when counter is equal
Greater-than comparison		
Compare Unit 2 Configuration	Enable	
Triggered-Half Mode		Timer Compare 2 register is behaving in standard mode
Compare Value	DUTY_TICKS_MAX	
Auto Delayed Mode		standard compare mode
Compare Unit 3 Configuration	Enable	
Compare Value	50	
Greater-than comparison		Timer Compare 3 event is generated when counter is equal
Compare Unit 4 Configuration	Disable	

The next section to configure on the Timer C configuration tab is the Dead Time section. Locate this section and set the Rising Value to DEAD_TIME_RISING_NS and Falling Value to DEAD_TIME_FALLING_NS. DEAD_TIME_RISING_NS and DEAD_TIME_FALLING_NS defined on code to have 75 ticks Rising value and 200 ticks Falling value.

Figure 40. Timer C configuration tab - part 3

The screenshot shows the 'Timer C' configuration tab with the same sub-tabs as Figure 39. The 'Dead Time' section is expanded, showing the following settings:

Parameter	Value	Description
Dead Time Configuration	Enable	
Prescaler (PSC - 16 bits value)	$t_{DTG} = t_{HRTIM} * 8$	
Rising Value	DEAD_TIME_RISING_NS	
Rising Sign		Positive deadtime on rising edge
Rising Lock		Deadtime rising value and sign is writable
Rising Sign Lock		Deadtime rising sign is writable
Falling Value	DEAD_TIME_FALLING_NS	
Falling Sign		Positive deadtime on falling edge
Falling Lock		Deadtime falling value and sign is writable
Falling Sign Lock		Deadtime falling sign is writable

The last two sections to configure on the Timer C configuration tab are the Output 1 Configuration and Output 2 Configuration sections. These are located toward the bottom of the tab.

Under the Output 1 Configuration section, change the Set Source Selection number to 1, then the 1st Set Source event to the Timer period event forces the output to its active state.

Change the Reset Source Selection number to 2. Change the 1st Reset Source event to Timer compare 1 event forces the output to its inactive state. Then change the 2nd Reset Source event to Timer compare 2 event forces the output to its inactive state.

Finally, set the Fault Level to Output at inactive level when in FAULT state.

Figure 41. Timer C configuration tab - part 4

Timer C	User Constants	NVIC Settings	DMA Settings	GPIO Settings
Fault Lines Configuration	ADC Triggers Configuration	Burst Mode Configuration		
HRTIM Interrupt Configuration	Synchro Configuration	High Resolution	External Event Configuration	

Configure the below parameters :


Search (Ctrl+F)

- Falling Sign: Positive deadtime on falling edge
- Falling Lock: Deadtime falling value and sign is writable
- Falling Sign Lock: Deadtime falling sign is writable
- Swap Output1 and Output2: TC1 Output is sensitive to TC2 Control Registers and vice... Disable
- Output 1 Configuration
 - Output1 Configuration: TC1
 - Polarity: Output is active HIGH
 - Set Source Selection : Please enter the number of Activ. **1**: Timer period event forces the output to its active state
 - 1st Set Source
 - Reset Source Selection : Please enter the number of Ac. **2**: Timer compare 1 event forces the output to its inactive state
 - 1st Reset Source: Timer compare 2 event forces the output to its inactive state
 - 2nd Reset Source
 - Idle Mode: The output is not affected by the burst mode operation
 - Idle Level: Output at inactive level when in IDLE state
 - Fault Level: **Output at inactive level when in FAULT state .**
 - Chopper Mode Enable: Output signal is not altered
 - Burst Mode Entry Delayed: The programmed Idle state is applied immediately to the Output
- Output 2 Configuration
 - Output2 Configuration: TC2
 - Polarity: Output is active HIGH
 - Set Sources: nothing to set as Dead Time is enabled, Ou... 0
 - Reset Sources: nothing to set as Dead Time is enabled, ... 0
 - Idle Mode: The output is not affected by the burst mode operation
 - Idle Level: Output at inactive level when in IDLE state
 - Fault Level: The output is not affected by the fault input
 - Chopper Mode Enable: Output signal is not altered
 - Burst Mode Entry Delayed: The programmed Idle state is applied immediately to the Output

The Output 2 Configuration section is left unchanged as this output is driven by the dead-time configuration entered earlier.

Finally, the ADC trigger must be configured for the HRTIM1 module. Under HRTIM1 select the ADC Triggers Configuration tab. Enable the ADC Trigger 1 and set the Update Trigger Source to Timer C, and enter the number of Trigger Sources Selection to 1. From the 1st Trigger Source drop-down box, select ADC Trigger on Timer C compare 3. This is the event that triggers the ADC.

Figure 42. ADC triggers configuration

 

6.2.5 FMAC configuration

The last peripheral, which requires configuration is that of the FMAC. As discussed earlier, the FMAC is used to execute the controller and compute the new value of the duty cycle for this voltage mode step-down converter. To enable the FMAC, expand the Computing category on the left-hand side of the window. Select FMAC and on the configuration pane tick the Activated box. Also, tick the box to enable the FMAC interruption under the NVIC Settings tab.

Figure 43. FMAC configuration window



6.2.6 IRQ handler configuration

By default, STM32CubeMX creates interrupt handlers for the configured peripherals. These are created in a separate interrupt handler .c file within the project. If the user wishes to create their interrupt handler function then the automatic generation of the IRQ handler function must be disabled for that peripheral.

In this application note, the user writes his SysTick handler function and therefore the automatic generation of this IRQ handler must be disabled. To do this click on the NVIC subcategory within the System Core category on the left-hand side of the window. Click on the Code Generation tab. Untick the Generate IRQ handler checkbox for Time base: System tick timer as per the image below.


Figure 44. Automatic IRQ handler generation disabled

Enabled interrupt table	<input type="checkbox"/> Select for init sequence ordering	Generate Enable in Init	<input type="checkbox"/> Generate IRQ handler	Call HAL handler
Non maskable interrupt	<input type="checkbox"/>	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>
Hard fault interrupt	<input type="checkbox"/>	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>
Memory management fault	<input type="checkbox"/>	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>
Prefetch fault, memory access fault	<input type="checkbox"/>	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>
Undefined instruction or illegal state	<input type="checkbox"/>	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>
System service call via SWI instruction	<input type="checkbox"/>	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>
Debug monitor	<input type="checkbox"/>	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>
Pendable request for system service	<input type="checkbox"/>	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>
Time base: System tick timer	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
EXTI line2 interrupt	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
EXTI line4 interrupt	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
DMA1 channel1 global interrupt	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
EXTI line[9:5] interrupts	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
EXTI line[15:10] interrupts	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
FMAC interrupt	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Within the code, the DMA interrupt is disabled. Therefore the IRQ handler for the DMA is also not needed and can be unticked.

Finally, generate the project by clicking the GENERATE CODE button. This creates the necessary project files for the selected IDE. In this example, the IAR Embedded Workbench® from IAR Systems is used. However, there are multiple IDEs for which STM32CubeMX can generate project files, including the free use of STM32CubeIDE from STMicroelectronics.

Figure 45. Code generation launch

 

A prompt appears once the project files are created, which asks if the user likes to open the project. Click Open Project to load the project into the selected IDE.

Figure 46. Project opening after code generation




The `main.c` file contains the code for this project. Open the `main.c` file and read the comments.

6.3 Program flow description

The `main.c` file contains the majority of the code for setting up and initializing the peripherals. Some of the code within this file is automatically generated by the STM32CubeMX tool as per the configuration process in the previous step of this application note. The `main.c` file is structured as shown in Figure 47.

Figure 47. Program flow within `main.c`

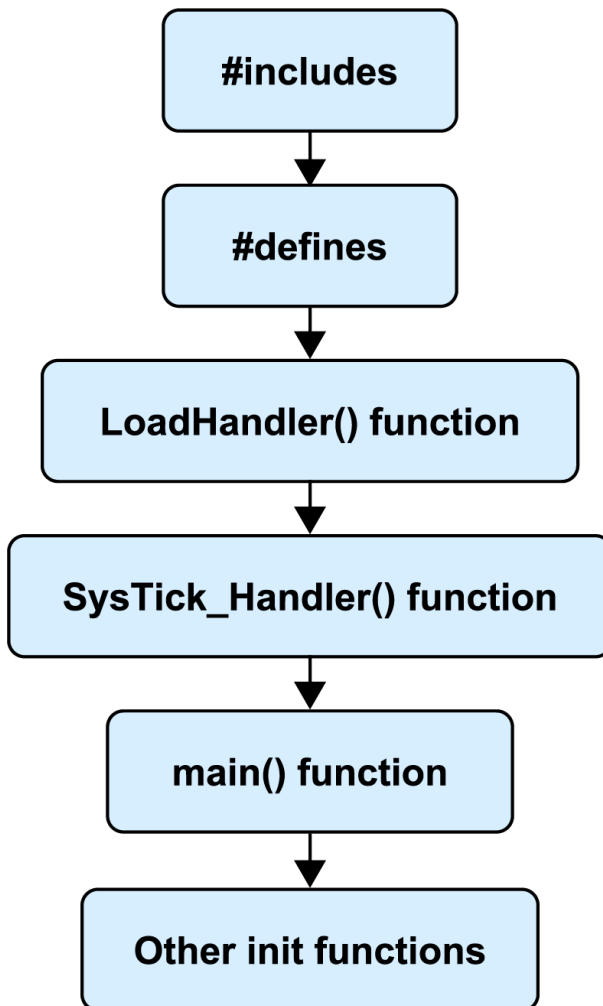

Within these code files, there are comments similar to `USER CODE BEGINS HERE` and `USER CODE ENDS HERE`. Any additional code to the project is kept between these two comments. This is because, outside of these comments, the code is automatically generated by the STM32CubeMX tool. If any changes are made to the project configuration within the tool, and the code is re-generated by clicking `GENERATE CODE`, the additional changes made outside of these comment bounds are lost. Keeping the user code within these comment bounds ensures that the code persists after the next time the code is re-generated using the STM32CubeMX tool. Figure 48 shows examples of the user code locations highlighted in fuchsia.

Figure 48. Example of user code locations within main.c

```

/**
 * @brief The application entry point.
 * @retval int
 */
int main(void)
{
    /* USER CODE BEGIN 1 */
    /* USER CODE END 1 */

    /* MCU Configuration-----*/

    /* Reset of all peripherals, Initializes the Flash interface and the Systick. */
    HAL_Init();

    /* USER CODE BEGIN Init */
    /* USER CODE END Init */

    /* Configure the system clock */
    SystemClock_Config();

    /* USER CODE BEGIN SysInit */
    /* USER CODE END SysInit */


    /* Initialize all configured peripherals */
    MX_GPIO_Init();
    MX_DMA_Init();
    MX_RTC_Init();
    MX_ADC1_Init();
    MX_HRTIM1_Init();
    MX_FMAC_Init();
    /* USER CODE BEGIN 2 */

    /*## Configure the FMAC peripheral #####*/
    sFmacConfig.InputBaseAddress = INPUT_BUFFER_BASE;
    sFmacConfig.InputBufferSize = INPUT_BUFFER_SIZE;
    sFmacConfig.InputThreshold = INPUT_THRESHOLD;
    sFmacConfig.CoeffBaseAddress = COEFFICIENT_BUFFER_BASE;
}

```


The structure of the main function within the `main.c` file is represented in Figure 49. This is the function that the MCU jumps to after power on – the entry point within the code. Therefore, this function contains calls to all of the initialization functions to set up the peripherals onboard the MCU. After this, the controller for the buck converter is set up and initialized with the calculated coefficients. Finally, the ADC is started and begins sampling the output voltage and the PWM outputs are enabled to drive the buck switches.

Figure 49. Function flow of `main()` within `main.c`

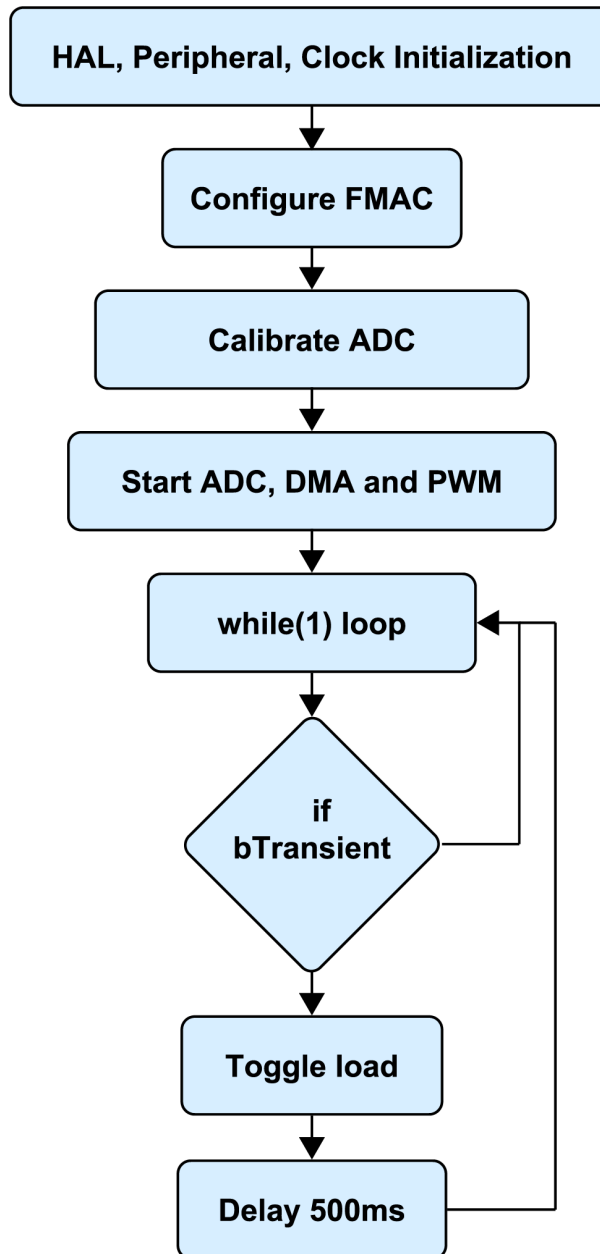

The sampling of the ADC module is triggered by the HRTIM module, in this case by comparing unit 3, which is set to a certain number of HRTIM ticks after the beginning of the switching period to avoid switching noise corrupting the sample. Once the sampling and conversion are complete, the ADC triggers the DMA to copy the result directly from the `ADC_results` register to the FMAC input register. This process is depicted in Figure 50.

Figure 50. ADC, DMA, and FMAC timing diagram

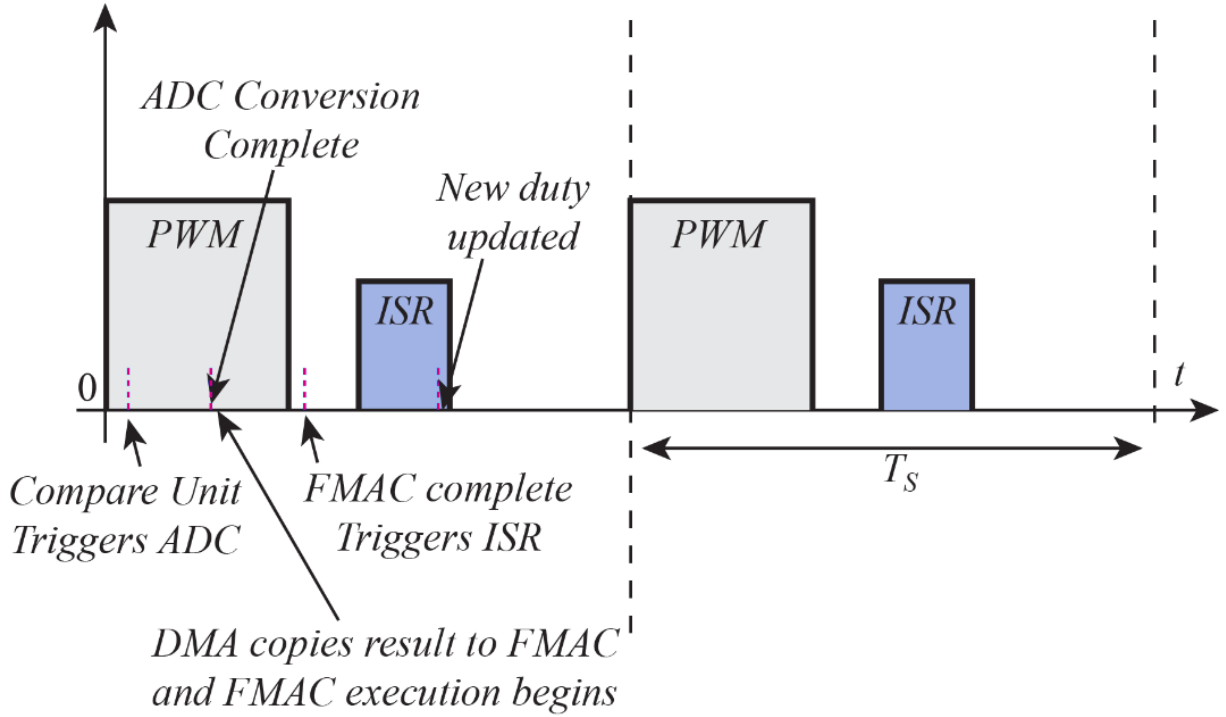


6.4 Interrupt service routine

After the FMAC completes the execution of the 3p3z controller, it triggers an interrupt. The interruption causes the MCU to jump from wherever it is, most likely sitting in the `while(1)` loop within `main()`, and execute the code within the FMAC ISR. The FMAC ISR is a separate function that is located towards the end of the `stm32g4xx_it.c` file included with this project. It has the function name `FMAC_IRQHandler(void)`.

The purpose of this FMAC ISR is to perform bounds checking on the output of the 3p3z controller executed using the FMAC. The output of the controller is the new value of the duty cycle and is written to the compare unit 1 register of the HRTIM. However, the compare unit has a maximum value equal to that of the period register. Therefore, the logic depicted in [Figure 51](#) is implemented within the user code section of the FMAC ISR.

Figure 51. FMAC ISR flow

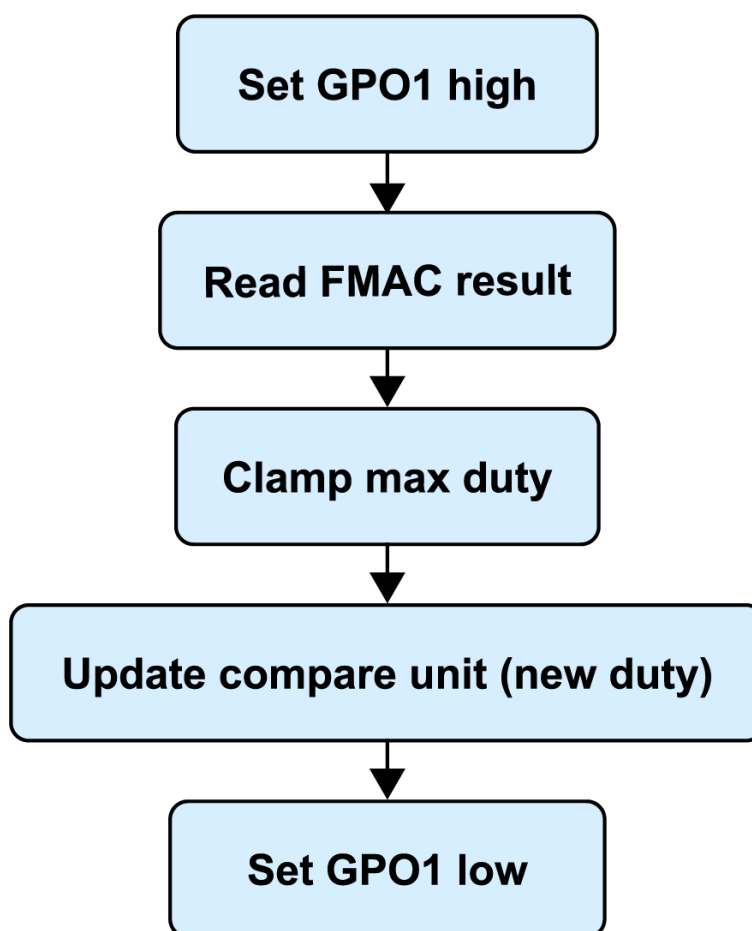

6.5 3p3z controller coefficients

Depending on the example source, respectively either the G4 intropack example or either the D-Power pack generated example, the 3p3z controller coefficients are defined in the `main.h` (resp. `app_dpowers.h`) header file. This can be easily accessed by locating `#include "main.h"` (resp. `#include "app_dpowers.h"`) towards the top of the `main.c` file (resp. `app_dpowers.h`), then right-clicking on `main.h` (resp. `app_dpowers.h`) and selecting `Open main.h` (resp. `app_dpowers.h`) from the menu.


Further down this file, there is a `/* USER CODE BEGIN Private defines */` section where the definitions for the FMAC configuration begin. The controller coefficients are defined below the FMAC configuration parameters. These coefficients (`B0`, `B1`, `B2`, `B3`, `A1`, `A2`, `A3`) are given in a fixed-point hexadecimal form. Earlier in this application note, it is shown how the compensator poles and zeros, in the continuous-time domain, are converted into discrete-time controller coefficients. The last step required is to convert these discrete-time controller coefficients into fixed point form for use on the fixed point FMAC.

6.6 ST-WDS configuration

The power supply design tool ST-WDS from Biricha is used to generate the fixed-point controller coefficients for this controller implemented on the FMAC. ST-WDS is free-to-use and can be downloaded for free from the Biricha website.

The .wds file associated with this application note is included in the project downloads in the appendix of this application note. However, the process for recreating the WDS project settings is included here for completeness.

Figure 52. Biricha ST-WDS

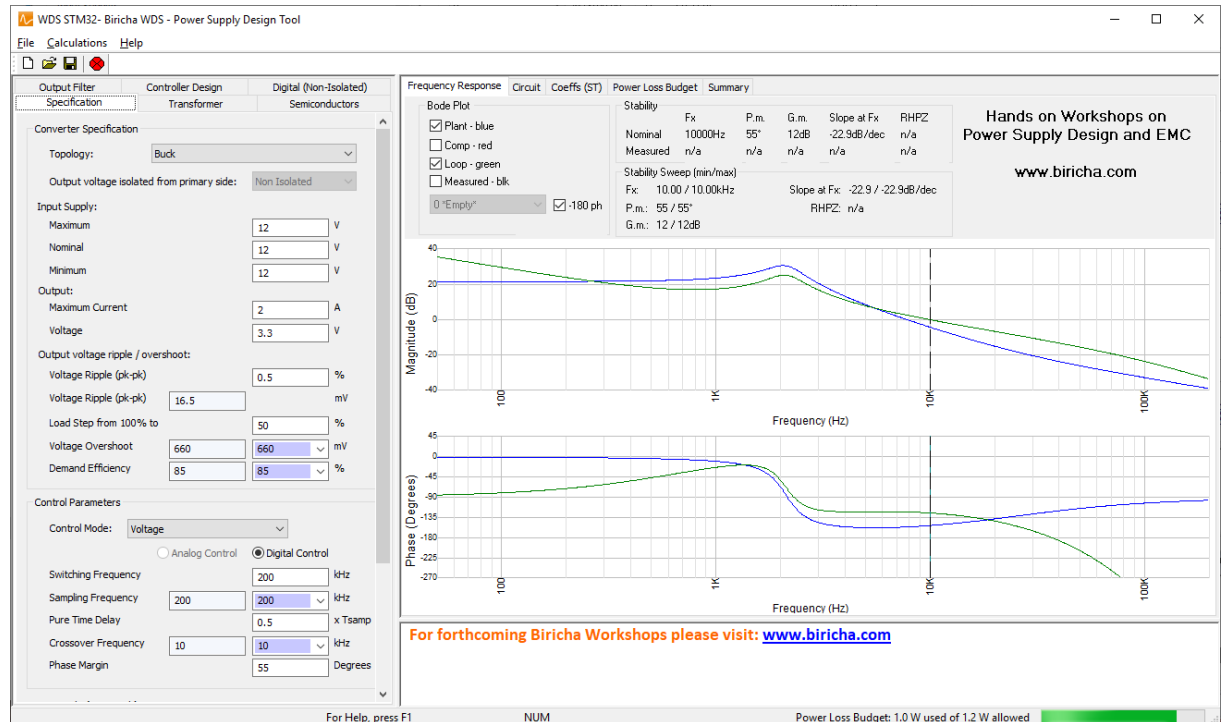

The initial screen of ST-WDS is shown in Figure 52. The left-hand pane is used for entering the specification of the power supply along with the other pertinent design parameters. The right-hand pane displays the control loop Bode plots, schematic, and outputs the required digital controller coefficients.

To calculate the digital controller coefficients the power supply specification must first be entered. On the `Specification` tab, enter the specification shown in [Table 2](#).

Table 2. Discovery kit specification

Specification tab parameter	Value
Topology	Buck
Input supply max	5 V
Input supply nom	5 V
Input supply min	5 V
Output maximum current	0.2 A
Output voltage	3.3 V
Voltage ripple (peak-to-peak)	0.5%
Load step 100% to...	50%
Voltage overshoot	5 mV
Demand efficiency	92%
Control mode	Voltage, digital control
Switching frequency	200 kHz
Pure time delay	1
Crossover frequency	8 kHz
Phase margin	50°
Maximum duty limit	90%
Minimum duty limit	0%

The Specification tab may now look like the screenshot shown in Figure 53.

Figure 53. ST-WDS specification tab

Output Filter	Controller Design	Digital (Non-Isolated)	
Specification	Transformer	Semiconductors	
Converter Specification			
Topology:	Buck		
Output voltage isolated from primary side:	Non Isolated		
Input Supply:			
Maximum	5	V	
Nominal	5	V	
Minimum	5	V	
Output:			
Maximum Current	0.2	A	
Voltage	3.3	V	
Output voltage ripple / overshoot:			
Voltage Ripple (pk-pk)	0.5	%	
Voltage Ripple (pk-pk)	16.5	mV	
Load Step from 100% to	50	%	
Voltage Overshoot	660	5	mV
Demand Efficiency	85	92	%
Control Parameters			
Control Mode:	Voltage		
	<input type="radio"/> Analog Control	<input checked="" type="radio"/> Digital Control	
Switching Frequency	200	kHz	
Sampling Frequency	200	200	kHz
Pure Time Delay	1	x Tsamp	
Crossover Frequency	10	8	kHz
Phase Margin		50	Degrees
Duty Cycle (per switch)			
Maximum Duty Limit	90	%	
Minimum Duty Limit	0	%	
Maximum	67.953	%	
Nominal	67.953	%	
Minimum	67.953	%	

The `Transformer` tab is not used as this is a step-down converter. This tab is only applicable for topologies that include a power stage transformer. Next, click on the `Semiconductors` tab and enter the specification shown in Table 3.

Table 3. Semiconductors tab parameter

Semiconductors tab parameter	Value
ON resistance	56 mΩ
Rise time	20 ns
Fall time	20 ns
Parasitic capacitance (Coss)	79 pF
Forward voltage drop	0.02 V

The `Semiconductors` tab may now look like the screenshot shown in Figure 54.

Figure 54. ST-WDS semiconductor tab

Output Filter	Controller Design	Digital (Non-Isolated)
Specification	Transformer	Semiconductors
Primary Switch		
"On" Resistance	< <input type="text" value="20"/>	<input type="text" value="56"/> mΩ
Rise Time	< <input type="text" value="20.155"/>	<input type="text" value="20"/> ns
Fall Time	< <input type="text" value="20.155"/>	<input type="text" value="20"/> ns
Parasitic Cap (Coss)	< <input type="text" value="2029.204"/>	<input type="text" value="79"/> pF
Peak Switch Voltage	<input type="text" value="5.02"/>	V
Average Switch Current	<input type="text" value="0.136"/>	A
RMS Switch Current	<input type="text" value="0.167"/>	A
Peak Switch Current	<input type="text" value="0.254"/>	A
Conduction Losses	<input type="text" value="0.002"/>	W
Switching Losses	<input type="text" value="0.005"/>	W
Recommended values for calculations		
Diode/Switch		
Forward Voltage Drop	<input type="text" value="0.6"/>	<input type="text" value="0.02"/> V
Peak Voltage Stress	<input type="text" value="4.989"/>	V
Average Current	<input type="text" value="0.064"/>	A
RMS Current	<input type="text" value="0.115"/>	A
Peak Current	<input type="text" value="0.254"/>	A
Conduction Losses	<input type="text" value="0.001"/>	W
Recommended values for calculations		
Note: Values exclude the effects of parasitics not listed		

The Output Filter tab is next and has the specification shown in Table 4.

Table 4. Output filter parameters

Output filter tab parameter	Value
Specified peak-to-peak ripple	25%
L0 inductance	51 μ H
L0 DCR	380 m Ω
C0 capacitance	100 μ F
C0 ESR	170 m Ω

The Output Filter tab may now look like the screenshot shown in Figure 55.

Figure 55. ST-WDS output filter tab

Specification	Transformer	Semiconductors
Output Filter	Controller Design	Digital (Non-Isolated)
Power Choke		
Specified Ripple (pk-pk)		25 %
Specified Ripple (pk-pk)	0.05	A
L0 Inductance	109.594	51 μ H
L0 DCR		380 m Ω
Actual % Ripple (pk-pk)	53.7	%
Actual Ripple (pk-pk)	0.107	A
Peak Current	0.254	A
Average Current	0.2	A
Power Dissipation	0.015	W
DCM/CCM Boundary	0.053	A
Recommended values for calculations		
Output Filter Capacitor		
C0 Capacitance	480.399	100 μ F
C0 ESR	28.018	170 m Ω
C0 ESR Zero	9362.055	Hz
Specified Overshoot	5	mV
Actual Overshoot	26.168	mV
Specified Ripple (pk-pk)	16.5	mV
Actual Ripple (pk-pk)	18.099	mV
RMS Current	0.031	A
Ripple Current (pk-pk)	0.106	A
Peak Voltage	3.318	V
Power Dissipation	0.16	mW
Recommended values for calculations		
Calculated capacitance is based on the overshoot requirement to meet both overshoot and voltage ripple specifications (without second stage filter).		

On the next tab, *Controller Design*, a Type-III compensator is automatically designed by ST-WDS by placing the compensator poles and zeros to achieve the desired crossover frequency and phase margin. There is no need to enter any parameters into this tab as the poles and zeros are already calculated and may match those given in [Table 5](#).

Table 5. Controller design parameters

Controller design parameter	Value
Pole at the origin	1195.78 Hz
First pole	9362.055 Hz
Second pole	100000 Hz
First zero	1843.463 Hz
Second zero	2217.222 Hz

Figure 56. ST-WDS controller design tab

Specification	Transformer	Semiconductors
Output Filter	Controller Design	Digital (Non-Isolated)

Controller Type

Type III ▼

$$H_c(s) = \frac{\omega_{zp0}}{s} \frac{\left(\frac{s}{\omega_{z1}} + 1\right) \left(\frac{s}{\omega_{z2}} + 1\right)}{\left(\frac{s}{\omega_{p1}} + 1\right) \left(\frac{s}{\omega_{p2}} + 1\right)}$$

Op-amp Transconductance Amp

Transconductance Factor gm n/a μMho/μS

PWM Parameters

PWM Ramp Height (pk-pk) n/a V

Current Sense and Slope Compensation

Current Sense Gain < n/a V/A

Magnetizing "Free" Ramp n/a V(pk-pk)

Optimal External Ramp n/a V(pk-pk)

Amount of Ramp to Add n/a V(pk-pk)

Ramp Slope n/a mV/μsec

V. on Current Sense Pin n/a V

Controller Poles and Zeros

Automatic placement Manual placement

Pole at the origin	1195.78	1195.78	Hz
First Pole	9362.055	9362.055	Hz
Second Pole	100000	100000	Hz
First Zero	1843.463	1843.463	Hz
Second Zero	2217.222	2217.222	Hz

The last configuration tab is Digital (Non-Isolated). Enter the specification given in the following table.

Table 6. Digital nonisolated parameters

Digital nonisolated tab parameter	Value
PWM controller clock frequency	5440 MHz
Maximum PWM period count	27200
ADC bits	12 bits
ADC range	3.3 V
Pre-ADC input scaling	0.2

Figure 57. ST-WDS digital nonisolated tab

Specification	Transformer	Semiconductors	
Output Filter	Controller Design	Digital (Non-Isolated)	
PWM Parameters			
PWM Master Clock Frequency	<input type="text" value="5440"/>	MHz	
Max PWM Period Count	<input type="text" value="27200"/>	<input type="text" value="27200"/> ▾	
MIN	<input type="text" value="0"/>		
MAX	<input type="text" value="24480"/>		
Sampling Divider and ADC			
ADC Bits	<input type="text" value="12"/>	bits	
ADC Range	<input type="text" value="3.3"/>	V	
Pre-ADC Input Scaling	<input type="text" value="0.89"/>	<input type="text" value="0.2"/> ▾	
Voltage on ADC Pin	<input type="text" value="0.66"/>	V	
REF	<input type="text" value="819"/>		
DAC (if available)			
DAC Bits	<input type="text" value="n/a"/>	bits	
DAC Range	<input type="text" value="n/a"/>	V	
Raw Floating Point Controller Coefficients from BZT			
A1	<input type="text" value="1.521558802886"/>	B0	<input type="text" value="1.553498602786"/>
A2	<input type="text" value="-0.35645887262"/>	B1	<input type="text" value="-1.361492352512"/>
A3	<input type="text" value="-0.165099930267"/>	B2	<input type="text" value="-1.547613028951"/>
K	<input type="text" value="109.5970696"/>	B3	<input type="text" value="1.367377926347"/>
<input type="button" value="Copy to Clipboard"/>			

Now that the controller coefficients are calculated, they need to be converted into the format required for a use with the fixed point FMAC. To do this within ST-WDS, click on the *Coeffs (ST)* tab on the right-hand pane. Here, set the *Controller Type* and *Output setting* to *FMAC (Fixed Point)*. Earlier within the *STM32CubeMX* configuration, the *ADC result* is configured to be left-aligned. Therefore, click on the *ADC Result Left-Aligned* radio button within ST-WDS. The pane may now look like [Figure 58](#).

Figure 58. Fixed point controller coefficient calculation in ST-WDS

The screenshot shows the ST-WDS software interface for calculating fixed-point controller coefficients. The **Coeffs (ST)** tab is selected. The **Controller Type and Output** section has **FMAC (Fixed Point)** selected, and **ADC Result Left-Aligned** is also selected. The **Pre Left Shift** is set to 3 bits and **Post Left Shift** is set to 5 bits. The **Output Gain** is set to 5. The **3p3z Controller** block diagram shows the transfer function:
$$\frac{B_3 z^{-3} + B_2 z^{-2} + B_1 z^{-1} + B_0}{-A_3 z^{-3} - A_2 z^{-2} - A_1 z^{-1} + 1}$$
 The **Floating Point Controller Coefficients** section displays: B0: 1.553498602786, B1: -1.361492352512, B2: -1.547613028951, B3: 1.367377926347, A1: 1.521558802886, A2: -0.35645887262, A3: -0.165099930267, K: 109.59707. The **Controller Coefficients (FMAC - Fixed Point Format)** section shows: B0*K (hex): 0x5521, B1*K (hex): 0xB564, B2*K (hex): 0xAB31, B3*K (hex): 0x4AEE, B0*K (double): 0.665073806596, B1*K (double): -0.582873328571, B2*K (double): -0.662554112669, B3*K (double): 0.585393022497, A1 (hex): 0x616, A2 (hex): 0xFE93, A3 (hex): 0xFF57, A1 (double): 0.047548712590, A2 (double): -0.011139339769, A3 (double): -0.005159372821.

The fixed-point coefficients are now displayed at the bottom of the window. It is now possible to copy these to the clipboard for use within the code. Click the *Copy Hex to Clipboard* button. The following coefficients may now be on the clipboard:

```
#define B0 (0x5521)
#define B1 (0xB564)
#define B2 (0xAB31)
#define B3 (0x4AEE)
#define A1 (0x616)
#define A2 (0xFE93)
#define A3 (0xFF57)
#define pre_shift (+3)
#define post_shift (+5)
#define REF (812)
#define DUTY_TICKS_MIN (0x60)
#define DUTY_TICKS_MAX (24480)
```

These are the coefficients that are used within the example application.

6.7 CCM-SRAM usage

The CCM-SRAM is an area of memory that is tightly coupled to the Arm® Cortex® core. This allows the core to execute the code at the maximum clock rate. And this happens without any wait-states as typically found when execution from the flash memory.

This functionality is ideal for routines that are time-critical such as the control loop implementation discussed in this application note. The STM32G474RE device featured on the Discovery kit contains 32 Kbytes of CCM-SRAM that can also be accessed via the DMA.

To use the CCM-SRAM area of memory, the memory areas must be defined in the linker files. The code must be copied from the flash memory to the CCM-SRAM area at program startup. Therefore, there are several steps to follow to achieve this. The application note *Use STM32F3/STM32G4 CCM SRAM with IAR™ EWARM, Keil® MDK-ARM and GNU-based toolchains* (AN4296) contains step-by-step instructions for implementing this functionality using the different IDEs.


7 Design example

7.1 Power stage component selection

The discovery kit is designed to allow the user to explore the many features that the STM32G4 series has to offer. This section focuses on the design of the step-down converter power stage and presents the design equations used to select the appropriate components.


The step-down converter is implemented on this discovery kit as part of a buck-boost converter. It means that there are boost switches as well as buck-switching FETs. The extract from the schematic shown in [Figure 59](#) identifies the relevant switches. The full schematic can be downloaded from [B-G474E-DPOW1](#).

Figure 59. Discovery kit schematic: buck-boost power stage

 

When using the converter in buck mode, the boost switches are not driven (the high-side switch is ON, and the low-side switch is OFF). The simplified circuit shown in [Figure 60](#) can be used to describe the power stage.

Figure 60. Step-down converter simplified power stage

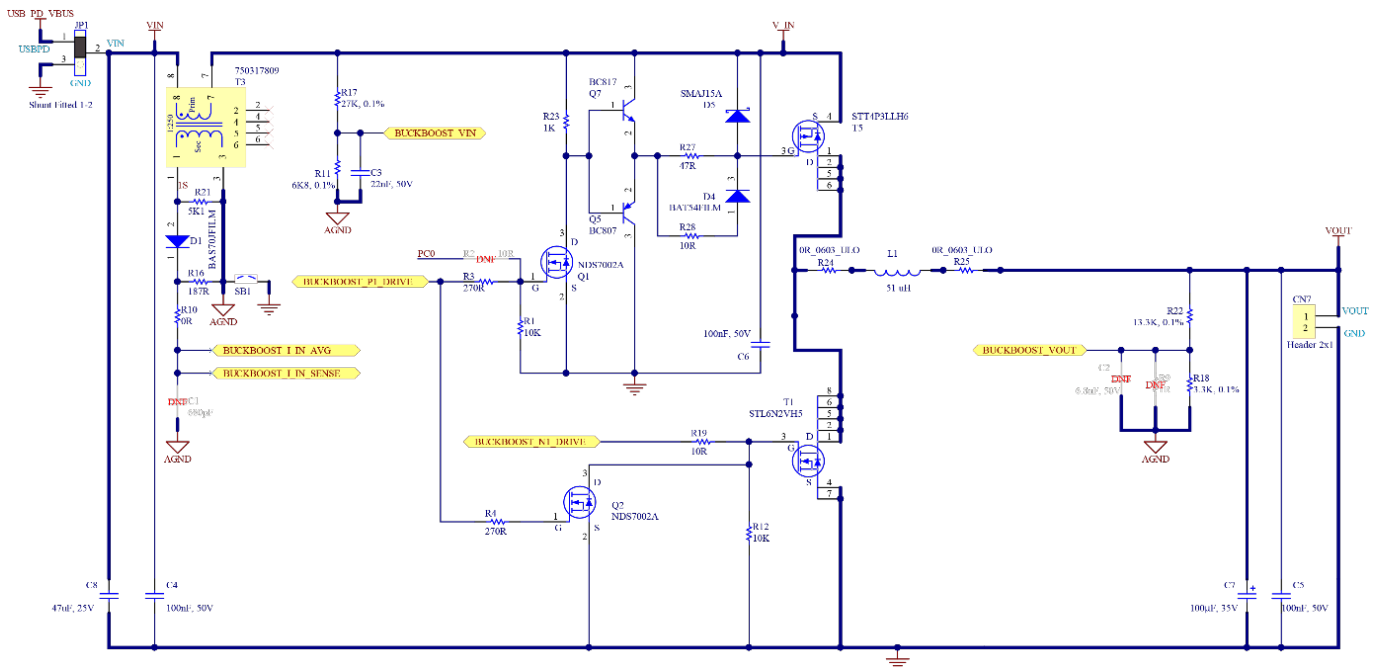

There are some constraints on the choice of the power stage components as this power stage is used for both buck and boost applications. In this design example, the buck specification given in Table 7 is considered. The power stage can also be designed using the ST-WDS power-supply design tool from Biricha. However, the equations for selecting the power inductor and filter capacitor are presented here for completeness.

Table 7. Power stage parameters

Specification	Value
Input voltage	5 V
Output voltage	3.3 V
Output current (I_O)	0.2 A
Ripple current ($\Delta I_L\%$)	50%
Output voltage ripple	1% peak-to-peak
Switching frequency	200 kHz

First, the steady-state duty cycle is calculated using (42). This does not include any of the parasitics.

$$D = \frac{V_{OUT}}{V_{IN}} = \frac{3.3V}{5V} = 66\% \quad (42)$$

7.1.1 Power inductor

The power stage inductor is sized based on the maximum allowable ripple current. It is according to the switching frequency given the input and output voltage specification. Using the standard equation for the voltage rise on an inductor given in (43) rearranged for inductance, the inductance required to meet the specification can be calculated using (44).

$$V = L \cdot \frac{dI}{dt} \quad (43)$$

$$L_0 = \frac{D \cdot T_S \cdot (V_{IN} - V_{OUT})}{\Delta I_L\% \cdot I_O} \quad (44)$$

Where T_S is the switching period, therefore:

$$L_0 = \frac{66\% \cdot 5 \mu s \cdot (5V - 3.3V)}{50\% \cdot 0.2A} = 56 \mu H \quad (45)$$

The REDEXPERT online tool from Würth Elektronik can be used to identify a suitable inductor. For this power stage, a 51 μH inductor is selected.

7.1.2 Output filter capacitor

The output filter capacitor is sized based on either the output voltage ripple requirement, or the transient load step requirement, whichever requires the larger value of capacitance. The majority of the voltage ripple at the switching frequency on the output voltage of the step-down converter is due to the voltage drop across the parasitic equivalent series resistance (ESR) of the electrolytic capacitor used in the output filter. The maximum value of the ESR can be calculated given the voltage ripple requirement and the known current ripple.

$$R_{ESR(max)} = \frac{V_{RIPPLE}}{\Delta I_L} \quad (46)$$

$$R_{ESR(max)} = \frac{V_{OUT} \cdot V_{RIPPLE}\% \cdot L_0}{D \cdot T_S \cdot (V_{IN} - V_{OUT})} \quad (47)$$

$$R_{ESR(max)} = \frac{3.3V \cdot 1\% \cdot 51 \mu H}{66\% \cdot 5 \mu s \cdot (5V - 3.3V)} = 0.33 \Omega \quad (48)$$

For a given series of electrolytic capacitors, the product of the capacitance and ESR is relatively constant. Therefore, given the maximum ESR value calculated previously, the required capacitance can be calculated. For the WCAP-ASLL aluminum electrolytic capacitors from Würth Elektronik, this constant is around 1.7×10^{-5} , therefore the capacitance can be calculated in (49).

$$C_{0(min)} = \frac{1.7 \cdot 10^{-5}}{R_{ESR(max)}} \quad (49)$$

$$C_{0(min)} = \frac{1.7 \cdot 10^{-5}}{0.33} = 51 \mu F \quad (50)$$

As this is the minimum value of output capacitance, a capacitor with 100 μF is selected.

7.2 PCB layout


The layout of the step-down converter is shown in Figure 61. In this figure, various key components of the step-down converter are identified. When laying out the step-down converter PCB, it is important to consider good PCB design practices. For example, loops with high di/dt must be minimized. Although this is a very low-power design, switching noise can still couple onto critical traces such as those routed to the ADC.

In this design, resistors R18 and R22 (towards the lower right-hand side of the step-down converter) make the resistive divider that scales the output voltage of the step-down converter before it is fed to the ADC. There may be an antialiasing filter on the ADC input to remove frequencies above the Nyquist frequency. This can be formed by placing a capacitor in parallel with R18. On this PCB, there is a footprint for this C2. However, no capacitor is placed. A potential improvement may be to add this capacitor. This may also help reduce any high-frequency switching noise that can be picked up by this trace.

The ADC pin for this output voltage feedback is PA3 that is a short distance away from this divider with no high dv/dt traces crossing this trace and a full unbroken ground plane for the return current, therefore, the signal may already be clean.

In Figure 61 the current path of the step-down converter is shown as a series of colored arrows. The fuchsia arrow indicates the current through the current sense transformer (not used for voltage mode) and high-side MOSFET. During the off-time of the high-side switch, the current flows through the low-side MOSFET, which is indicated by a blue arrow. The output filter inductor and capacitor are in the output current path highlighted by the green arrows.

Figure 61. Hardware layout of the power stage

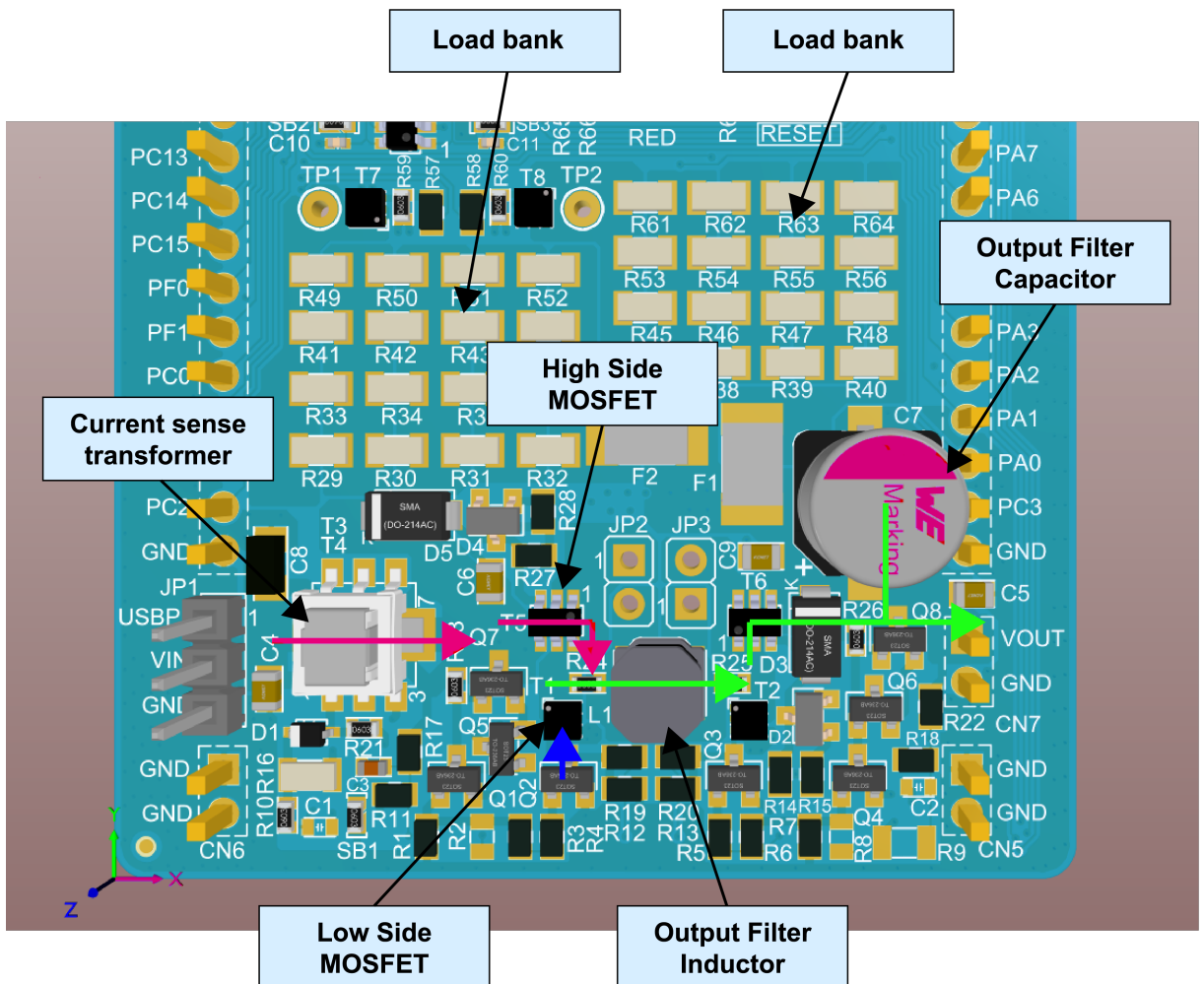

8 Getting started

8.1 Overall usage

The STM32 MCU embedded in the discovery kit comes preflashed with example software. This example software exercises the other functions of the discovery kit such as control of the RGB LED. To run the step-down converter, the user must first compile the project associated with this application note and flash the MCU.

The following dependencies are required to do this:

- PC with Windows® 7 or later
- STM32 compatible IDE, such as STM32CubeIDE, IAR Embedded Workbench®, or Keil® µVision
- STM32CubeMX (from v6.9.2) together with STM32Cube firmware library for G4 (from v1.2.0) installed

To get started simply:

1. Connect the micro-USB cable from the PC to CN3 on the discovery kit.
2. Apply power via the USB Type-C® and connect this to CN2 on the discovery kit.
3. Ensure that the jumper JP1 is in the USB PD-VIN position.

8.2 Loading the project

This voltage mode buck example project, as well as the associated ST-WDS design files, are available from the Biricha website:

www.biricha.com/ST-Discovery-Kit

Opening the Project


1. Open STM32CubeMX by clicking on the icon shown in [Figure 62](#) (note that the icon and the path may differ slightly).

Figure 62. Example.ico




2. Generate the project by clicking the `GENERATE CODE` button within STM32CubeMX.

Figure 63. Code generation

 


3. This generates the project for the selected IDE. In this case, it is an IAR Systems® project.
4. When prompted with the dialog box, open the project by clicking `Open Project`.

Figure 64. Project opening

 


5. Depending on the IAR Embedded Workbench® used version, the default debugger may need to be changed to `STLINK-V3`. Right-click on the project name and select `Options`.

Figure 65. Example options

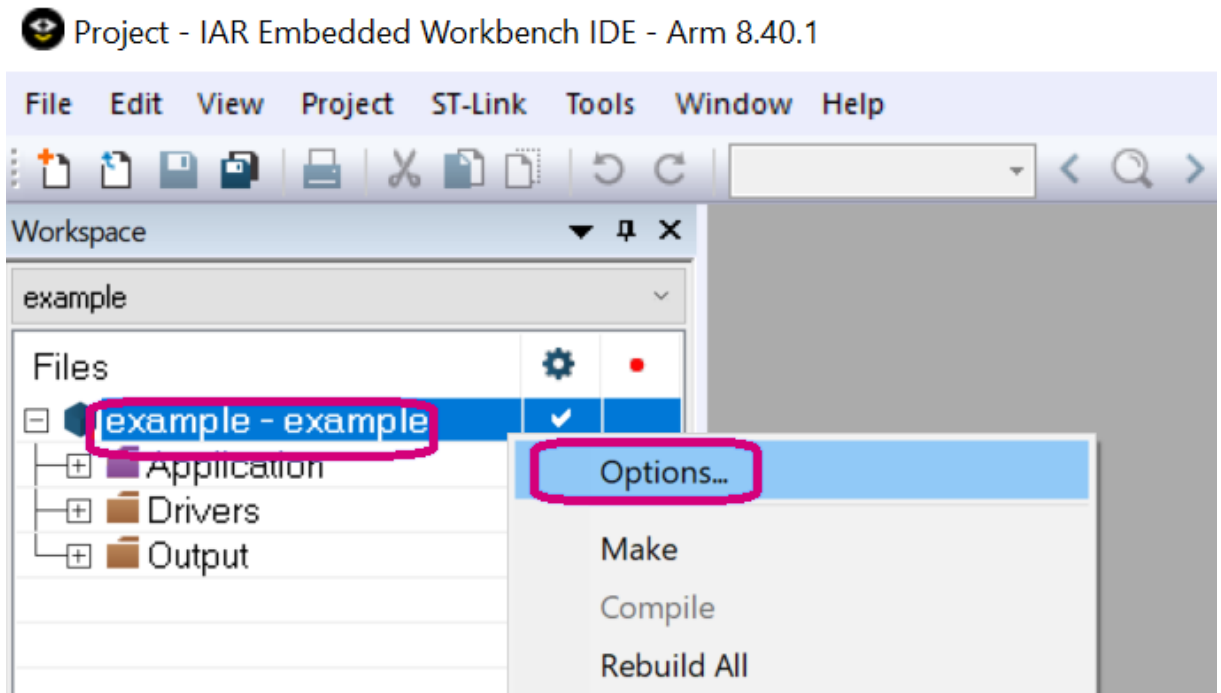


Then select `ST-LINK` and choose `ST-LINK/V3`. Click `OK` to finish.

Figure 66. ST-LINK version selection

 


6. Inside the IAR Systems® IDE click the Download and Debug icon that compiles and downloads the code to the MCU.

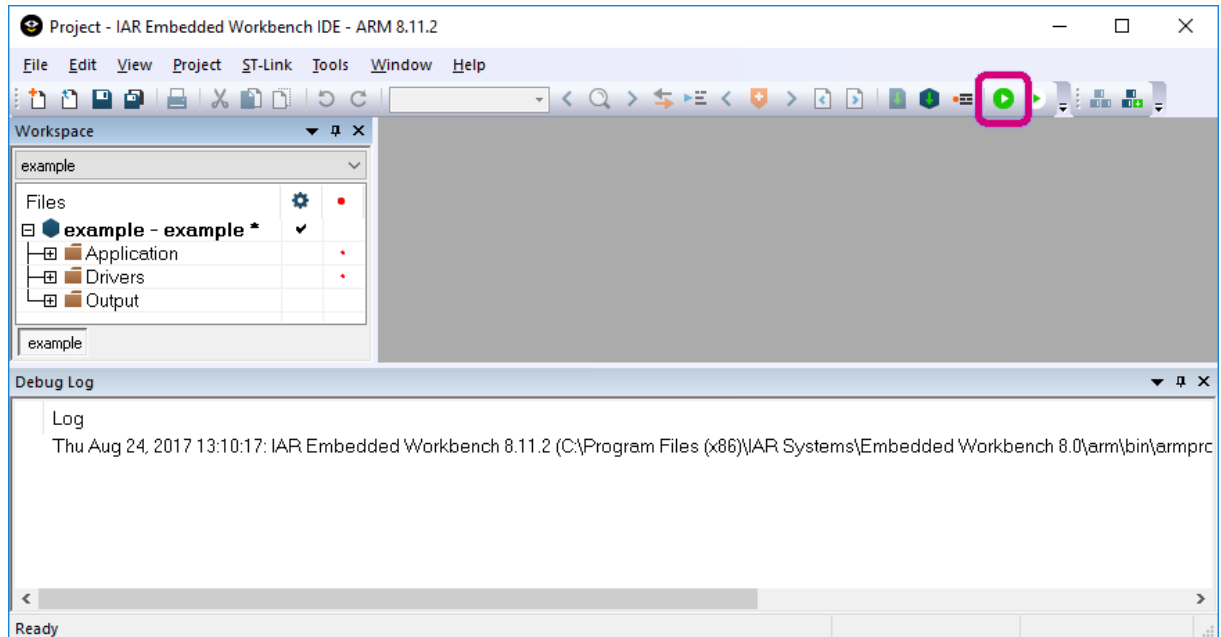Figure 67. Code compilation and downloading


7. G4 IntroPack example, in the application, User folder, the three generated C-files are:
 - a. main.c: Initialization code
 - b. stm32g4xx_hal_msp.c: MCU support package initialization
 - c. stm32g4xx_it.c: Interrupt handlers for ISRs
8. D-Power pack example, in the application, User folder, the generated C-files are:
 - a. app_X-CUBE-DPower.c: Application program body.
 - b. DCDC_Control_Layer.c: Hardware control function body.
 - c. DCDC_Fault_Processing.c: DC/DC fault management.
 - d. DCDC_Globals.c: Global variables for the application.
 - e. DCDC_IRQ_Handlers.c: Interrupt service routines.
 - f. DCDC_PWMnCurrVoltFdbk.c: Functions to drive PWM signals accordingly to existing features.
 - g. DPC_STM32_Interface.c: Source file for the library wrapper.
 - h. main.c: Main program body
 - i. stm32g4xx_hal_msp.c: MSP initialization and deinitialization codes.
 - j. stm32g4xx_it.c: Interrupt service routines.
9. The code is now ready to run. The IDE moves the program counter to the `int main(void)` function.

Figure 68. Program counter set for running

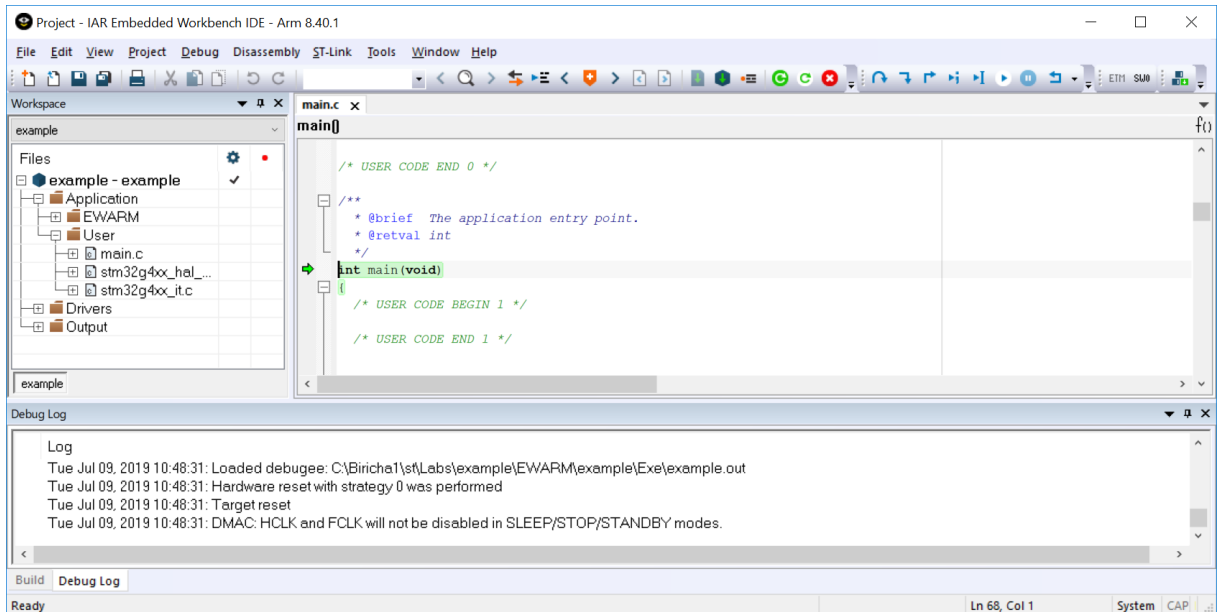

10. The buttons along the top menu bar have the functions described below. Click the Go button to run the code.

Figure 69. Top menu buttons



Go



Break



Stop debugging



Reset

- Go: this runs the code
- Break: this halts the code
- Stop debugging: this terminates the debug session
- Reset: this resets the code to the beginning and restarts

11. Click on Stop Debugging to end the debug session.

12. The firmware is downloaded into the microcontroller flash memory and as such, IAR Systems® can now be closed if the debugging features are not being closed. The same program restarts each time power is applied to the discovery kit as it is running from the MCU flash memory.

13. Close IAR Systems® to stop the debugger. If IAR Systems® asks to Terminate the debug session, click OK.

8.3 Onboard load


The step-down converter on the discovery kit includes two onboard load banks. Figure 61 shows the two load banks and the position of two test pins that indicate whether the load bank is enabled (test pins are not populated). When TP1 is pulled LOW, load bank 1 is ON. When TP2 is pulled LOW, load bank 2 is ON. The load banks have total resistance and, given the 3.3 V output voltage, the power consumption is shown in Table 8.

Table 8. Onboard load steps

Load (%)	Load (Ω)	Iout (A)	Pout (W)	LED status
0%				
Load 1 OFF	$\infty \Omega$	0 A	0 W	All OFF
Load 2 OFF				
50%				
Load 1 ON	33 Ω	0.1 A	0.33 W	Green
Load 2 OFF				
100%				
Load 1 ON	16.5 Ω	0.2 A	0.66 W	Green and orange
Load 2 ON				

Note that the PTC (F1, F2) adds approximately 1 Ω of resistance in series with each load bank. The load banks can be controlled by the MCU through means of toggling an output pin, which is connected to a MOSFET. The MOSFET switches the resistive load bank in and out of the circuit as shown in Figure 70.

Figure 70. Onboard load banks controlled via MOSFETs

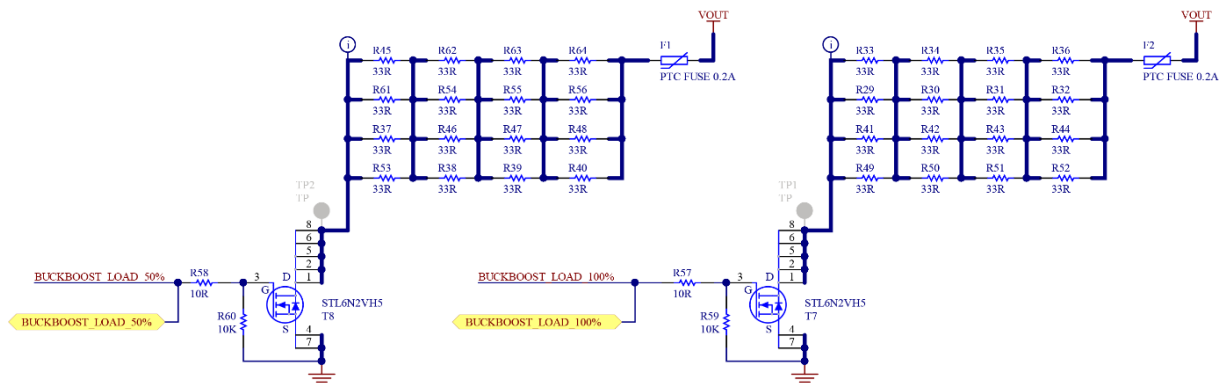

Furthermore, the user can control the switching of the load using the joystick onboard the discovery kit. The operation of the onboard load banks can be controlled as follows:

- Left: Manual adjustment of the load
 - Up: Increase the load
 - Down: Decrease the load
- Right: Automatic load switching (transient mode)

The automatic load switching, or transient mode, is used later in the application note. It is used to test the transient response of the step-down converter and the control loop regulating the output voltage. The status of the load bank during the transient is indicated by the LEDs on the discovery kit board. If load bank 1 is enabled, the green LED lights up. If load bank 2 is enabled, the orange LED also lights up.

8.4 Source files

The downloadable package for this application note consists of the following files:

STM32CubeMX project files:

- `Buck_VoltageMode_HW.ioc`
 - This file contains all configuration data for STM32CubeMX setting up the pins and peripherals used. The closed-loop is mostly hardware, thanks to the FMAC usage for the controller computation.
- `Buck_VoltageMode_SW.ioc`
 - This file contains all configuration data for STM32CubeMX setting up the pins and peripherals used. The closed-loop is using the MCU for the controller computation.
- `Buck_VoltageMode_SW_CCM_SRAM.ioc`
 - This file contains all configuration data for STM32CubeMX setting up the pins and peripherals used. The closed-loop is using the MCU for the controller computation, which is located in CCM-RAM for the best efficiency.

Source codes G4 intro pack example:

- `main.c`
 - This file provides the `main.c` function and associates support functions for this application to control the hardware on the board
- `stm32g4xx_hal_msp.c`
 - Microcontroller support package initialization functions
- `stm32g4xx_it.c`
 - It interrupts service routines.
- `system_stm32g4xx.c`
 - It provides the `SystemInit()` initialization functions for this MCU configuring the system clock.

Source codes D-Power pack example:

- `app_X-CUBE-DPower.c`
 - This file provides functions for this application to control the hardware on the board.
- `DCDC_Control_Layer.c`
 - Hardware control functions body
- `DCDC_Fault_Processing.c`
 - DC/DC fault management
- `DCDC_Globals.c`
 - Global variables for the application
- `DCDC_IRQ_Handlers.c`
 - Interrupt Service routines
- `DCDC_PWMnCurrVoltFdbk.c`
 - Functions to drive PWM signals accordingly to existing features
- `DPC_STM32_Interface.c`
 - Source file for the library wrapper
- `main.c`
 - Main program body
- `stm32g4xx_hal_msp.c`
 - MSP initialization and deinitialization codes
- `stm32g4xx_it.c`
 - Interrupt service routines

ST-WDS from Biricha files:

- Buck_VoltageMode_xxx.wds
 - To match the STM32CubeMX project file, the ST-WDS configuration file enables the user to load the step-down converter design in the PSU design tool from Biricha. The user can then modify the control loop parameters and obtain the updated controller coefficients.

Omicron Lab Bode Analyzer Suite files:

- Buck_VoltageMode_xxx.bode3
 - To match the STM32CubeMX project file, the Bode Analyzer Suite configuration file configures the tool for loop measurement of the step-down converter. The file also contains the previously measured traces stored in memory locations.

8.5 Open-loop operation

Before exercising the step-down converter under closed-loop control, it is prudent to check the switching waveforms and dead time are correctly functioning. This check can be performed under the open-loop operation of the step-down converter. This means that the controller is taken out of the loop and the buck switches are driven with a fixed duty cycle.

The example software is written such that when a compiler directive is defined, the FMAC interrupt is not enabled, and the HRTIM module is set up with a fixed duty cycle.

To run the step-down converter under open-loop, locate and uncomment the line of code `#define RUN_OPEN_LOOP`. Within the `main()` function, the function call to set up the compare unit with a fixed duty cycle is now called rather than the function, to enable the FMAC interrupt.

To check the HRTIM output waveforms, connect the oscilloscope probes to the following pins:

- PB12 - BUCKBOOST_P1_DRIVE – High-side buck MOSFET
- PB13 - BUCKBOOST_N1_DRIVE – Low-side buck MOSFET

These signals must not be HIGH at the same time as this may lead to a potential shoot-through event. During the configuration of STM32CubeMX, dead time is inserted between the two channels to ensure that the switches are never ON at the same time. The amount of dead time can be measured using the scope and compared to the value set earlier in this application note.

The dead-time ticks f_{DTG} are generated from f_{HRTIM} and a prescaler. For the configuration discussed earlier in this application note:

- $f_{DTG} = f_{HRTIM} * 8$, and because $f_{HRTIM} = 170$ MHz:
- $f_{DTG} = 170$ MHz * 8 = 1360 MHz, therefore:
 - 1 dead-time tick = 0.735 ns

Earlier, the dead time is configured to have:

- Rising value = 75 ticks = 55 ns
- Falling value = 200 ticks = 147 ns

Therefore, between the falling edge of PB13 and the rising edge of PB12, there are 55 ns of dead time as measured in Figure 71. Between the falling edge of PB12 and the rising edge of PB13, there are 147 ns of dead time as measured in Figure 72.

Figure 71. Rising edge dead-time, Ch1: high-side FET, Ch2: low-side FET, dead-time measured as 54 ns


 


Figure 72. Falling edge dead-time, Ch1: high-side FET, Ch2: low-side FET, dead-time measured as 147 ns

 

The output voltage of the step-down converter is currently not regulated as the FMAC ISR is not running. Instead, a fixed duty cycle is providing some output voltage by driving the switches in a complementary manner. With none of the loads enabled the output voltage may be around 1.5 V. If the load is added by moving the joystick left or right, then the output voltage also changes.

8.6 Closed-loop control

8.6.1 Load regulation

The converter is initially tested under open-loop conditions with no control over the output voltage. The next step is to close the control loop to regulate the output voltage.

To run the step-down converter under closed-loop control, locate and comment on the line of code `#define RUN_OPEN_LOOP` by changing it to `// #define RUN_OPEN_LOOP`. Rebuild the project then download and debug the code.

With the converter running, the digital FMAC compensator now regulates any changes in the load on the converter. The load regulation can be tested by varying the onboard load using the joystick and measuring any change in the output voltage.

Table 9. Closed-loop load regulation

Load	Iout	Vout
0% Load 1 OFF Load 2 OFF	0 A	3.3 V
50% Load 1 ON Load 2 OFF	0.1 A	
100% Load 1 ON Load 2 ON	0.2 A	

8.6.2 Transient response


The onboard load allows the user to perform transient response tests on the closed-loop digital power supply to assess the performance of the controller. The transient response test is a useful method of determining if the implemented controller is stable, the speed of the response, and whether there is a sufficient phase margin in the system.

The converter's transient response can be measured using an oscilloscope. To measure the transient response, set up the oscilloscope as follows:

- Channel 1 -> Connect to header marked V_{out}
- Channel 2 -> Put the probe tip in the hole marked TP1
- Set coupling on Channel 1 to AC and set the volts per division to 20 mV
- Set the horizontal scale, in seconds per division time base, to 100 μ s
- From the Trigger menu: Set the trigger to the falling edge of Channel 2 and set the Mode to Normal.

Set the load to the transient mode by pressing the Up arrow on the blue joystick. The orange load LEDs must now flash with half a second interval. When the green LED is ON, the load is set to 50%. When both LEDs are ON, the load is set to 100%. The undershoot and the settling time can then be observed on the oscilloscope during the 50% to 100% load transient. Using the example project provided with this Discovery kit, the converter may have a well-tuned controlled loop as shown in Figure 73.

Figure 73. Output voltage (Ch3) transient from load change 50% to 100% (Ch1)

 


Note: For this figure, output voltage undershoot is 30 mV and settling time is 150 μ s.

Figure 73 shows the transient response of the closed-loop digital step-down converter for a 50% to 100% step load transient with a settling time of fewer than 150 μ s, and an undershoot of less than 40 mV with no ringing.

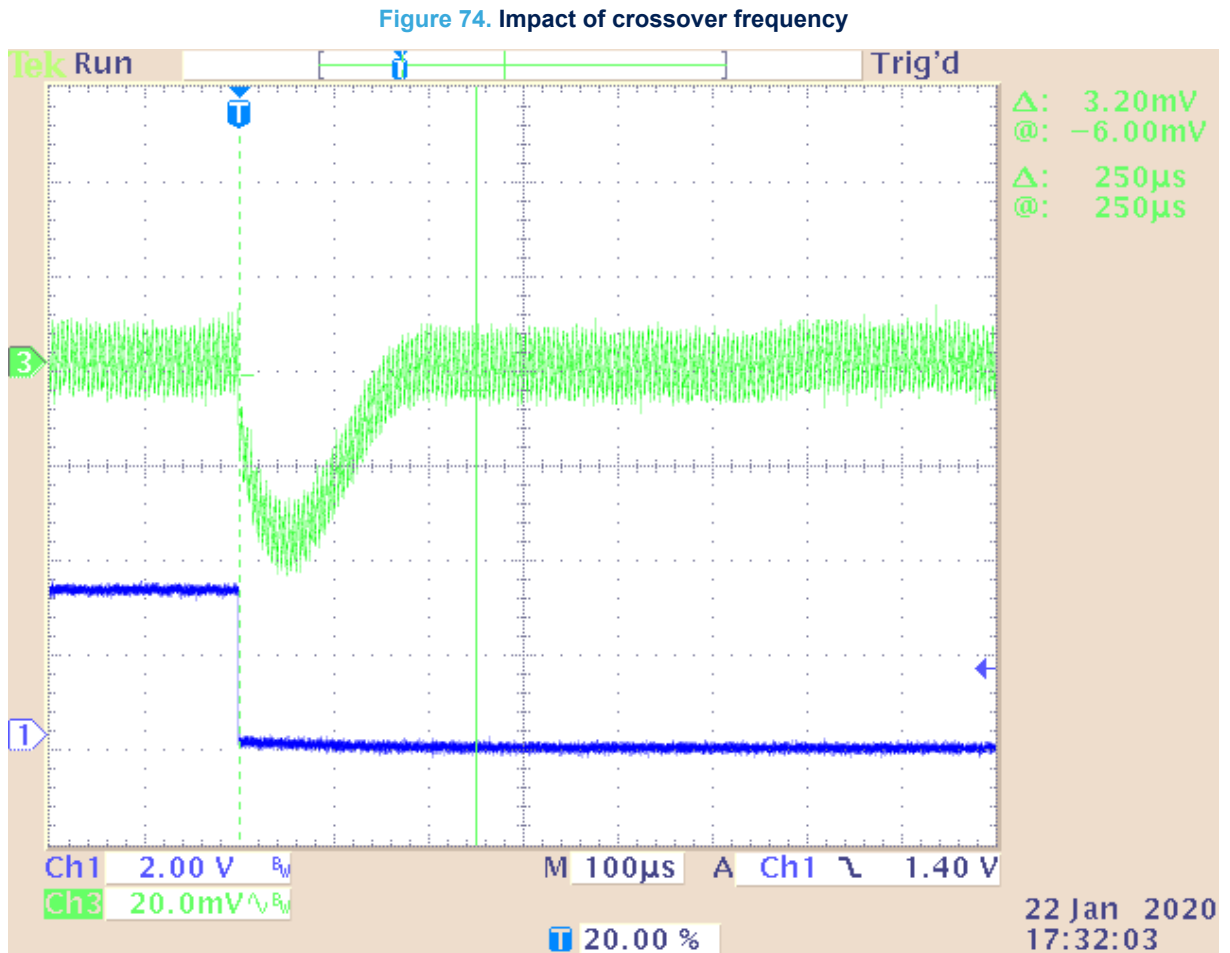8.6.3 Impact of crossover frequency on the transient response

The transient response of the converter in Figure 73 indicates a stable and well-designed controller. This is using the controller which is described in detail in Section 4 of this application note. The controller is designed to have a crossover frequency of 8 kHz and a phase margin of 50°. The choice of crossover frequency and phase margin in the frequency domain affects the transient response as seen in the time domain.

For example, if ST-WDS is used to redesign the controller using a lower crossover frequency, then it may result in a slower transient response and as shown in Figure 74. *Impact of crossover frequency*. In this plot, the controller is redesigned with a crossover frequency of 4 kHz, half that of the previous controller.




Note: For this figure, output voltage (Ch3) transient from load change 50% to 100% (Ch1) with loop crossover of 4 kHz, output voltage undershoot is 40 mV and settling time is 250 μ s.

It follows therefore that if the crossover frequency is increased the transient response speeds up also and undershoot reduces. However, there is an upper limit to the crossover frequency as at higher frequencies the phase erosion becomes more significant and reduces the loop phase margin. The issue of phase erosion in the discrete-time system is discussed in detail in Section 8.6.4: *Impact of phase margin on the transient response*.

8.6.4 Impact of phase margin on the transient response

The phase margin is a measure of the relative stability of the control loop. The lower the phase margin the more oscillatory the transient response in the time domain. ST-WDS is used again to redesign the controller using a lower phase margin. The new controller is designed with the same crossover as initially, 8 kHz, however a phase margin of 30°. The resulting controller coefficients can be pasted into the code which is then recompiled and downloaded onto the MCU. The transient response is given in Figure 75 for the system with a phase margin of 30°.

Figure 75. Impact of phase margin on the transient response

 

Note: For this figure, output voltage (Ch3) transient from load change 50 to 100% (Ch1) with loop crossover of 8 kHz and a designed phase margin of 30°, output voltage undershoot is 30 mV and settling time is 200 µs.

In Figure 75 there are several oscillations in the transient response as it recovers from the transient back to its steady state. The initial recovery time is shorter than when the phase margin is 50°, however, the output voltage overshoots from the desired setpoint, and the net result is that there are oscillations during the recovery. If the phase margin is reduced further, the oscillations take longer to decay. With a phase margin of 0°, the system may oscillate indefinitely.


8.6.5 Bode plot measurement under closed-loop control

The real-life loop response of the step-down converter can be verified through measurement using a frequency response analyzer. In this application note, the Bode 100 vector network analyzer from Omicron Lab is used to perform the measurement. The Bode 100 injects a sinusoidal signal into the feedback loop of the power supply and measures how that signal changes as it passes through the controller and the plant power stage.


A small modification is required to the discovery kit to measure the loop. The feedback path of the output voltage must be broken and an injection resistor needs to be inserted. The injection transformer is then connected across this resistor. The injection transformer superimposes the sinusoidal signal from the Bode 100 onto the feedback voltage, which is being used to close the loop.

The schematic for this modification is shown in [Figure 76](#). The measurement probes are then connected as follows: CH1 (or the control measurement point) is connected to the end of the injection resistor, which is not connected to the output voltage. Then CH2 (or the output measurement point) is connected to the end of the injection resistor, which is directly connected to the output voltage. The grounds of the probes may be connected to the header marked GND closest to this. Note that JP2 and JP3 are not fitted by default on this board.

Figure 76. Connection setup for control-to-output transfer function measurement

 

A frequency sweep from 100 Hz to 100 kHz is recommended (up to half the switching frequency) with the signal injection level adjusted to give a continuous smooth measurement result without affecting the steady-state response of the loop. Once a clean continuous measurement is obtained, the `.bode3` file can be saved from within Omicron Lab's Bode Analyzer Suite and then imported into ST-WDS as shown in [Figure 77](#).

 Figure 77. Loop measurement at 100% load imported into ST-WDS


Note: *Black means the measured loop, and green means the simulated loop.*

In **Figure 77** the actual measurement of the loop (control-to-output) transfer function is plotted as the black trace. This is compared with the simulated loop plotted in green. The magnitude plot shows a good correlation between simulated and measured loop responses with a crossover frequency of 8 kHz in simulated and 7.33 kHz as measured.

The phase response is also a good match at the lower frequencies. Around the double-pole frequency of the plant (2 kHz), there is some discrepancy that is likely due to the AC resistance of the inductor that is not included in the plant model. This has some effect on the Q factor of the complex conjugate pole, and therefore the rate at which the phase transitions. The result is a higher phase margin than anticipated. If the phase margin is too high, it is possible to redesign the control loop to take into account the additional phase. However, it is also prudent to check the crossover and phase margin at different loads. This is discussed in the next section.


8.7 Waveform display in IAR Systems®

If the user has access to IAR Systems® then it is possible to use the timeline feature within this to plot variables captured using data log breakpoints. This is suitable for slow-changing variables in real-time, or fast-changing variables that are stored in a buffer and then transferred via the debugger to the IDE at a slower rate.

An example of this functionality is included in the project provided `Buck_VoltageMode_SW`. Note that this project executes the 3p3z controller called within the ADC ISR implementing a controller running on the main core rather than the FMAC. To exercise this example, open the `Buck_VoltageMode_SW.ioc` file within the folder and click **GENERATE CODE**. Open IAR Systems®, locate, and uncomment the line of code `#define PLOT_WAVEFORM`, build, and run the code. Note that there is now an additional function within the `SysTick_Handler` ISR located towards the top of the `main.c` file:

```
WaveFormDisplay(&Vout, &CompareReg);
```

Double-click on `Vout` and then right-click on the highlighted text and select **Set Data Log Breakpoint for 'Vout'**. Repeat this process for `CompareReg`.

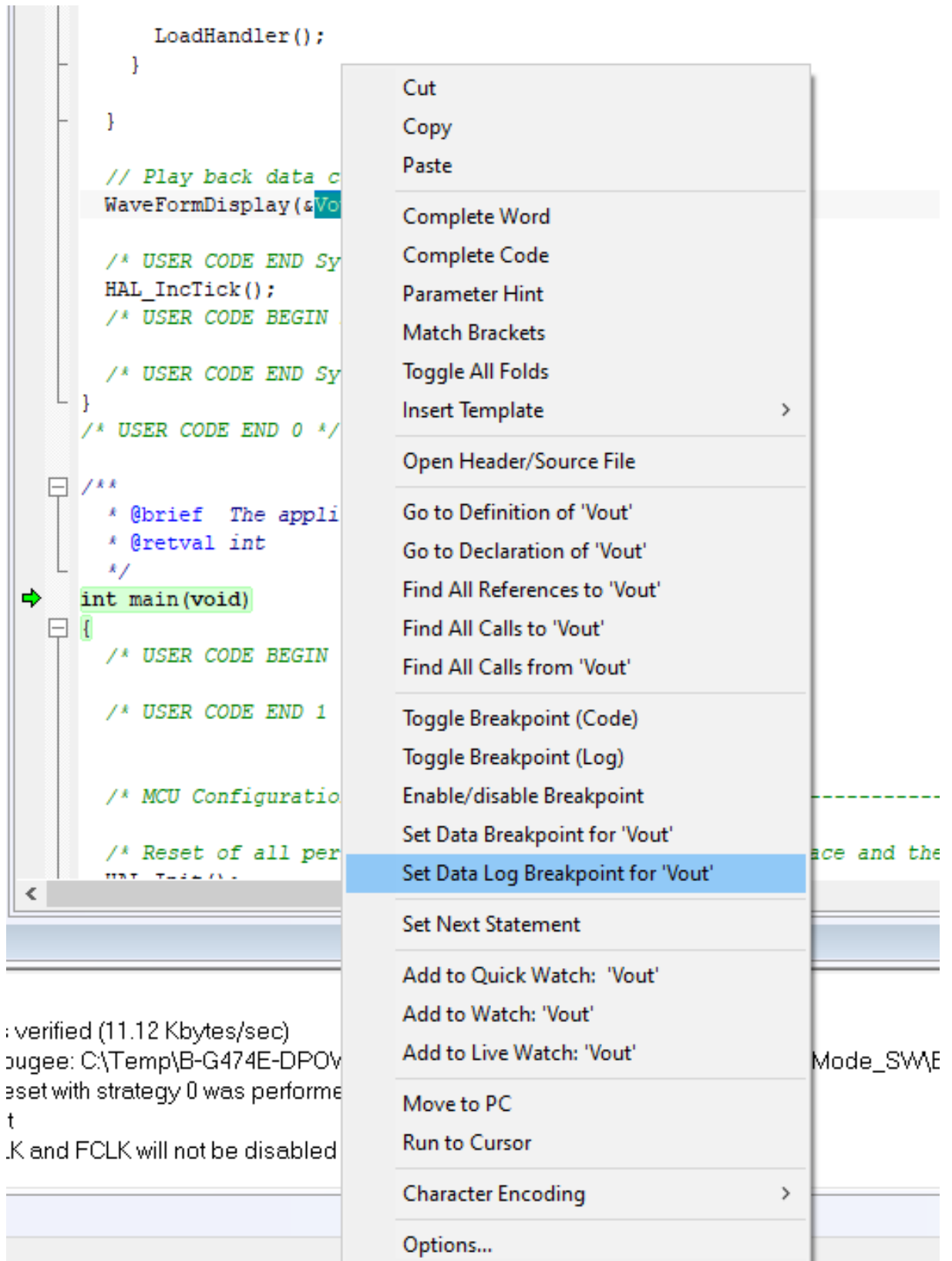Figure 78. Add the data log breakpoint to capture the variable each time it is updated


This forces the debugger to record the value of these variables each time they are updated. For this reason, the update of these variables is performed in a slower function within the `SysTick_Handler` so as not to overload the debugger.


The data is captured within the ADC ISR located in the `stm32g4xx_it.c` file. The code snippet below shows the data being passed to the `WaveFormRecord()` function each time the ISR is called.

```
if (Waveform.m_State == WAVEFORM_RECORD)
{
    WaveFormRecord(VoltageSensing, Demo.CtrlFloat.m_Out);
}
```

The waveform structure state is changed to `WAVEFORM_RECORD` every time the user presses the load increment/decrement button on the discovery kit. This can be seen in the `HAL_GPIO_EXTI_Callback()` GPIO interrupt function, which is included in `STM32G474RE_Discovery.c`. This function calls `WaveFormTrigger()` which in turn changes the state to begin recording the waveform during the ADC ISR.

From the ST-Link menu on the toolbar click on `Timeline` as shown in Figure 79.


Figure 79. Enabling timeline view

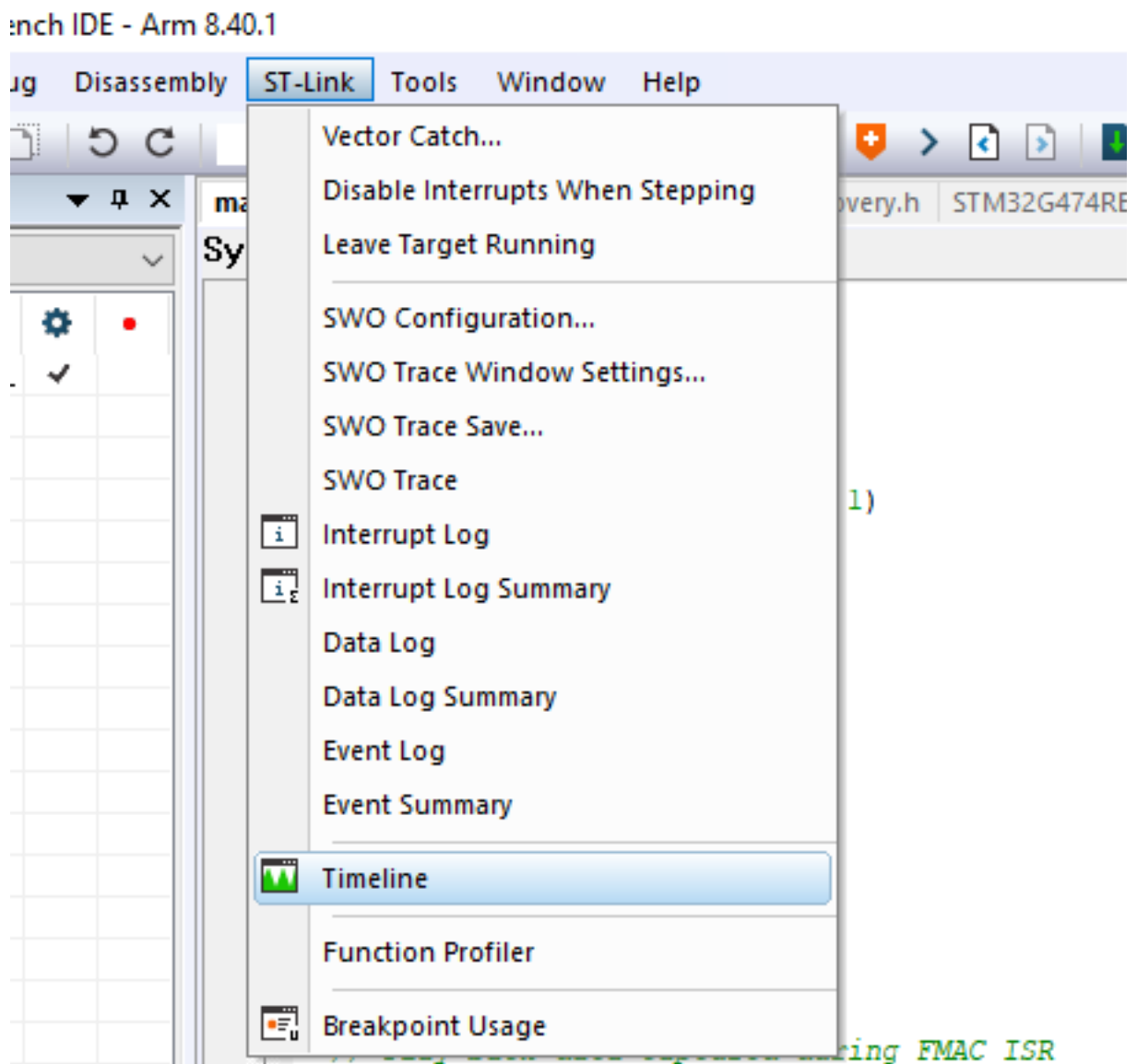

This shows the timeline pane in the IAR Systems® workspace. If the graph pane is not visible, the user may need to right-click in the blue area and click `Enable`.

Right-click on the `Vout` blue graph window and untick `Hexadecimal`, set `Size` -> `Large`, and `Zoom` -> `100 ms`. Repeat this process for `CompareReg`. The graph windows must look like [Figure 80](#).

Figure 80. Timeline pane

 

Note:

2For this figure, the timeline view requires some manual adjustment of the scale to view the information presented.

If the waveforms are invisible, try to right-click on the graph window, go to `Navigate` -> `End`, and then use the horizontal scroll bar to scroll the view to the left until the window is filled.

As mentioned above, the data captured by the ADC is replayed by the function `WaveFormDisplay` at a much slower rate to allow the debugger to capture the data via the data log breakpoint. Therefore, the horizontal time axis is now much slower than the sampled signal.

It is now possible to zoom in on the output voltage to view the transients in more detail by changing the scale. Right-click on the `Vout` graph pane and click on `Viewing Range`. In the dialog box, select `Custom Limits` and enter limit values to fill the entire vertical axis with data from the output voltage. This may take several attempts to find the appropriate values. In [Figure 81](#) the values 765 and 785 are used for the output voltage and 15000 and 20000 are used for the compare register. The graph window must now look like [Figure 81](#).

Figure 81. Timeline view with an adjusted scale



8.8 Step-down converter usage with the X-CUBE-DPower pack

Refer to the X-CUBE-DPower user manual (UM3102) available at www.st.com to install the pack and start up with the wanted converter.

8.8.1 Configure the converter parameters using the GUI

As shown in Figure 82, they are many user parameters that are now available when using X-CUBE-DPower.

Figure 82. X-CUBE-DPower – GUI parameters for the step-down converter

The screenshot displays the X-CUBE-DPower GUI configuration interface. The main window is titled 'STMicroelectronics.X-CUBE-DPower.1.1.0 Mode and Configuration'. It features a sidebar on the left with a search bar and a list of categories including Security, Computing, and Middleware and Software Packs. The main area is divided into 'Mode' and 'Configuration' sections. The 'Mode' section has three checked options: 'Library Digital Power Converter', 'DC-DC converter in CCM', and 'Device DSMPS'. The 'Configuration' section includes a 'Reset Configuration' button and a 'Topology parameters' section highlighted with a pink box. This section contains a table of parameters with a search bar and an 'Info button'. The table lists parameters such as Input Voltage (Vdc), Output Voltage (Vdc), Voltage Control Loop Frequency (Hz), Current Control Loop Frequency (Hz), PWM switching frequency (Hz), HRTIM Clock (Hz), HRTIM prescaler ratio, TIMx Clock (Hz), Dead Time Rising Edge (ns), and Dead Time Falling Edge (ns). The 'PWM switching frequency (Hz)' parameter is highlighted in blue. Below the table, a 'Parameter information' section is highlighted with a pink box, providing details for the 'PWM switching frequency (Hz)' parameter, including its description: 'PWM signals frequency (Hz)'.

Parameter	Value
Input Voltage (Vdc)	5.0
Output Voltage (Vdc)	3.3
Voltage Control Loop Frequency (Hz)	50000
Current Control Loop Frequency (Hz)	70000
PWM switching frequency (Hz)	200000
HRTIM Clock (Hz)	544000000
HRTIM prescaler ratio	1
TIMx Clock (Hz)	170000000
Dead Time Rising Edge (ns)	75
Dead Time Falling Edge (ns)	200

Parameter information

PWM switching frequency (Hz)
 PWM switching frequency (Hz)
Parameter Description:
 PWM signals frequency (Hz)

The parameters are described using either the information button then selecting the parameter, or clicking directly on the parameter.

8.8.2 Command the converter using board UI

To interact with the user, the B-G474E-DPOW1 board implements one joystick selection and four colored LED indicators.

The step-down converter, generated from X-CUBE-DPower, redefines the user interaction as presented in this paragraph. Note that it behaves differently from the standard G4 IntroPack example.

The joystick is useful to command the converter as follows:

- Up button: Activate automatic load transients toggling
- Down button: Deactivate automatic load transients toggling
- Right button: Increase the total of activated load resistors
- Left button: Decrease the total of activated load resistors
- Center button: Unused

LEDs inform about the converter status as follows:

- Green: The system is running. Highlighting details are given in the state machine diagram [Figure 83](#).
- Red: An error or a fault is detected. Highlighting details are given in the state machine diagram [Figure 83](#).
- Orange: While not meaningful during automatic mode activation, it reflects only the total of activated load resistors during manual mode activation as follows:
 - OFF: No load resistors
 - 1 flash/s: 50% of load resistors
 - 2 flash/s: 100% of load resistors
- Blue: Reflect the mode activation as follow:
 - ON: Automatic mode
 - OFF: Manual mode

8.8.3 Topology dedicated files

Refer to the X-CUBE-DPower user manual (UM3102) available at www.st.com to clarify the project files architecture and usage.

Regarding the step-down converter, `app_dpowers.h` implements only the following user modalities (refer to the header file for a detailed description):


- `#define CHANGE_CTRL_TO_PID`
- `#define OVERCURRENT_PROTECTION`
- `#define OVERVOLTAGE_PROTECTION`
- `#define SHORT_CIRCUIT_PROTECTION`
- `#define OVERTEMPERATURE_PROTECTION`
- `#define DEBUG_MODE`
- `#define DEBUG_COMP_OUT`
- `#define RUN_OPEN_LOOP`
- `#define PLOT_WAVEFORM`

Note: The protections that were mentioned are not currently in effect.

8.8.4 State machine

The state machine implementation is provided in Figure 83.

Figure 83. X-CUBE-DPower – step-down converter state machine

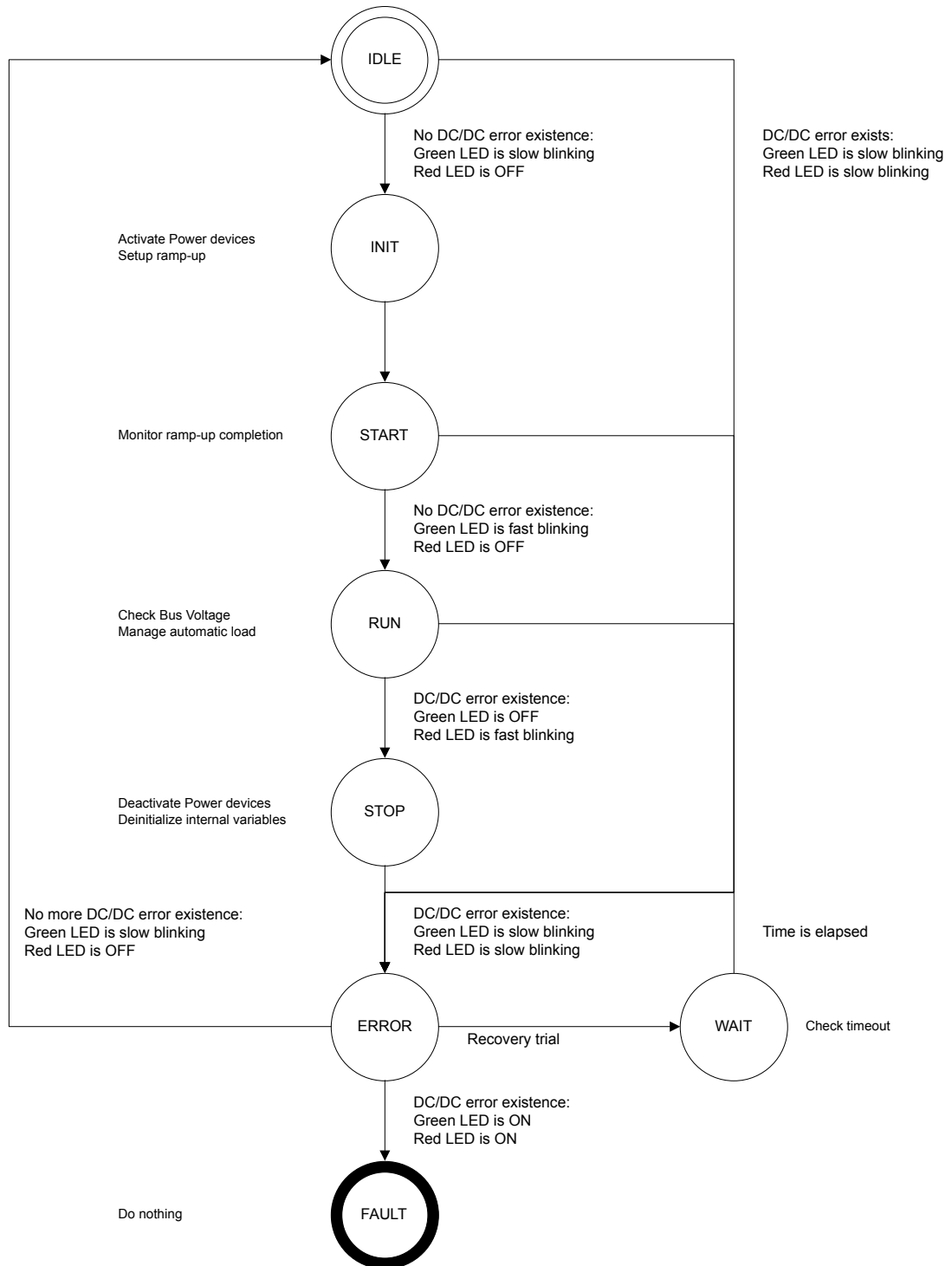

9 Measurements

This section exercises the step-down converter embedded in the discovery kit using the provided voltage mode control example, and discusses the captured measurement results.

9.1 Load regulation

The converter is now operating under closed-loop control and, as there is an integrator within the control loop, there is good load regulation. This means that the converter responds to any changes in load and regulates such that the output voltage remains constant.

This can be tested by observing the output voltage on the oscilloscope and varying the load using the joystick. The duty cycle is also monitored and this changes somewhat between the different load steps due to losses within the power stage.

Figure 84 shows the output voltage and PWM for 0% load – with the onboard load banks disabled. The oscilloscope measures the output voltage with a mean value of 3.32 V with a duty cycle of 61.2%. The load is then increased to 50% of the rated output current in Figure 85 and the output voltage remains constant at 3.32 V and the duty cycle increases to 65.55%. Finally, the load is increased to 100% of the rated output in Figure 86 and again the output voltage remains at 3.32 V and the duty cycle increases to 66.28%. This indicates that the controller is regulating the output voltage of the step-down converter given the changes in load.

Figure 84. Output voltage (Ch3) and PWM (Ch1) at 0% load

 


Figure 85. Output voltage (Ch3) and PWM (Ch1) at 50% load


 



Figure 86. Output voltage (Ch3) and PWM (Ch1) at 100% load

 

9.2 Transient response tests

As discussed in [Section 8: Getting started](#), the transient response can provide useful information about the stability of the closed-loop system. The transient response of the step-down converter can be measured by placing one oscilloscope channel on the output voltage and another oscilloscope channel on the test point associated with the onboard load being switched. The output voltage channel is AC coupled to see the deviation from the setpoint at the moment of the load transient. More details on how to measure the transient response are provided in [Section 8: Getting started](#).

Figure 87. Output voltage (Ch3) transient from load change 50% to 100% (Ch1)

 


Note: For this figure, output voltage undershoot is 30 mV and settling time is 150 μs.

Figure 87 shows the transient response for a step-change in load from 50% to 100%. The output voltage on Channel 3 deviates from the steady state by 30 mV and recovers back to the steady state within 150 μs. Importantly, there is no ringing in the recovery. This is an indication that there is a sufficient phase margin in the loop to ensure stability. A transient response with ringing is shown in [Section 8: Getting started](#).

It is prudent to check the transient response across a range of line and load conditions. In Figure 88 the transient response is shown for a step-change in load from 0% to 50%. The dynamics of the system are different at light load and therefore the response is significantly slower. In this instance, the recovery takes 420 μ s. However, the recovery still shows no sign of oscillation and therefore indicates that the system is stable.

Figure 88. Output voltage (Ch3) transient from load change 0% to 50% (Ch1)

 

Note: For this figure, output voltage undershoot = 30 mV, settling time = 420 μ s

9.3 Frequency response measurement results

The transient response can provide some information about the stability of the system and how the system responds to a large signal disturbance. However, it does not provide all of the information necessary to quantify the stability of the system. This information can be obtained by measuring the frequency response of the converter. A detailed procedure describing the measurement of the frequency response of the step-down converter is given in [Section 8: Getting started](#).

Figure 89. Measured loop response of the digital voltage mode loop at 100% load

 


Figure 89 shows the measured control-to-output loop response of the step-down converter at 100% load. The measurement of the loop is plotted as the black trace and compared with the simulated loop in green. A crossover frequency of 7.33 kHz is measured which is close to the desired crossover frequency of 8 kHz. A phase margin of 61° is achieved in the real measurement compared to 50° in the simulation. The discrepancy between the measured and simulated results is predominately due to the AC resistance of the inductor that is not included in the plant model. This has some effect on the Q factor of the complex conjugate pole and therefore the rate at which the phase transitions.

In [Figure 90](#) the loop response of the step-down converter at 50% load is measured. As expected, the overall loop response is very similar to that of the system at 100% load however there is some change in the damping of the double pole as the load changes. Therefore, the crossover frequency and phase margin change slightly. The system is still stable.

With no load, the system dynamics change considerably. The system takes longer to respond to any changes and this is observed in the transient load step test. The frequency response at 0% load is shown in Figure 91 and exhibits a much lower crossover frequency of 5.4 kHz however a higher phase margin of 92°. The system is therefore still stable as observed during the transient response test.

Figure 90. Measured loop response of the digital voltage mode loop at 50% load


 


Figure 91. Measured loop response of the digital voltage mode loop at 0% load

 


9.4 ISR plots (featuring FMAC and CPU load benefits)

The controller for this step-down converter is implemented using the FMAC module onboard the STM32G4 device. The FMAC module is a hardware module that can execute the controller in a few system clock cycles and is not using up any of the main core bandwidths. An ISR is called when the FMAC has finished the computation of the controller. To measure the timings, a GPIO pin is set HIGH upon entering the FMAC ISR.


In [Figure 92](#) the time from the ADC trigger to the FMAC ISR interrupt is measured. The ADC is triggered when the compare unit 3 match occurs shortly after the rising edge of the PWM signal, Channel 1, in [Figure 92](#). When the ADC is triggered, the sample of the output voltage is taken, converted, and then copied to the FMAC using the DMA controller. After the FMAC has finished execution the ISR is triggered. The GPIO pin is then set HIGH as the MCU enters the ISR as shown on Channel 4 in [Figure 92](#). The total time for this sample, conversion, and calculation process is measured as 750 ns.

Figure 92. PWM (Ch1) and FMAC ISR duration (Ch2)

 

The FMAC ISR is solely used for bounds checking of the controller output to a minimum and maximum value and then the update of the counter compare module register to set the new value of the duty cycle. Therefore, this is a very brief ISR containing only a few lines of code. The duration of the ISR is measured in [Figure 93](#) as 888 ns. Although this timing measurement does not include the time required to push and pop the stack before and after the ISR, there is still clearly ample bandwidth remaining on the MCU to run other controllers or implement other functions.

Figure 93. PWM (Ch1) and FMAC ISR duration (Ch2)

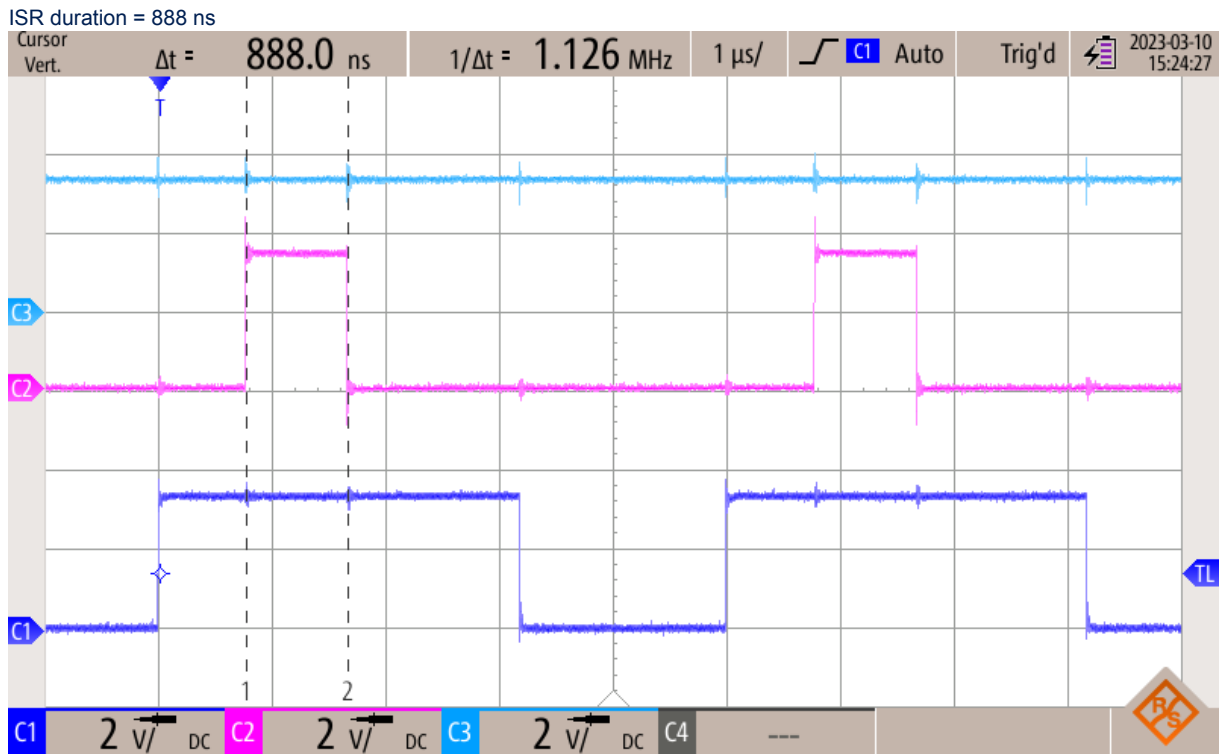

For STM32 MCUs without the FMAC module, the controller can be executed on the main core within the ADC ISR. The process for execution is then as follows. The ADC is triggered at the same point in time, the ADC samples the output voltage and completes the conversion. Now, an interrupt is triggered which is serviced by the main core. The time from the ADC trigger to entering the interrupt can be measured from [Figure 94](#) as a GPIO is again set HIGH as the ISR is entered. This time is measured as 600 ns.

Within the ADC ISR, the 3p3z controller is executed. This means that the duration of the ISR is significantly longer than the FMAC ISR. The ADC ISR containing the 3p3z controller executes within 1.850 ns as measured in Figure 95. Therefore, the total time from the ADC trigger to the PWM update is 2.450 μ s. This compares to 1.638 ns when the controller is implemented using the FMAC. However, the main core is now occupied for an additional 812 ns versus running the controller on the FMAC. Nevertheless, there is ample bandwidth to run other controllers or perform other functions when using either the main core or FMAC to implement the controller.

Figure 94. PWM (Ch1) and ADC ISR duration (Ch2)


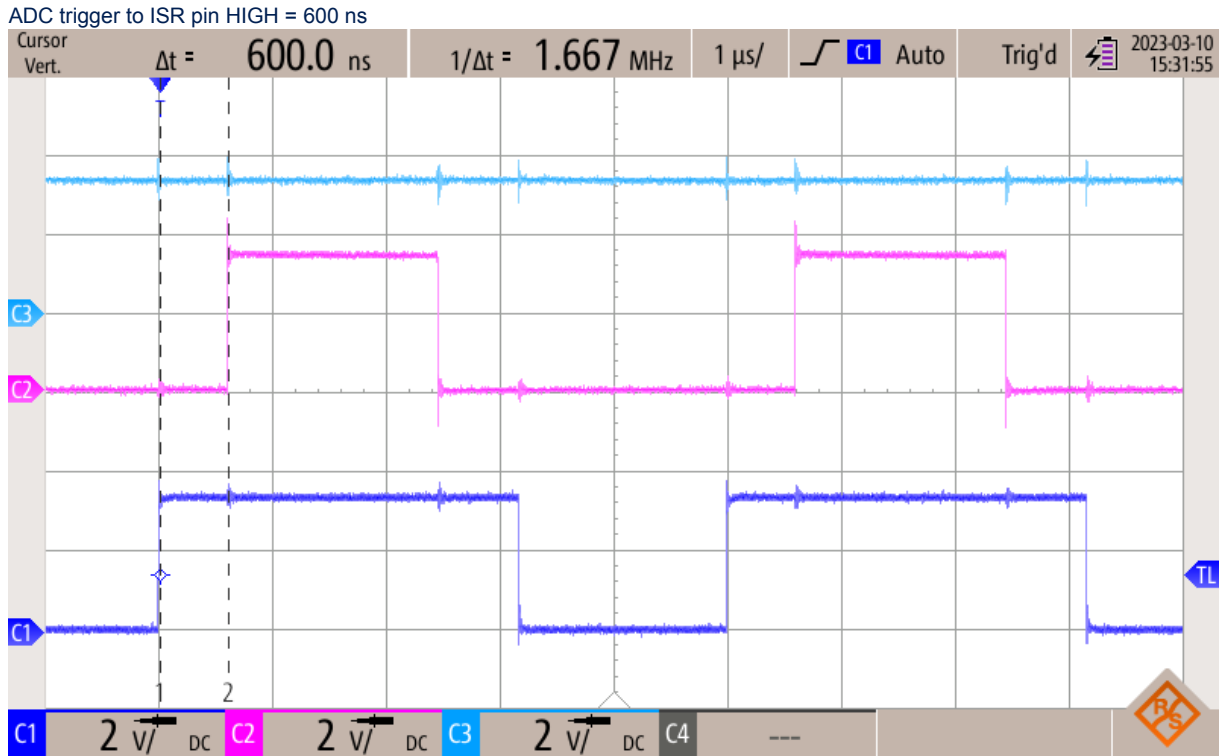


Figure 95. PWM (Ch1) and ADC ISR duration (Ch2)

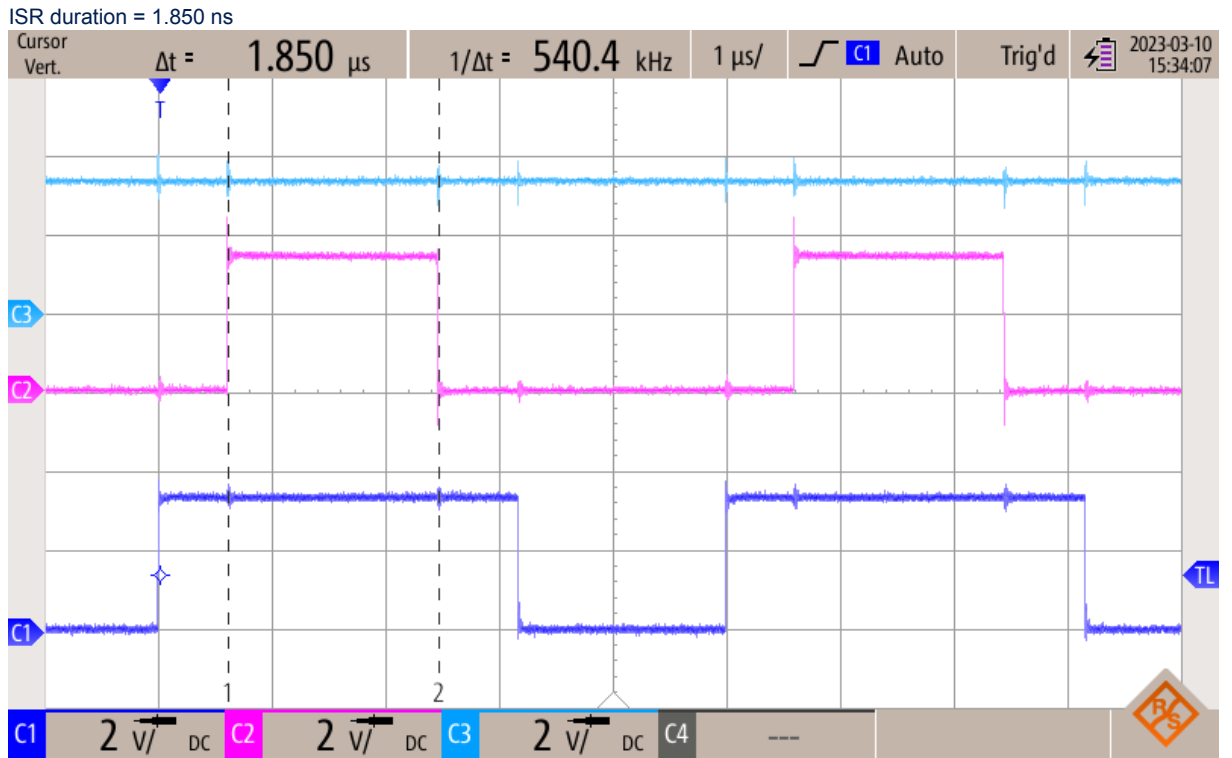

10 Summary

This application note provides a detailed explanation of the design and operation of the digitally controlled voltage mode step-down converter on the discovery kit. The controller is implemented using the FMAC on the STM32G4 MCU from STMicroelectronics.

This application note shows that the voltage mode step-down converter can be stabilized by applying control theory. The goal is to achieve a high crossover frequency and phase margin with an ideal transient response. The document provides all the equations necessary to calculate the digital controller coefficients. Additionally, the ST-WDS software tool from Biricha can be used to perform the same calculations with ease and obtain the required controller coefficients.

Several webinars are created to accompany this application note. Visit www.biricha.com/st to access the webinars related to this discovery kit.

Biricha digital power also runs regular hands-on training workshops that cover the principles of power supply design, the fundamentals of control theory, the transition to the discrete-time domain, and step-by-step embedded programming. These workshops are beneficial to both analog power supply design engineers who need to get familiar with digital power and embedded systems engineers who need to understand how to design and stabilize digital power supplies.

For more information on these workshops, visit www.biricha.com/st

11 Download links

- Discovery kit schematic and PCB design files:
www.st.com/stm32g4-dpower-disco
- Workshops and training:
www.biricha.com/st
- Project, ST WDS, Bode Analyzer Suite downloads:
www.biricha.com/ST-Discovery-Kit

Revision history

Table 10. Document revision history

Date	Version	Changes
19-Jun-2020	1	Initial release.
7-Dec-2022	2	Added <i>Section 8.8 Buck converter usage using the X-CUBE-DPower pack.</i>
6-Jan-2023	3	Updated <i>Introduction</i> about the buck voltage mode usage with X-CUBE-DPOWER.
29-Feb-2024	4	Updated: <ul style="list-style-type: none"> • Section 3.2: Step-by-step control loop • Section 6.2.4: HRTIM configuration • Section 6.5: 3p3z controller coefficients • Section 6.6: ST-WDS configuration • Section 8.1: Overall usage • Section 8.2: Loading the project • Section 8.4: Source files • Section 8.5: Open-loop operation • Section 8.7: Waveform display in IAR Systems® • Section 8.8.1: Configure the converter parameters using the GUI • Section 8.8.3: Topology dedicated files • Section 9.4: ISR plots (featuring FMAC and CPU load benefits) • Figure 34. Removing pin from the project • Figure 35. ADC parameter settings • Figure 39. Timer C configuration tab-part 2 • Figure 40. Timer C configuration tab - part 3 • Figure 72. Falling edge dead-time, Ch1: high-side FET, Ch2: low-side FET, dead-time measured as 147 ns • Figure 82. X-CUBE-DPower – GUI parameters for the step-down converter • Figure 92. PWM (Ch1) and FMAC ISR duration (Ch2) • Figure 93. PWM (Ch1) and FMAC ISR duration (Ch2) • Figure 94. PWM (Ch1) and ADC ISR duration (Ch2) • Figure 95. PWM (Ch1) and ADC ISR duration (Ch2)

Contents

1	General information	2
2	Step-down converter operation	3
2.1	Principle of operation	3
3	Voltage mode control explained	5
3.1	Advantages and disadvantages	5
3.2	Step-by-step control loop	5
3.3	Buck plant transfer function	7
3.4	Capacitor ESR zero	9
4	Voltage mode compensator design	11
4.1	Loop stability criteria	11
4.2	Crossover and phase margin specification	13
4.3	Types of compensators	14
4.4	Compensator pole/zero placement	15
5	Discrete-time controller	17
5.1	Bi-linear transform	17
5.2	3p3z controller	18
5.3	Pure time delays	20
5.4	Digital gains	22
6	Software implementation	23
6.1	Targeted application	23
6.2	Configuration using STM32CubeMX	23
6.2.1	Clock configuration	27
6.2.2	GPIO peripheral configuration	28
6.2.3	ADC peripheral configuration	32
6.2.4	HRTIM configuration	36
6.2.5	FMAC configuration	40
6.2.6	IRQ handler configuration	41
6.3	Program flow description	42
6.4	Interrupt service routine	46
6.5	3p3z controller coefficients	46
6.6	ST-WDS configuration	47
6.7	CCM-SRAM usage	57
7	Design example	58
7.1	Power stage component selection	58

7.1.1	Power inductor	59
7.1.2	Output filter capacitor	59
7.2	PCB layout	60
8	Getting started	61
8.1	Overall usage	61
8.2	Loading the project	62
8.3	Onboard load	67
8.4	Source files	67
8.5	Open-loop operation	69
8.6	Closed-loop control	72
8.6.1	Load regulation	72
8.6.2	Transient response	73
8.6.3	Impact of crossover frequency on the transient response	74
8.6.4	Impact of phase margin on the transient response	75
8.6.5	Bode plot measurement under closed-loop control	76
8.7	Waveform display in IAR Systems®	77
8.8	Step-down converter usage with the X-CUBE-DPower pack	81
8.8.1	Configure the converter parameters using the GUI	81
8.8.2	Command the converter using board UI	82
8.8.3	Topology dedicated files	82
8.8.4	State machine	83
9	Measurements	84
9.1	Load regulation	84
9.2	Transient response tests	87
9.3	Frequency response measurement results	89
9.4	ISR plots (featuring FMAC and CPU load benefits)	91
10	Summary	95
11	Download links	96
	Revision history	97
	List of tables	100
	List of figures	101

List of tables

Table 1.	User label setting	30
Table 2.	Discovery kit specification	48
Table 3.	Semiconductors tab parameter	50
Table 4.	Output filter parameters	51
Table 5.	Controller design parameters.	53
Table 6.	Digital nonisolated parameters.	54
Table 7.	Power stage parameters	59
Table 8.	Onboard load steps	67
Table 9.	Closed-loop load regulation.	72
Table 10.	Document revision history	97

List of figures

Figure 1.	B-G474E-DPOW1 top view	1
Figure 2.	B-G474E-DPOW1 bottom view	1
Figure 3.	Simplified power stage schematic	3
Figure 4.	Step-down converter operational waveforms	4
Figure 5.	Step-down converter voltage control loop	5
Figure 6.	PWM comparator comparing RC ramp to control voltage	6
Figure 7.	LC output filter of the step-down converter power stage	7
Figure 8.	Bode plot of the LC filter transfer function	8
Figure 9.	Ideal capacitor and capacitor with parasitic elements	9
Figure 10.	Ideal inductor and inductor with parasitic elements	9
Figure 11.	Closed and open-loop transfer functions	11
Figure 12.	Open-loop Bode plot of the step-down converter: plant, PWM, and compensator	12
Figure 13.	Step response for a system with decreasing crossover and phase margin (grey to green)	13
Figure 14.	Type-III compensator implemented in analog using op-amp	14
Figure 15.	Continuous-time signal sampled in discrete time using a trapezoidal approximation	17
Figure 16.	Trapezoidal approximation mapping from s to z-domain	18
Figure 17.	3p3z controller structure	19
Figure 18.	Sources of delay within the discrete-time system	20
Figure 19.	Time delay relationship to phase delay	21
Figure 20.	Additional gains within the digital system	22
Figure 21.	STM32CubeMX icon	23
Figure 22.	New project selection	23
Figure 23.	Board selection	24
Figure 24.	Peripherals default mode initialization	24
Figure 25.	Project naming	25
Figure 26.	Project saving	25
Figure 27.	Project manager configuration	26
Figure 28.	Clock configuration window	27
Figure 29.	GPIO peripheral configuration window	28
Figure 30.	GPIO renaming	29
Figure 31.	GPIO maximum output speed setting	30
Figure 32.	Pins location	31
Figure 33.	DMA mode and configuration screen	32
Figure 34.	Removing pin from the project	33
Figure 35.	ADC parameter settings	34
Figure 36.	NVIC settings tab	35
Figure 37.	All timers except C disabled	36
Figure 38.	Timer C configuration tab - part 1	37
Figure 39.	Timer C configuration tab-part 2	38
Figure 40.	Timer C configuration tab - part 3	38
Figure 41.	Timer C configuration tab - part 4	39
Figure 42.	ADC triggers configuration	40
Figure 43.	FMAC configuration window	40
Figure 44.	Automatic IRQ handler generation disabled	41
Figure 45.	Code generation launch	41
Figure 46.	Project opening after code generation	41
Figure 47.	Program flow within main.c	42
Figure 48.	Example of user code locations within main.c	43
Figure 49.	Function flow of main() within main.c	44
Figure 50.	ADC, DMA, and FMAC timing diagram	45
Figure 51.	FMAC ISR flow	46
Figure 52.	Biricha ST-WDS	47
Figure 53.	ST-WDS specification tab	49

Figure 54.	ST-WDS semiconductor tab	50
Figure 55.	ST-WDS output filter tab	52
Figure 56.	ST-WDS controller design tab	54
Figure 57.	ST-WDS digital nonisolated tab	55
Figure 58.	Fixed point controller coefficient calculation in ST-WDS	56
Figure 59.	Discovery kit schematic: buck-boost power stage	58
Figure 60.	Step-down converter simplified power stage	58
Figure 61.	Hardware layout of the power stage	60
Figure 62.	Example.ico	62
Figure 63.	Code generation	62
Figure 64.	Project opening	62
Figure 65.	Example options	63
Figure 66.	ST-LINK version selection	64
Figure 67.	Code compilation and downloading	65
Figure 68.	Program counter set for running	66
Figure 69.	Top menu buttons	66
Figure 70.	Onboard load banks controlled via MOSFETs	67
Figure 71.	Rising edge dead-time, Ch1: high-side FET, Ch2: low-side FET, dead-time measured as 54 ns	70
Figure 72.	Falling edge dead-time, Ch1: high-side FET, Ch2: low-side FET, dead-time measured as 147 ns	71
Figure 73.	Output voltage (Ch3) transient from load change 50% to 100% (Ch1)	73
Figure 74.	Impact of crossover frequency	74
Figure 75.	Impact of phase margin on the transient response	75
Figure 76.	Connection setup for control-to-output transfer function measurement	76
Figure 77.	Loop measurement at 100% load imported into ST-WDS	77
Figure 78.	Add the data log breakpoint to capture the variable each time it is updated	78
Figure 79.	Enabling timeline view	79
Figure 80.	Timeline pane	80
Figure 81.	Timeline view with an adjusted scale	80
Figure 82.	X-CUBE-DPower – GUI parameters for the step-down converter	81
Figure 83.	X-CUBE-DPower – step-down converter state machine	83
Figure 84.	Output voltage (Ch3) and PWM (Ch1) at 0% load	84
Figure 85.	Output voltage (Ch3) and PWM (Ch1) at 50% load	85
Figure 86.	Output voltage (Ch3) and PWM (Ch1) at 100% load	86
Figure 87.	Output voltage (Ch3) transient from load change 50% to 100% (Ch1)	87
Figure 88.	Output voltage (Ch3) transient from load change 0% to 50% (Ch1)	88
Figure 89.	Measured loop response of the digital voltage mode loop at 100% load	89
Figure 90.	Measured loop response of the digital voltage mode loop at 50% load	90
Figure 91.	Measured loop response of the digital voltage mode loop at 0% load	90
Figure 92.	PWM (Ch1) and FMAC ISR duration (Ch2)	91
Figure 93.	PWM (Ch1) and FMAC ISR duration (Ch2)	92
Figure 94.	PWM (Ch1) and ADC ISR duration (Ch2)	93
Figure 95.	PWM (Ch1) and ADC ISR duration (Ch2)	94

IMPORTANT NOTICE – READ CAREFULLY

STMicroelectronics NV and its subsidiaries (“ST”) reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST’s terms and conditions of sale in place at the time of order acknowledgment.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of purchasers’ products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. For additional information about ST trademarks, refer to www.st.com/trademarks. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2024 STMicroelectronics – All rights reserved