

---

**VIPower™: low consumption standby power  
with the VIPerx2A family**

---

**Introduction**

The new regulation on the power supply standby consumption for the battery charger is more and more stringent. Thanks to the VIPerx2A family low power consumption, a battery charger can be built in standby mode with no-load of 100 mW. This charger solution with the VIPer12A-E is presented in [Table 1](#).

Some general features:

- Ultra low standby power dissipation
- Burst mode operation in standby
- 72% typical efficiency
- Current mode controller
- Output short-circuit protection
- Thermal shutdown protection

**Table 1. Operation conditions**

Parameters	Limits
Input voltage range	90 to 264 VAC
Input frequency range	50 to 60 Hz
Output voltage	5 V
Output current	800 mA
Output power	4 W
Efficiency	72% typical
Line regulation	0.5%
Load regulation	1%
Output ripple	30 mVpp
Safety	Short-circuit protection


# Contents

- 1 Description ..... 3**
- 2 General circuit description ..... 4**
- 3 Charger application ..... 6**
  - 3.1 Schematic general description ..... 6
  - 3.2 Solutions for energy saving ..... 6
  - 3.3 Performance results ..... 7
    - 3.3.1 Input power consumption at no-load condition ..... 7
    - 3.3.2 Standby operation ..... 8
    - 3.3.3 Load, line regulation and efficiency ..... 9
    - 3.3.4 Load transient ..... 10
    - 3.3.5 Switching waveforms of normal operation at full load ..... 10
- 4 Transformer specification ..... 11**
- 5 Bill of material ..... 12**
- 6 Conclusions ..... 13**
- 7 Revision history ..... 14**

# 1 Description

The VIPer12A-E is a high voltage integrated circuit intended to be used as a primary side switch on the offline power supply, in a monolithic structure housed in DIP8 or SO-8 package. It includes a PWM driver, a power MOSFET with 730 V breakdown voltage, a start-up circuit and several protection circuits. It minimizes the count of external parts, reduces the product size and power consumption. This application note describes the results obtained when the VIPer12A-E is used in mobile charger applications.

Figure 1. Evaluation board bottom foil (not in scale)

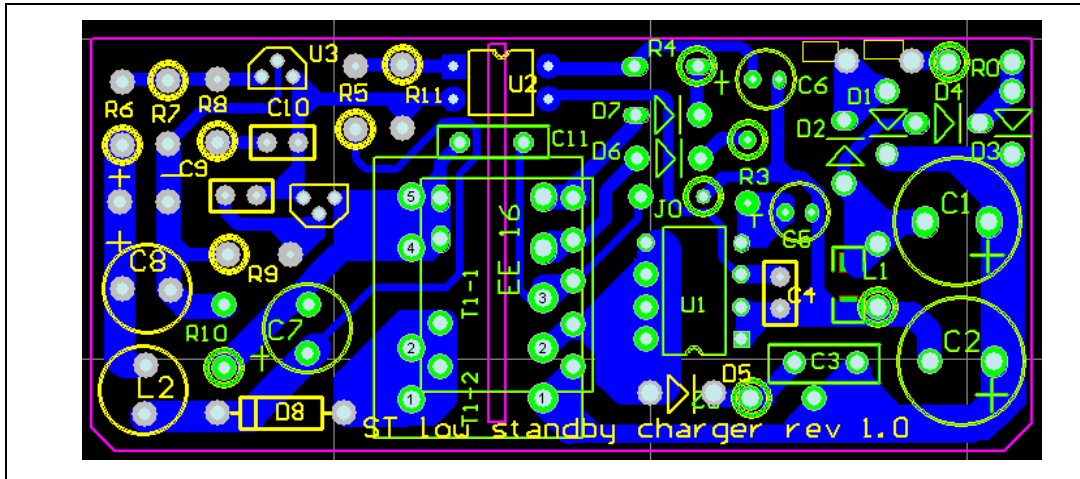


## 2 General circuit description

This board is a flyback regulator, delivering 0.8 A to 5 V. The AC input is rectified and filtered by the diodes D1, D2, D3, D4, the bulk capacitor C1, and C2 to generate the high voltage DC bus applied to the primary winding of the transformer, TR1. C1, L1, and C2 provide EMI filtering for the circuit. D9 and D10 form the snubber circuit, which reduces the leakage spike and voltage ringing on the drain pin of the VIPer12A-E.

The output voltage is regulated by a TL431 (U3) via an optocoupler (U2) to the feedback pin. The output voltage ripple is controlled by the capacitor, C7, with an additional LC PI filter configuration made up of L2 and C8. The output voltages can be modified by changing the transformer turn ratio and modifying the R6 and R7 resistance values in the feedback loop.

Figure 2. Application schematic

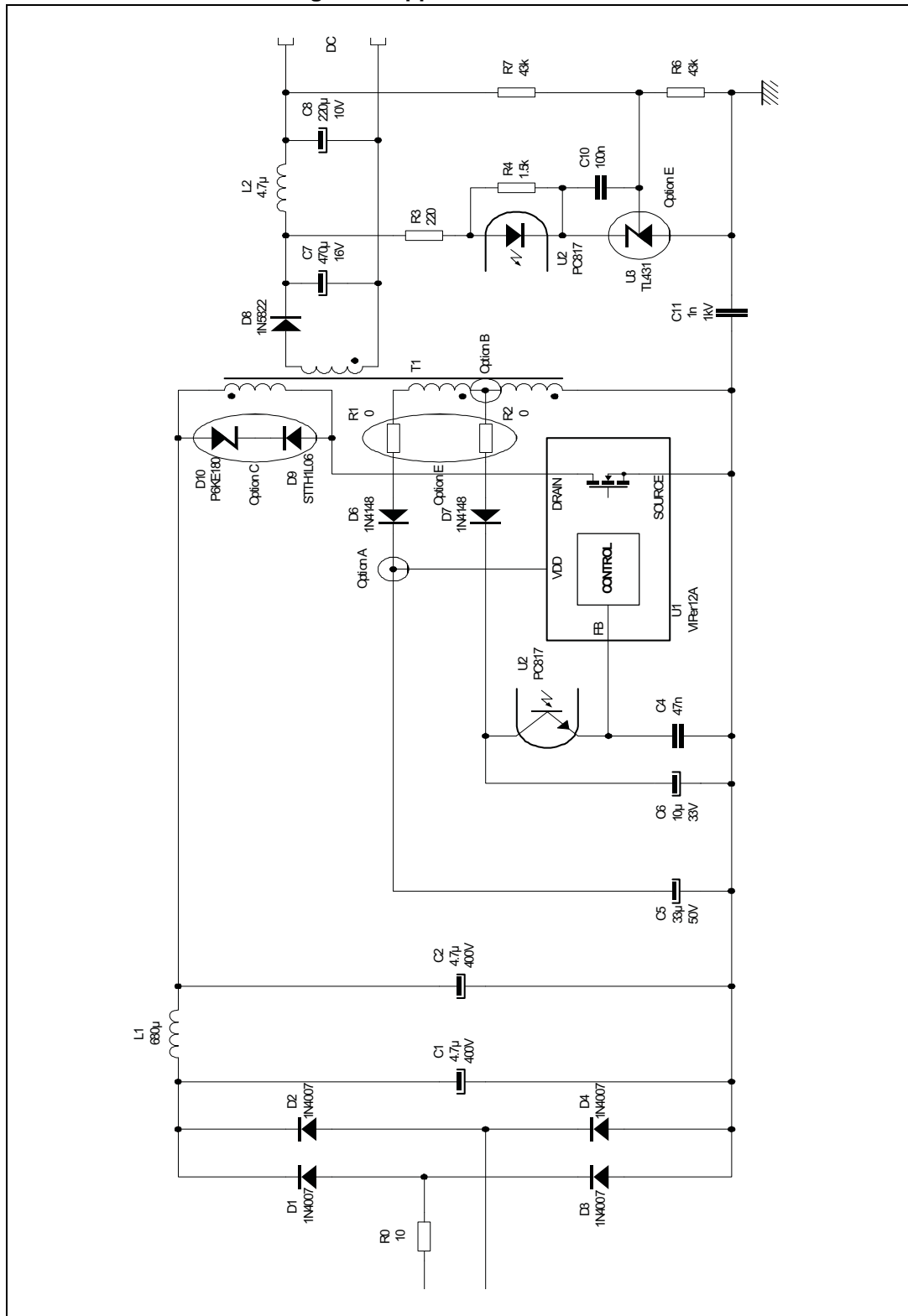

## 3 Charger application

### 3.1 Schematic general description

As the total input power dissipation at no-load condition of this solution is less than 0.1 W, the power losses of each component have to be saved. Below the major approaches adopted in this evaluation board.

### 3.2 Solutions for energy saving

1. Losses of the VIPer12A-E controller.

The power losses of the VIPer12A-E control part can be calculated by below formula:

$$P_{\text{viper}} = V_{\text{dd}} \cdot I_{\text{dd1}}$$

where:

-  $V_{\text{dd}}$  is the supply voltage of the VIPer12A-E control part (range: 9 V-38 V)

-  $I_{\text{dd1}}$  is the operation current of the VIPer12A-E control part (typical value: 4.5 mA)

$V_{\text{dd}}$  is set by considering two operative conditions; if the VIPer12A-E power has to be saved, the  $V_{\text{dd}}$  value has to be lowered and, at the same time the  $V_{\text{dd}}$  has to be higher than 10 V, which is the required normal operation value of the VIPer12A-E (with 1 V margin).

$V_{\text{dd}}$  value (10 V) fixes the suitable turn ratio between secondary and auxiliary winding.

2. Optimized voltage source for optocoupler.

In a flyback topology, the voltage source of the optocoupler primary side is normally connected to the  $V_{\text{dd}}$  of the IC directly, but in this board, in order to save energy, another winding is inserted in the transformer to supply the optocoupler; the voltage supplied by this winding is lower than the  $V_{\text{dd}}$  value (typical value 3 V).

3. Snubber circuit configuration.

An RCD clamp is a popular cheap solution, however it dissipates power even at no-load condition, in fact there is a reflected voltage across the clamp resistor all the time. The power losses on the resistor can be calculated as follows:

$$P_R = \frac{V_R^2}{R_{\text{min}}} + \frac{1}{2} \cdot L_{\text{LK}} \cdot I_{\text{lim}}^2 \cdot f_{\text{sw}}$$

where  $V_R$  is the reflected voltage;  $R_{\text{min}}$  is the resistor value;  $L_{\text{LK}}$  is the leakage inductance;  $I_{\text{lim}}$  is the peak current limitation value of the VIPer12A-E and  $f_{\text{sw}}$  is the switching frequency.

As at no-load condition, the energy  $\frac{1}{2} \cdot L_{\text{LK}} \cdot I_{\text{lim}}^2$  can be neglected, then the RCD losses could be considered as:

$$P_R = V_R \cdot V_R / R_{\text{min}}$$

in this case with  $V_R=70$  V,  $R_{\text{min}}=82$  k $\Omega$ ,  $P_R$  is around 60 mW.

This 60 mW power at no-load condition can be saved using the transil clamp to replace the RCD configuration in the snubber circuit.

4. Optional for the voltage reference devices (TS431 or TL431 or Zener)

The TS431, the TL431 and the Zener can be used as voltage regulators. The TS431 shows the low minimum operation current with the typical value of 150 A. This feature is quite useful, because the biasing resistor can be removed without any voltage regulation performance loss. With this device, the power losses can be saved on the biasing resistor with typical value of 5-8 mW.

The TL431 is a cost-effective solution for the constant voltage. The weakness of this device, in this special application, is its operation current higher than 1 mA. In order to get good voltage regulation performance at full load condition, a biasing resistor is very important, but this leads to an additional power loss.

If the requirement of the output voltage performance is not so tight, a Zener can be used as voltage reference. The standby power in no-load condition is lower than 0.1 W with the 3 optional solutions of voltage reference above. The best solution depends on customers' requests.

5. The short-circuit of resistors for current limitation on the auxiliary windings.

### 3.3 Performance results


#### 3.3.1 Input power consumption at no-load condition

Table 2. Standby power

Input power consumption		
V <sub>IN</sub>	I <sub>IN</sub>	P <sub>IN</sub>
100 V <sub>dc</sub>	505 μA	50.5 mW
300 V <sub>dc</sub>	252 μA	75.6 mW
380 V <sub>dc</sub>	215 μA/203 μA	81.7 mW/77.2 mW


As shown in [Table 1](#), the standby power is measured at DC voltage input in order to have more precision in the input power data. At the high line input of 380 V<sub>dc</sub> input, this board standby power is around 82 mW (with the TL431).

Figure 3. Standby consumption at 380 V<sub>dc</sub> input

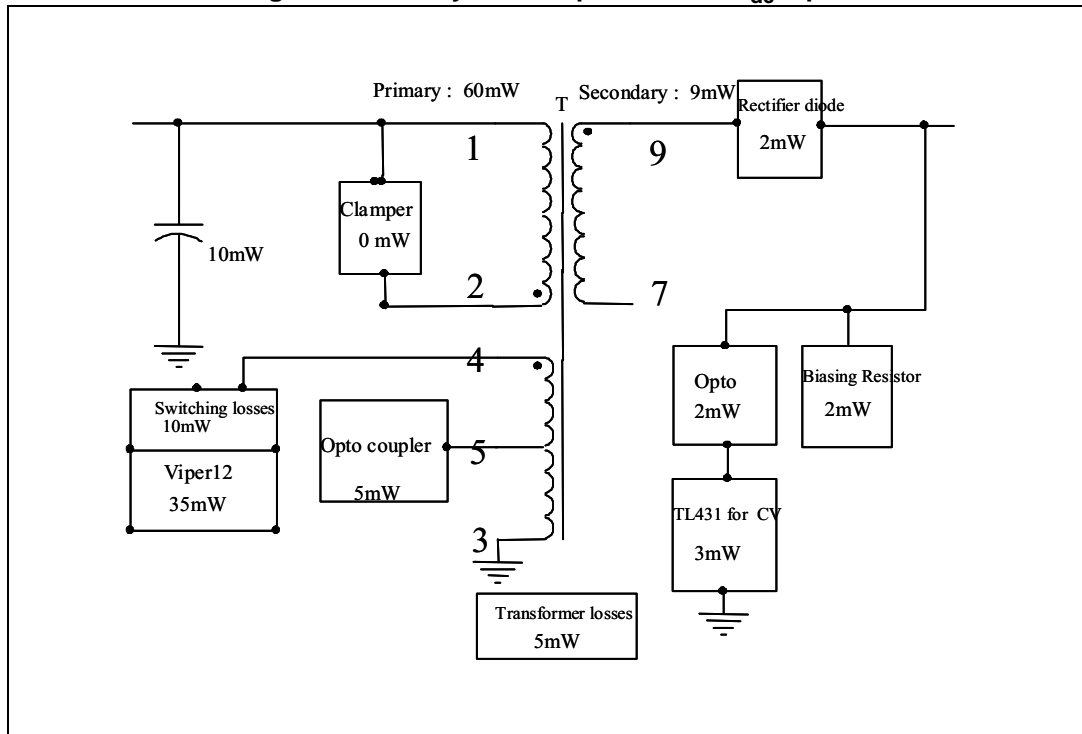

3.3.2 Standby operation

Figure 4. V<sub>ds</sub> and I<sub>d</sub> at burst mode

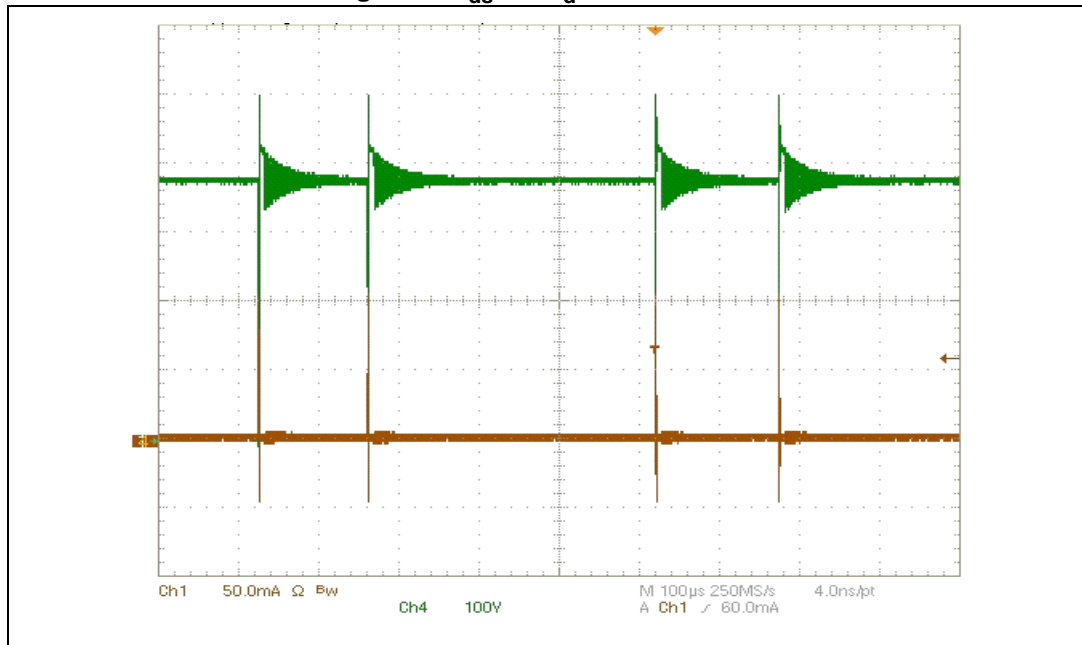


When no-load is applied to the secondary side, the VIPer12A-E works in burst mode by skipping some switching cycles and this behavior is shown in [Figure 4](#). Thanks to this feature, the VIPer12A-E can save a lot of the switching losses reducing the standby power consumption.




### 3.3.3 Load, line regulation and efficiency

Figure 5. Load regulation

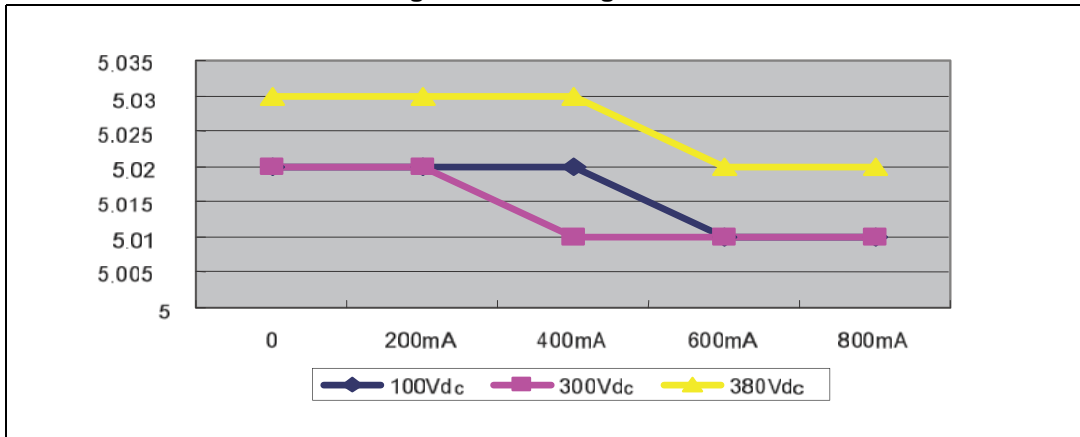

The output load changes from 0 A to full load 0.8 A while the line input voltage is set as 100 V<sub>dc</sub>, 300 V<sub>dc</sub>, 380 V<sub>dc</sub>. The board has a load, line regulation lower than 1%.

Figure 6. System efficiency

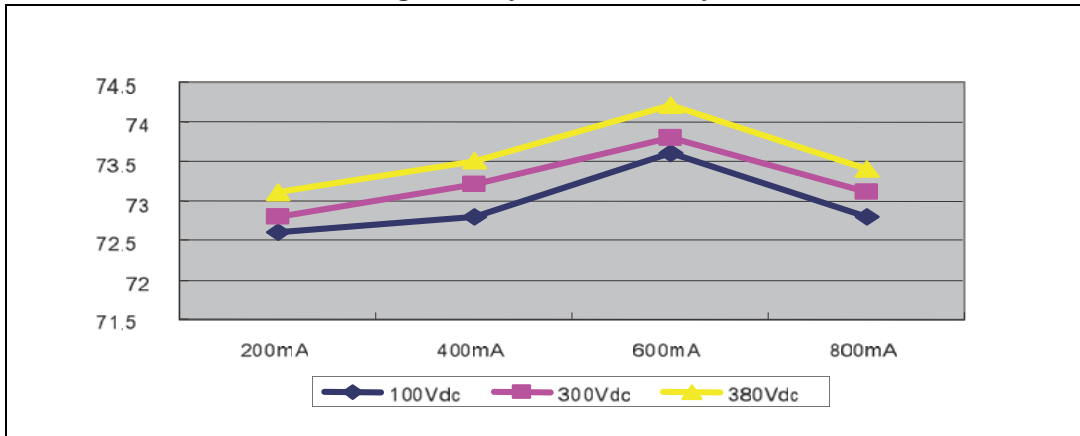

The measurements are based on input voltage of 100 V<sub>dc</sub>, 300 V<sub>dc</sub>, 380 V<sub>dc</sub>. The typical efficiency measured is about 73%. [Figure 6](#) shows the efficiency measured when I<sub>OUT</sub> is set at different values from 200 mA to maximum value of 800 mA.

### 3.3.4 Load transient

Figure 7.  $V_{ds}$  and  $I_d$  at  $V_{IN}=100\text{ V}_{dc}$ ,  $P_{OUT}=4\text{ W}$  - 50 mV/division


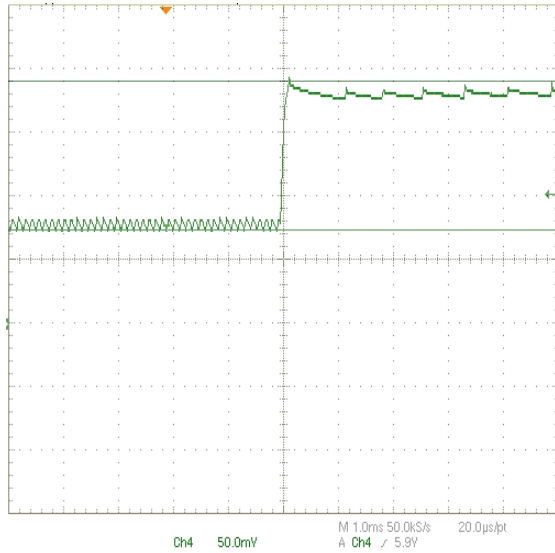


Figure 8.  $V_{ds}$  and  $I_d$  at  $V_{IN}=380\text{ V}_{dc}$ ,  $P_{OUT}=4\text{ W}$  - 50 mV/division

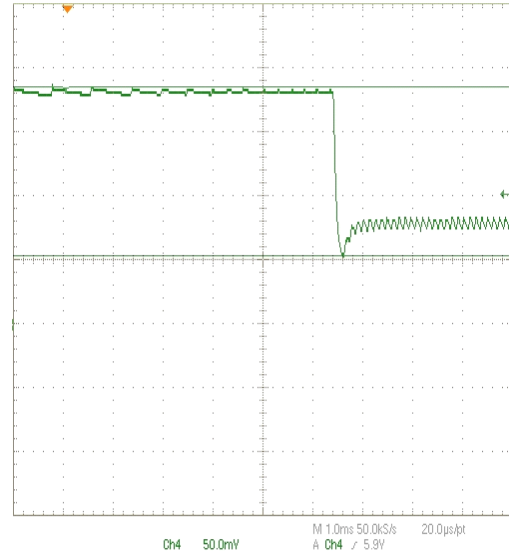

As shown in [Figure 7](#) and [Figure 8](#) the maximum overshoot and undershoot value of the output voltage is less than 150 mV at transient tests.

### 3.3.5 Switching waveforms of normal operation at full load

Figure 9.  $V_{ds}$  and  $I_d$  at  $V_{IN}=100\text{ V}_{dc}$ ,  $P_{OUT}=4\text{ W}$

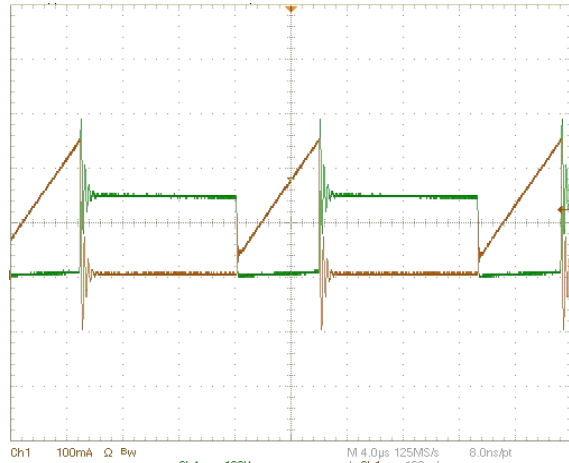


Figure 10.  $V_{ds}$  and  $I_d$  at  $V_{IN}=380\text{ V}_{dc}$ ,  $P_{OUT}=4\text{ W}$




[Figure 8](#) and [Figure 9](#) show the drain voltage and drain current during normal operation at full load. The power supply operates in the continuous current mode at low line input and in discontinue current mode at high line input as seen from the waveforms.

## 4 Transformer specification

Table 3. Transformer characteristics

Winding description	Symbol	Number turns	Wire size	Start pin	End pin	Remarks
Primary	P1	145	0.19 mm	2	1	EE-16; $L_p = 2.5$ mH at 1 V, 1 kHz
Secondary	S1	11	0.50 mm	9	7	Tipple isolated wire
Auxiliary1	A1	16	0.10 mm	4	5	
Auxiliary2	A2	15	0.10 mm	5	3	

Figure 11. Transformer structure

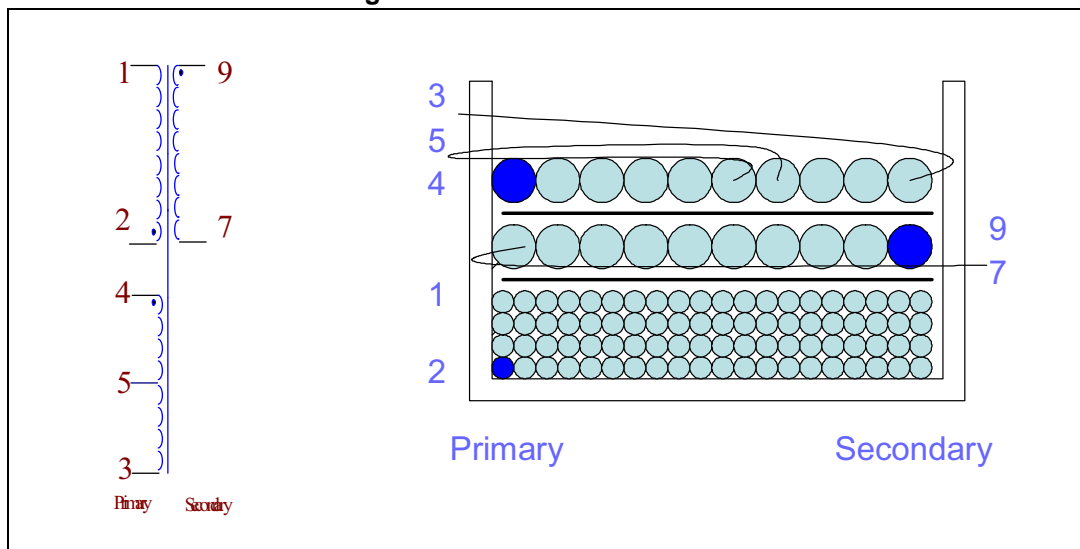

## 5 Bill of material

**Table 4. Bill of material**

Symbol	Part list description	Note
C1,C2	Elect Cap 4.7 $\mu$ F/400 V	
C4	47 nF/25 V	
C5	Elect cap 33 $\mu$ F/25 V	
C6	Elect cap 10 $\mu$ F/6.3 V	
C7	Elect cap 470 $\mu$ F/16 V	
C8	Elect cap 220 $\mu$ F/10 V	
C10	Film 100 nF/50 V	
C11	Y cap 1 nF/1 KV	
R0	10 $\Omega$	Fuse
R1,R2	0 $\Omega$	
R3	220 $\Omega$	
R4	1.5 K $\Omega$	TL431:1.5 K/TS431: remove
R6	43 K $\Omega$	
R7	43 K $\Omega$ /130 K $\Omega$	TL431:43 K/TS431: 130 K
D1,D2,D3,D4	1N4007	
D6,D7	1N4148	
D8	1N5822	
D9	STTH1L06	
D10	P6KE180	
L1	680 $\mu$ H	
L2	4.7 $\mu$ H	
T1	2.7 mH EE-16 vertical	
U1	VIPer12A-E	
U2	PC817	
U3	TL431/TS431	

## 6 Conclusions

When the board works in standby, it consumes less than 0.1 W meeting the “Blue Angel” norm. The total power consumption measured at 100 V<sub>dc</sub> input with zero load on output is approximately 50 mW, while at 380 V<sub>dc</sub> input this value is about 80 mW.

This unit operates in burst mode when the output load is reduced to zero and normal operation is resumed automatically when the power gets back to a level higher than the standby power. The output voltage remains regulated even when the board works in burst mode.

## 7 Revision history

**Table 5. Document revision history**

Date	Revision	Changes
10-Nov-2014	2	Content reworked to improve readability, no technical changes.

**IMPORTANT NOTICE – PLEASE READ CAREFULLY**

STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST's terms and conditions of sale in place at the time of order acknowledgement.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers' products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2014 STMicroelectronics – All rights reserved